


Problem 1: Design of a PI current controller

The parameters of a DC motor are $R = 0.87 \Omega$ and $L = 16 \text{ mH}$. An ordinary PI current controller is used. The current-control bandwidth is required to be $\alpha_c = 2\pi \cdot 300 \text{ rad/s}$.

- (a) Derive the expressions for the controller gains according to the principle of internal model control.
- (b) Derive the expressions for the controller gains by cancelling the pole of the open-loop system and by requiring that the 0-dB crossover angular frequency of the loop transfer function is α_c .

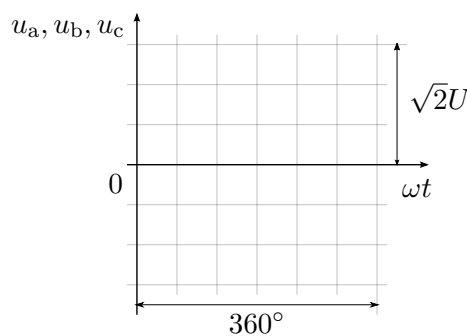Problem 2: Waveforms in a balanced three-phase system

Sketch the waveforms of balanced three-phase voltages on the squared paper (or the grid below).



Hint: It is convenient to use a 6×6 grid to draw these waveforms. You can first mark the points corresponding to zero crossings and peak values. It is also worth noticing that $\cos(60^\circ) = 1/2$ and mark these points on the grid.

Problem 3: Power in single-phase and three-phase systems


The purpose of this problem is to demonstrate that the instantaneous power in a balanced three-phase system is constant in steady state.

- (a) A single-phase load is fed with the voltage $u(t) = \sqrt{2}U \cos(\omega t)$ and it draws the current $i(t) = \sqrt{2}I \cos(\omega t - \varphi)$. Derive the expressions for the instantaneous power and the average power.


Hint: The trigonometric product-to-sum identity may be useful:

$$\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$$

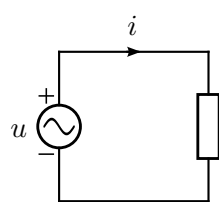- (b) A balanced three-phase load is fed with balanced three-phase voltages. Derive the expressions for the instantaneous power and the average power.



(a)

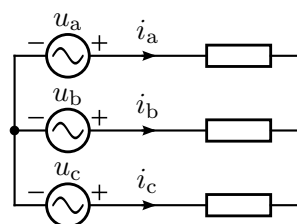

(b)

Problem 4: Transmission losses

The figure below shows two different configurations to feed the same power to the resistive load:

- (a) The balanced three-phase supply feeds the three resistors R_{load} . The resistance of the transmission wires is R .
- (b) The single-phase supply, taken from one phase of the previous three-phase supply, feeds the load resistor $R_{load}/3$. The same transmission wires are also used as in the previous case.

The resistance R of the wires can be assumed to be much smaller than the resistance R_{load} . Compare the transmission losses in these two cases.

