

# Ch 7. Alternating Current Circuits

- Lecture outcomes (what you are supposed to learn):
  - Root Mean Square (tehollisarvot)
  - Phase and Phase shift (vaihekulma ja vaihesiirto)
  - Phasors as vectors and complex numbers (osoitin)
  - Real, Reactive, Complex power (Pätö- , Lois-, Näennäisteho)
  - Power factor (tehokerroin)
  - Electric energy

# Introduction

- Electricity discovered around 600 BC
- Extensive use started at the end of 19<sup>th</sup> century
- Batteries produce DC-voltage
- DC generator or Dynamo at beginning of 19<sup>th</sup> century
- DC power system for lighting 1882
  - Low voltage (100 V)
  - Large losses and voltage drop in wires
- AC motor and generator + transformer
- AC power system with high voltage



Courtesy of CRC Press/Taylor & Francis Group



Courtesy of CRC Press/Taylor & Francis Group

# Why AC won the battle ?

- Voltage level can be adjusted with transformers
- High-voltage allow for long transmission lines
  - Low losses
  - Low wire cross-section
- AC system produce rotating field necessary to spin motors
- Is the battle over? Rectifiers, inverters, HVDC, local DC



Courtesy of CRC Press/Taylor & Francis Group

Where dc-system won?

# Basic quantities

- Waveform

$$v = V_{\max} \sin \omega t$$



- Frequency (taajuus):

$$f = \frac{\omega}{2\pi}$$

- Root Mean Square (tehollisarvo)

- Makes it possible to quantify distorted waves
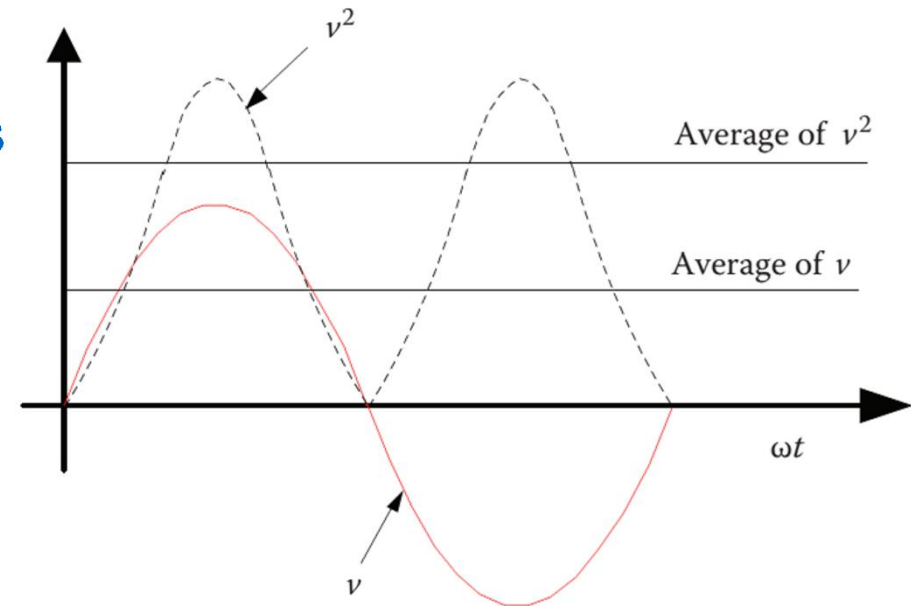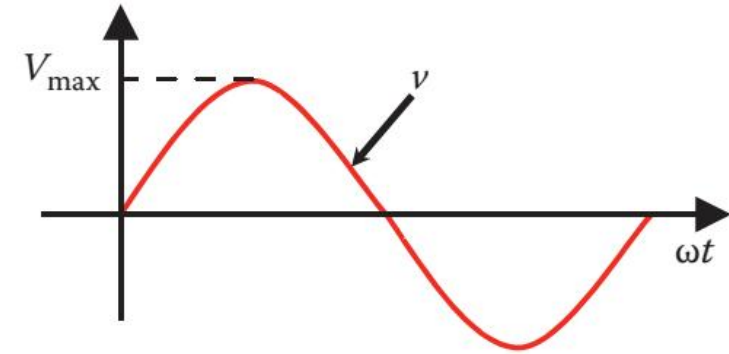
$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$




# Phase shift

- Waveform

$$v = V_{\max} \sin \omega t$$


- Resistive load:

$$i = \frac{V_{\max}}{R} \sin \omega t$$

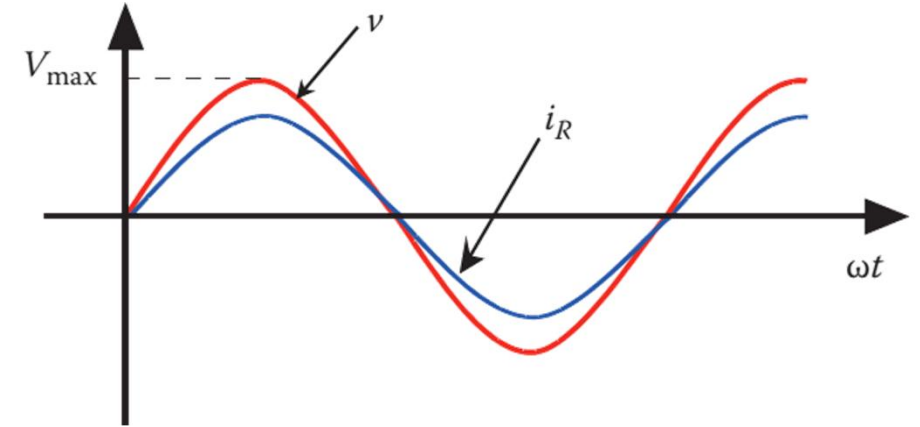

- Inductive load:
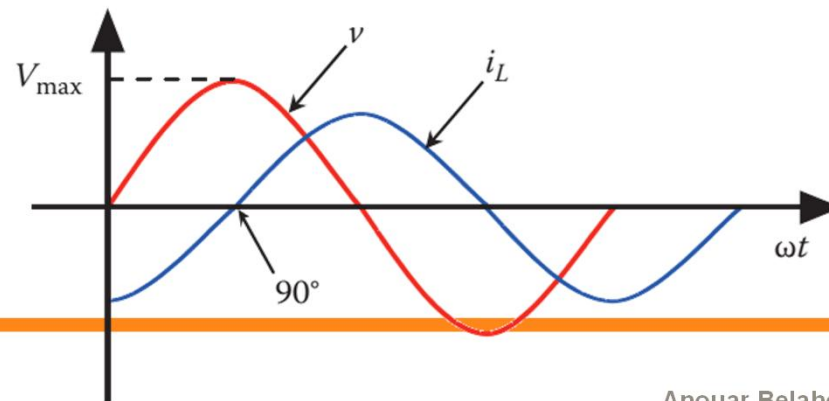
$$i = \frac{1}{L} \int_0^t v dt = -\frac{V_{\max}}{\omega L} \cos \omega t$$



$\omega L = X_L$   
Reactance

# Phase shift

- Waveform

$$v = V_{\max} \sin \omega t$$

- Capacitive load:

$$i = C \frac{dv}{dt} = \omega C V_{\max} \cos \omega t$$



- Complex load:

$$i = I_{\max} \sin(\omega t - \theta)$$

What is the unit of reactance

$$\frac{1}{\omega C} = X_c$$


Reactance

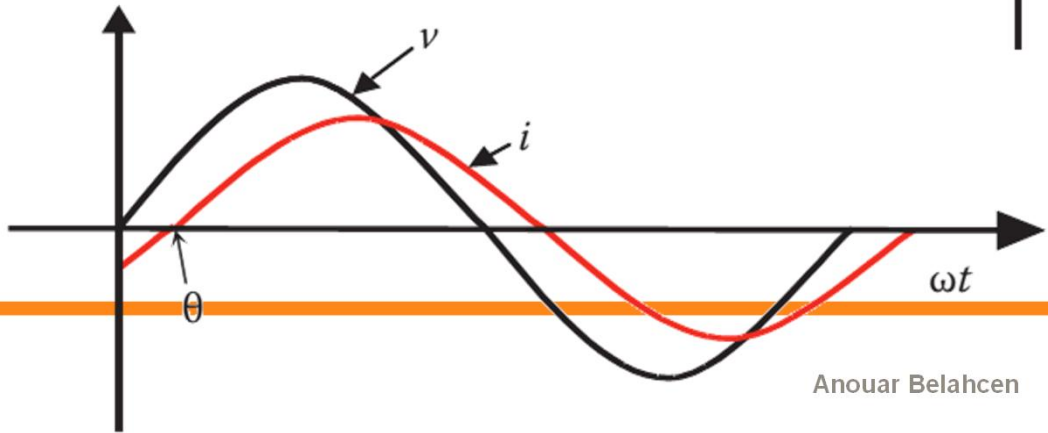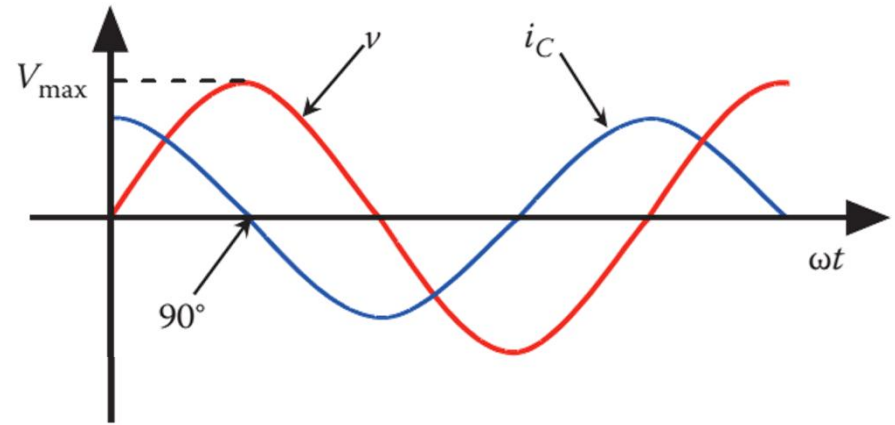

Anouar Belahcen
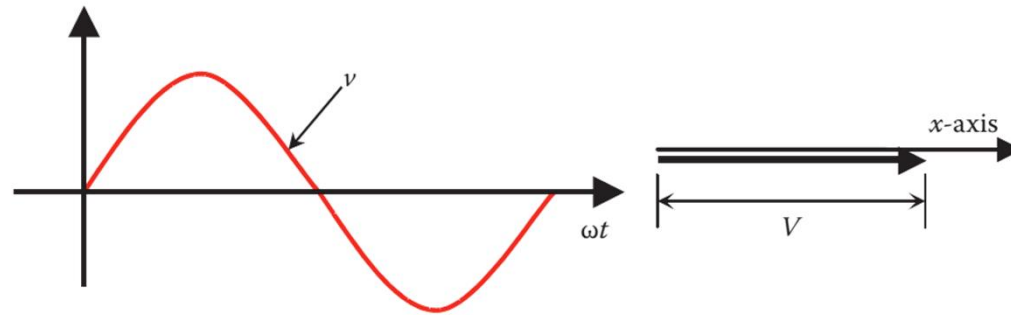
# Concept of Phasors


- Graphical representation with mathematical basis
- Give quick information on magnitude and phase shifts



- Vector length proportional to rms value
- Angle with respect to  $x$ -axis equals to phase shift
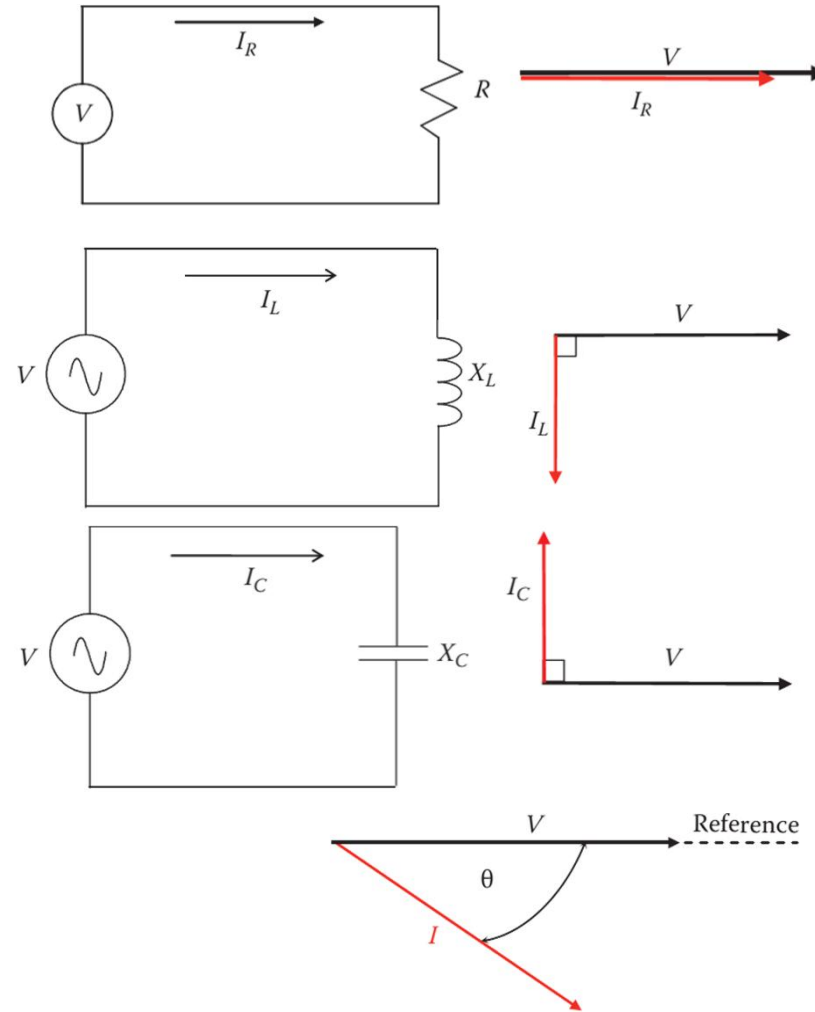
# Concept of Phasors


- Resistive load
- Inductive load
- Capacitive load
- Complex load






# Lagging and leading phase shifts


## Current lagging voltage

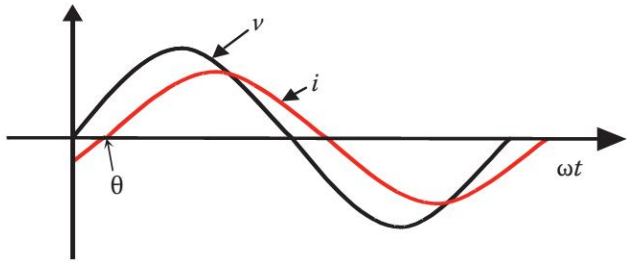

$$i = I_{\max} \sin(\omega t - \theta)$$

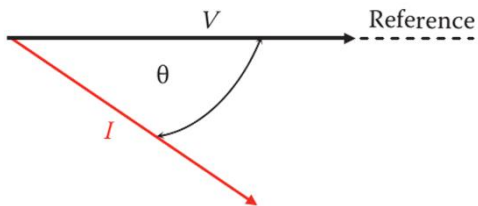


## Current leading voltage

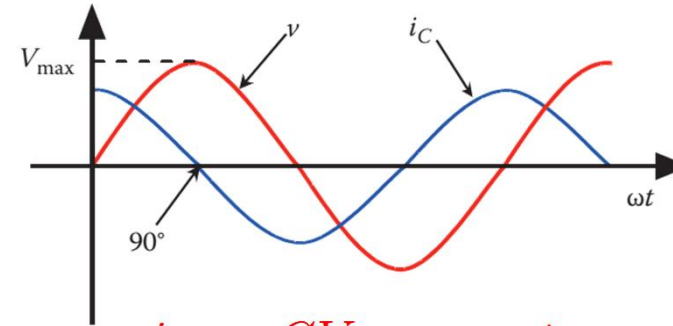



$$i = \omega C V_{\max} \cos \omega t$$
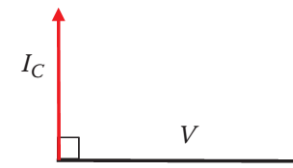
$$= \omega C V_{\max} \sin\left(\omega t + \frac{\pi}{2}\right)$$


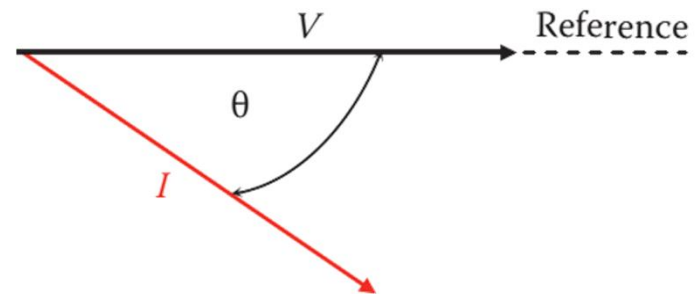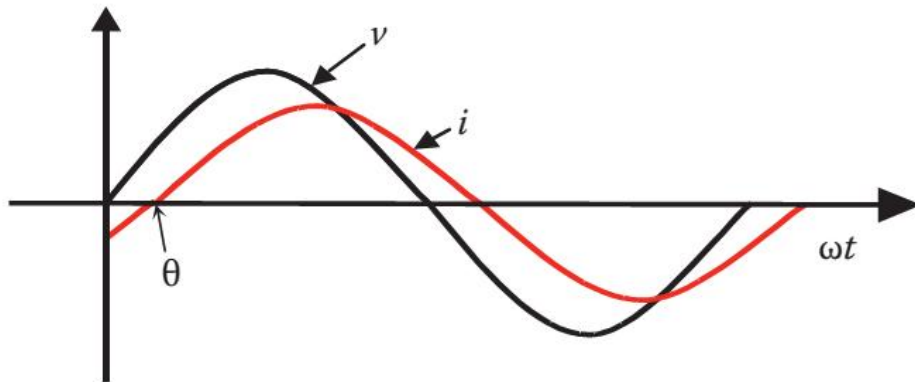
# Complex representation of Phasors

- Phasors are good visuals but not convenient to compute
- Vectors can be represented as complex numbers
- Calculus with complex number is handy.



$$\bar{V} = V \angle 0^\circ$$

$$\bar{I} = I \angle -\theta^\circ$$

# Complex numbers calculus

$$\bar{A} = A\angle\theta^\circ = A[\cos\theta + j\sin\theta] = X + jY$$

- Real component


$$A\cos\theta = X$$

- Imaginary component

$$A\sin\theta = Y$$

- Conjugate
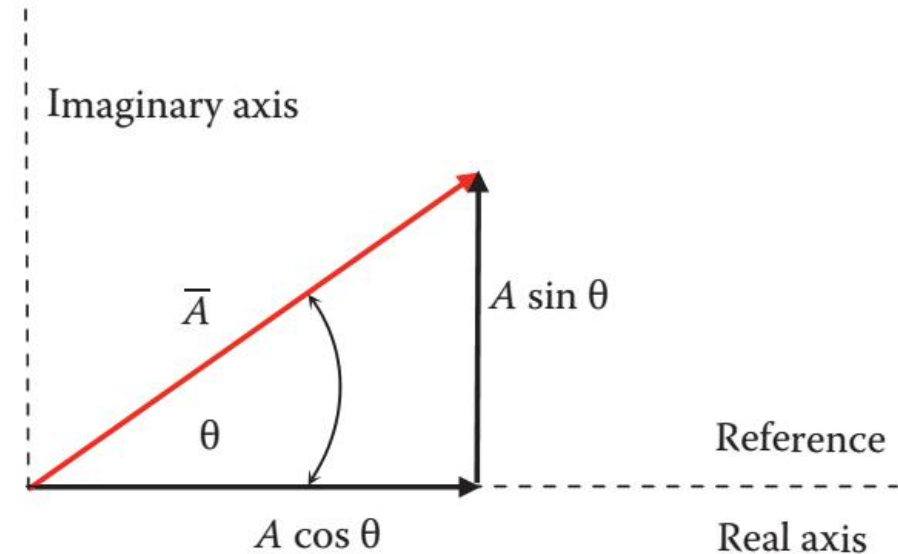
$$\bar{A}^* = X - jY = A\angle-\theta^\circ$$



# Impedances

- Basic impedances

- Resistance

$$R = \frac{\bar{V}}{\bar{I}_R} = \frac{V \angle 0}{I_R \angle 0} = R \angle 0$$

- Inductance

$$\bar{X}_L = \frac{\bar{V}}{\bar{I}_L} = \frac{V \angle 0}{I_L \angle -90^\circ} = X_L \angle 90^\circ$$

- Capacitance


$$\bar{X}_C = \frac{\bar{V}}{\bar{I}_C} = \frac{V \angle 0}{I_C \angle 90^\circ} = X_C \angle -90^\circ$$

- Complex

- Series and parallel connections of basic impedances
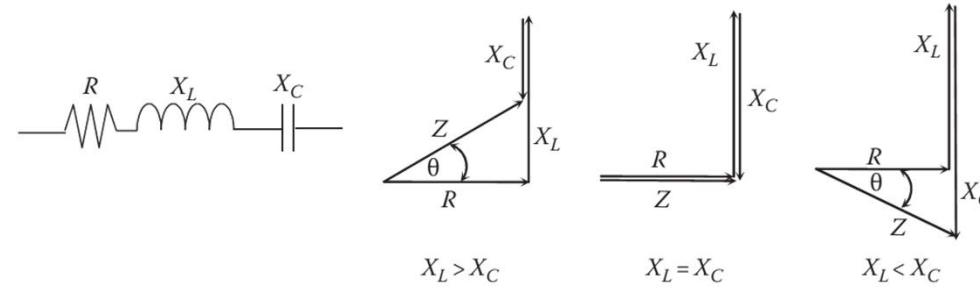
# Admittance


- Series connected impedances are additive



$$\bar{Y} = \frac{1}{\bar{Z}}$$

What is the unit of admittance

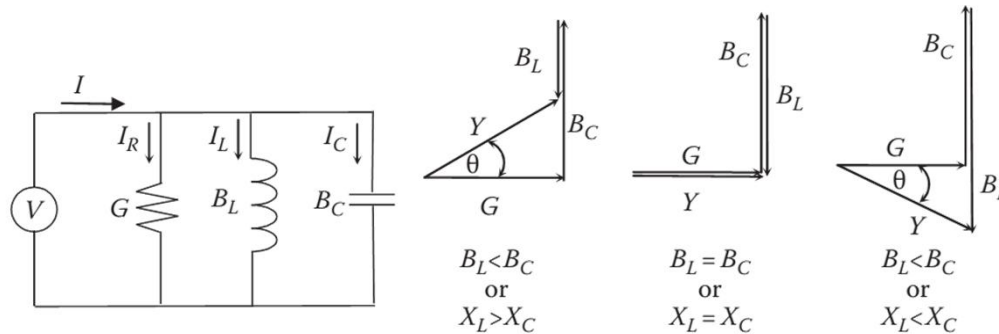- Parallel connected impedances are not additive
- Parallel connected admittances are additive



$$\bar{G} = \frac{1}{R} = \frac{1}{R} \angle 0^\circ$$

$$\bar{B}_L = \frac{1}{X_L} = \frac{1}{X_L} \angle -90^\circ$$


$$\bar{B}_C = \frac{1}{X_C} = \frac{1}{X_C} \angle 90^\circ$$

# Electric power





- Instantaneous power
- For a complex load

$$p = vi$$
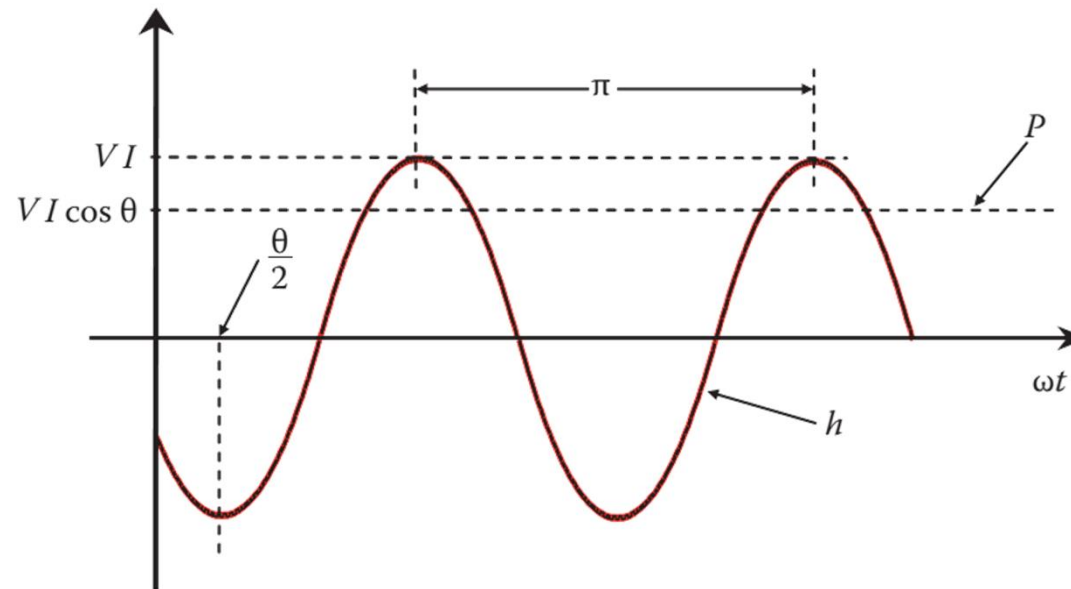
$$\begin{aligned} p &= [V_{\max} \sin(\omega t)][I_{\max} \sin(\omega t - \theta)] \\ &= VI [\cos(\theta) - \cos(2\omega t - \theta)] \end{aligned}$$



# Instantaneous power

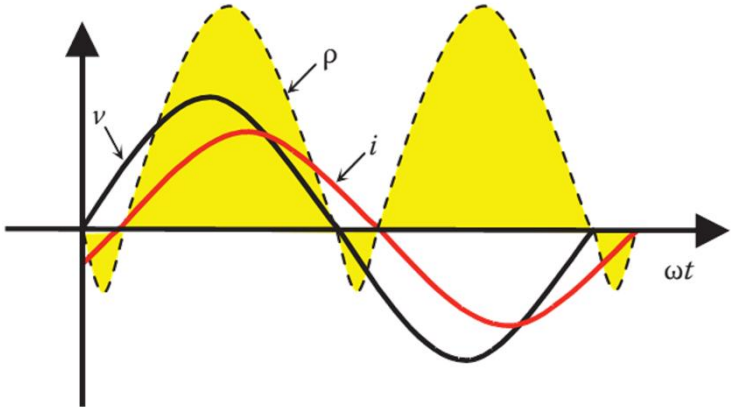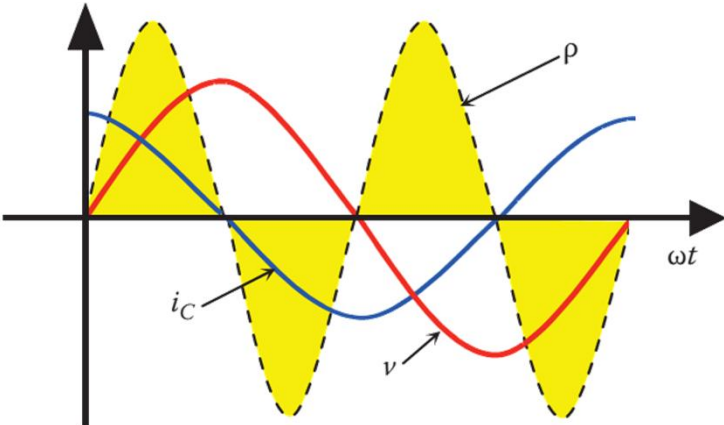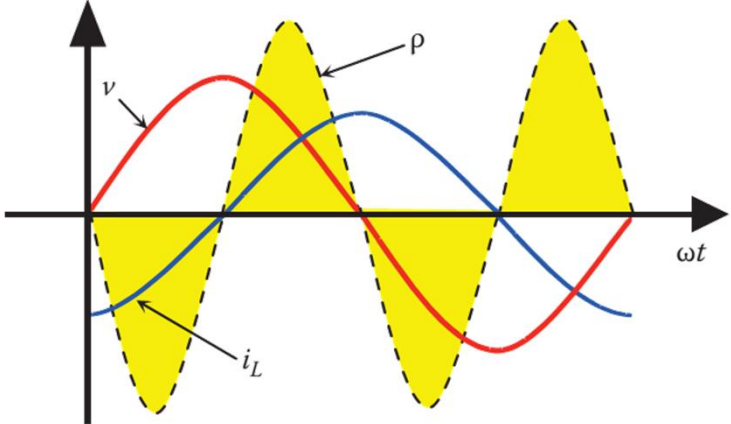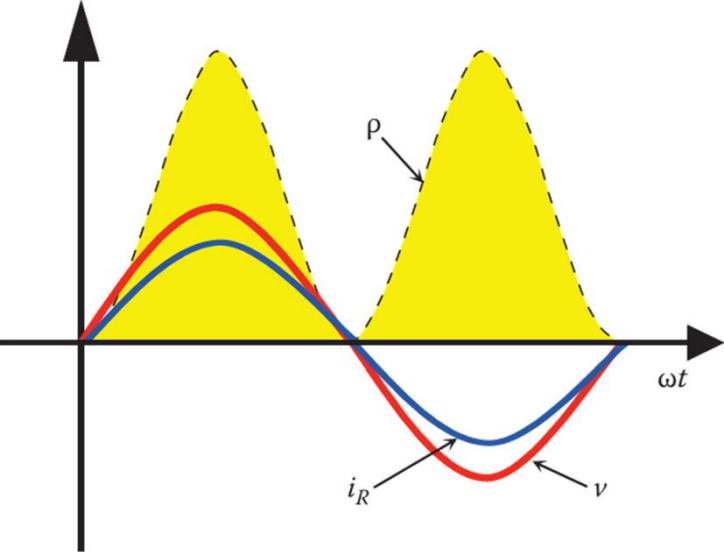


# Electric energy

- Energy is the time integral of the power


– Constant power

$$E = pT$$

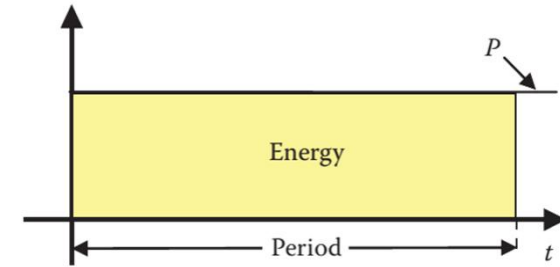


– Discrete power

$$E = \sum_i p_i T_i$$

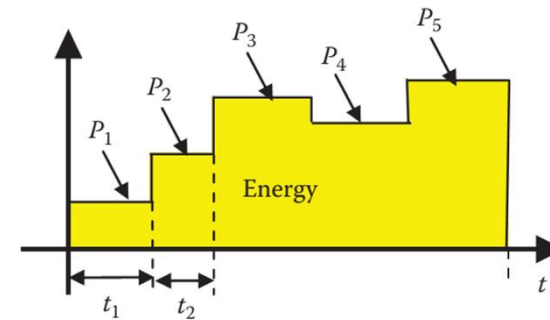

– Variable power

$$E = \int_0^T p dt$$

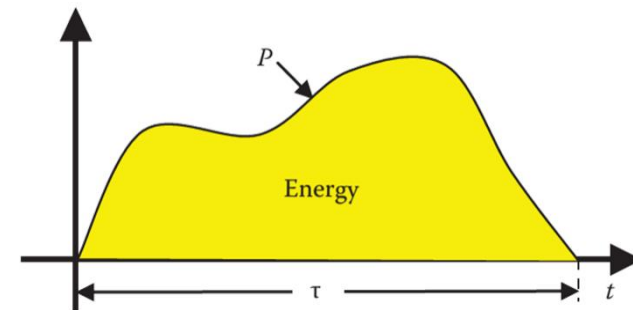



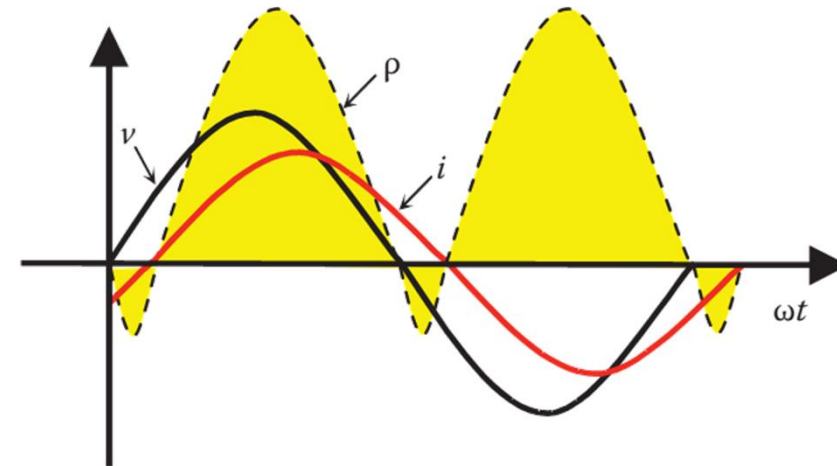
# Active, Reactive and Complex Power

- The power that produces energy is the average of  $p = vi$

$$P = \frac{1}{2\pi} \int_0^{2\pi} p d(\omega t) \\ = VI \cos(\theta)$$





- This is called Active or Real power
- The Complex or Apparent power is defined as

$$S \equiv \bar{V} \bar{I}^*$$

Why not?  
 $S \equiv \bar{V} \bar{I}$   
It is a 100-years old  
convention
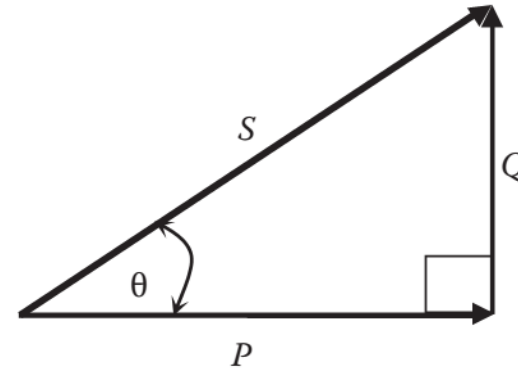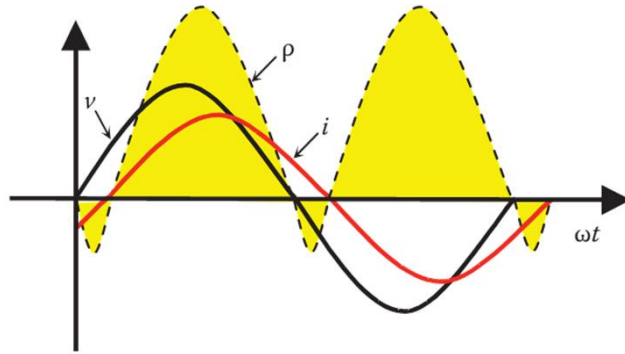
# Active, Reactive and Complex Power

- Part of the instantaneous power does not produce energy, it is called Reactive or Imaginary power  $Q \equiv VI \sin(\theta)$



$$S = \bar{V} \bar{I}^* = VI \cos(\theta) + jVI \sin(\theta)$$


- In case of sinusoidal quantities the reactive power is well defined but not obvious in case of distorted quantities !

# Power factor

- The power factor is defined as the ratio of real to apparent power


$$pf = \frac{P}{S} = \cos(\theta)$$

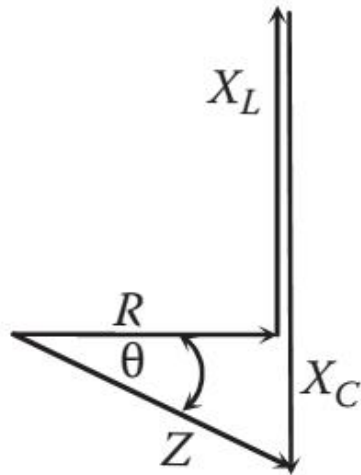- In an electric circuit it can be calculated as




$$pf = \frac{R}{Z} = \frac{R}{\sqrt{X^2 + R^2}}$$
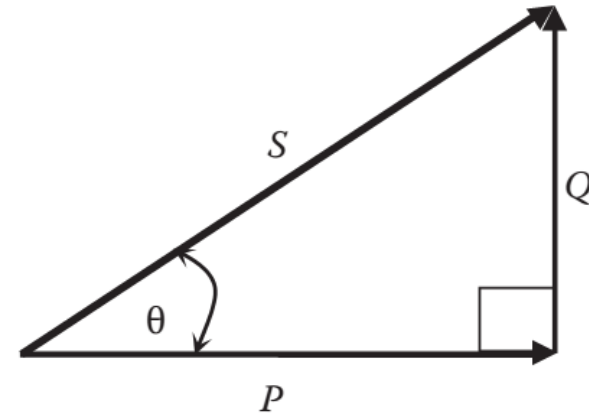
$$pf = \frac{P}{S} = \frac{P}{\sqrt{P^2 + Q^2}}$$


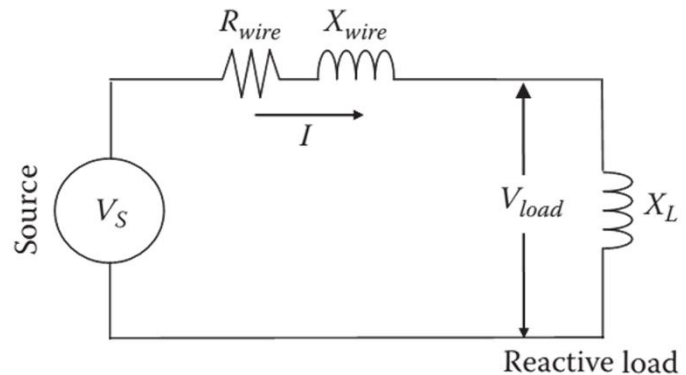
# Problems with power factor

- Increases losses in the transmission line
- Reduces the sparse capacity of transmission line
- Reduces the voltage across the load
- Need for power factor correction



$$\bar{I} = \frac{\bar{V}_s}{R_{wire} + j(X_{wire} + X_{load})}$$

$$P_{loss} = I^2 R_{wire}$$

$$V_{load} = \frac{V_s}{\sqrt{\left(\frac{R_{wire}}{X_L}\right)^2 + \left(1 + \frac{X_{wire}}{X_L}\right)^2}}$$

# Summary of the lecture

- Sinusoidal voltage and current represented by phasors
- Phasor has amplitude and phase → complex number
- The nature of load (resistive, reactive) produces phase shift between voltage and current → power factor
- Real power produces work, reactive power is a parasitic effect that increases the line losses
- Real mean square useful measure of AC-quantities even under distortion.