


Ch 8. Three-phase systems

- Lecture outcomes (what you are supposed to learn):
 - Generation of three-phase voltages
 - Connection of three-phase circuits
 - Wye-Delta transformation
 - Power of three-phase connected loads

Introduction

- High power equipments are built as three-phase systems.
- Three-phase systems can produce rotating field without special control.
- Three phase generator produce more power than single phase one with the same volume.
- Three-phase systems are more reliable. They can deliver power even if one phase fails.



Schematic structure of Power systems

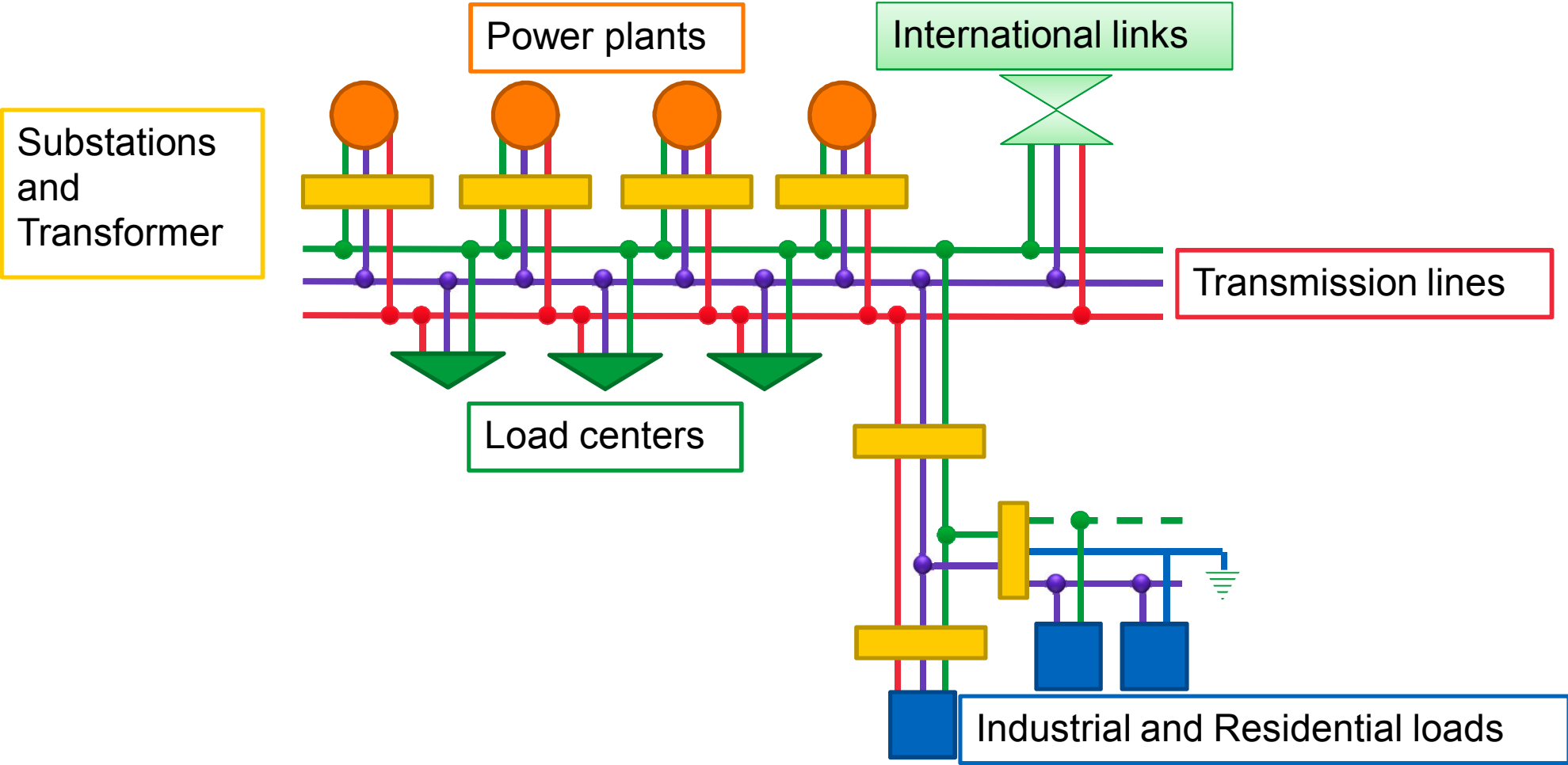

Generation of three-phase voltages (kolmivaihejärjestelmä)


- Simple three-phase generator

$$e = nBl\omega$$

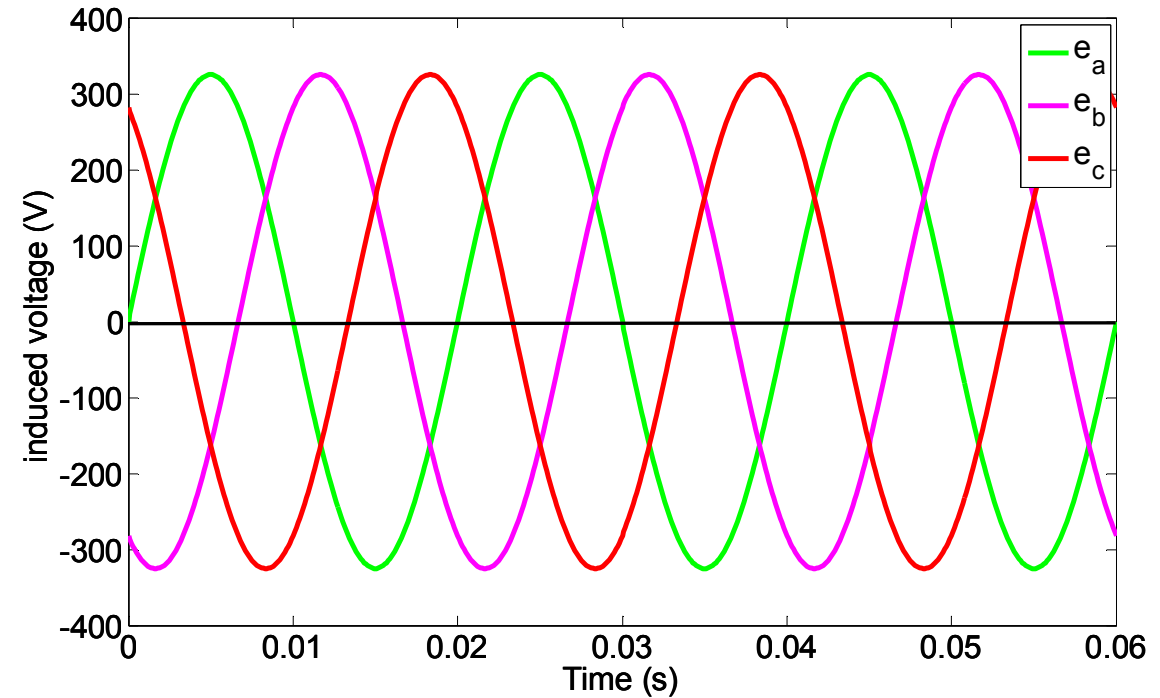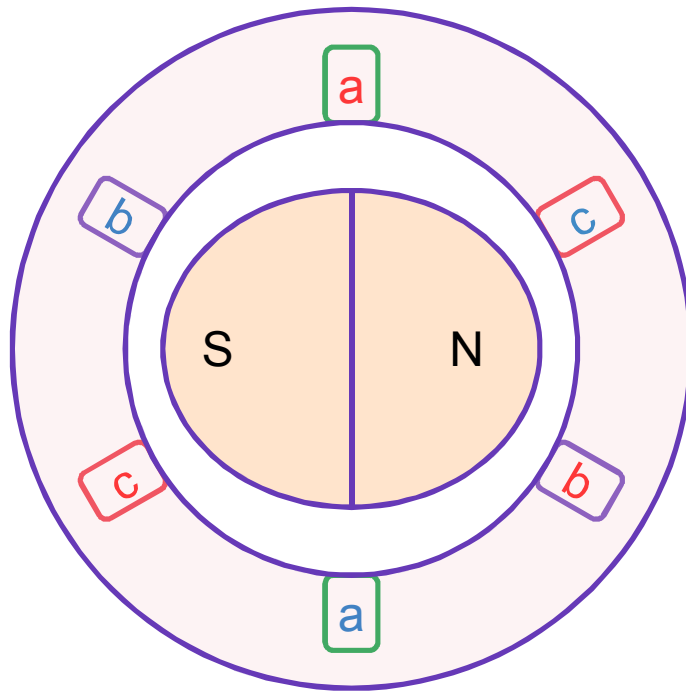

Generation of three-phase voltages

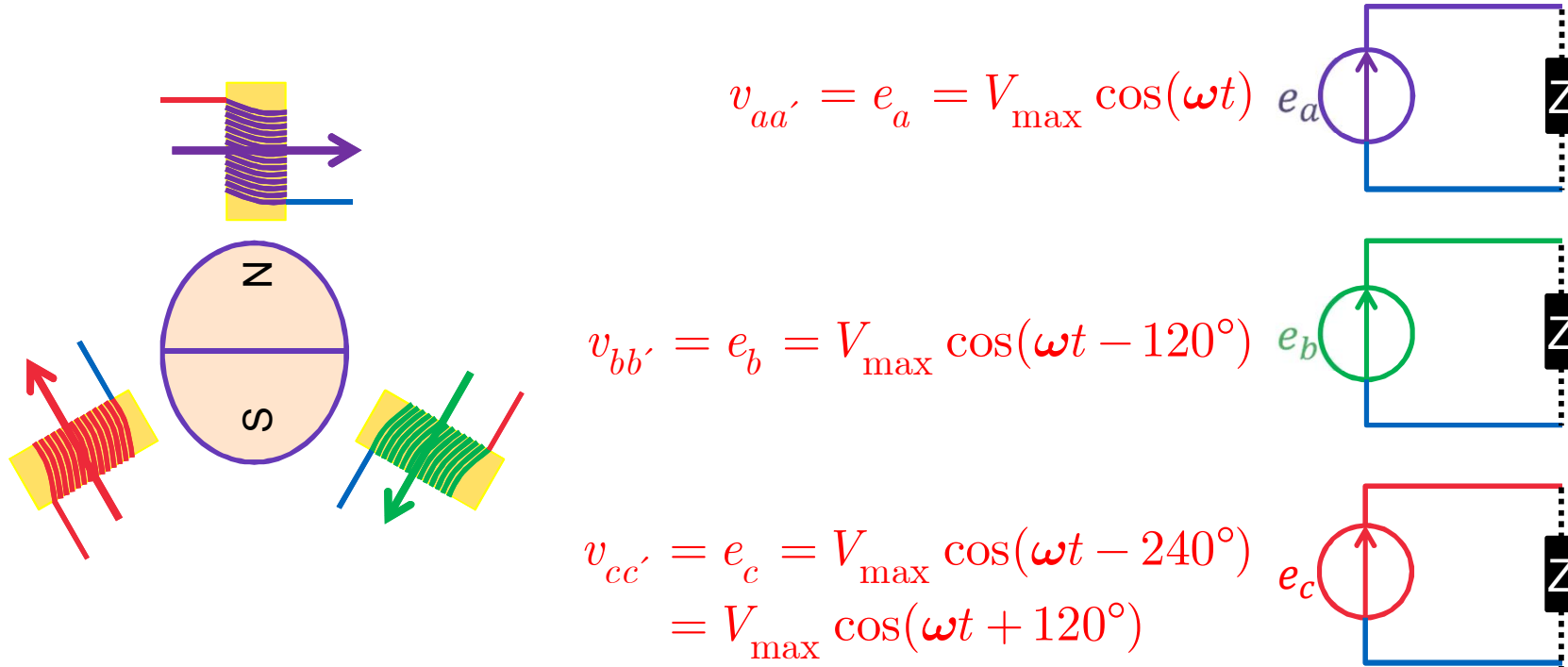- 3 single-phase circuits at different phase angle!




Generation of three-phase voltages

- The voltage of each phase are called phase voltages
- The phase voltages are written in complex form

$$\bar{V}_{aa'} = \frac{V_{\max}}{\sqrt{2}} \angle 0^\circ = V \angle 0^\circ$$

$$\bar{V}_{bb'} = \frac{V_{\max}}{\sqrt{2}} \angle -120^\circ = V \angle -120^\circ$$

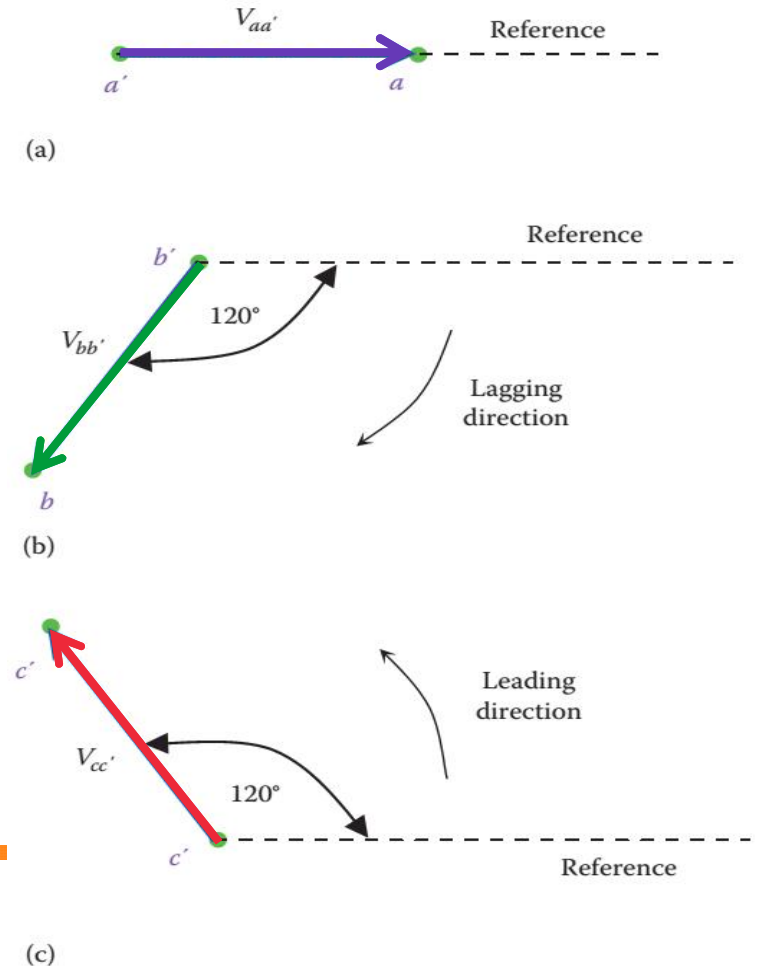
$$\bar{V}_{cc'} = \frac{V_{\max}}{\sqrt{2}} \angle 120^\circ = V \angle 120^\circ$$







Anouar Belahcen

Connecting the 3-phase voltages

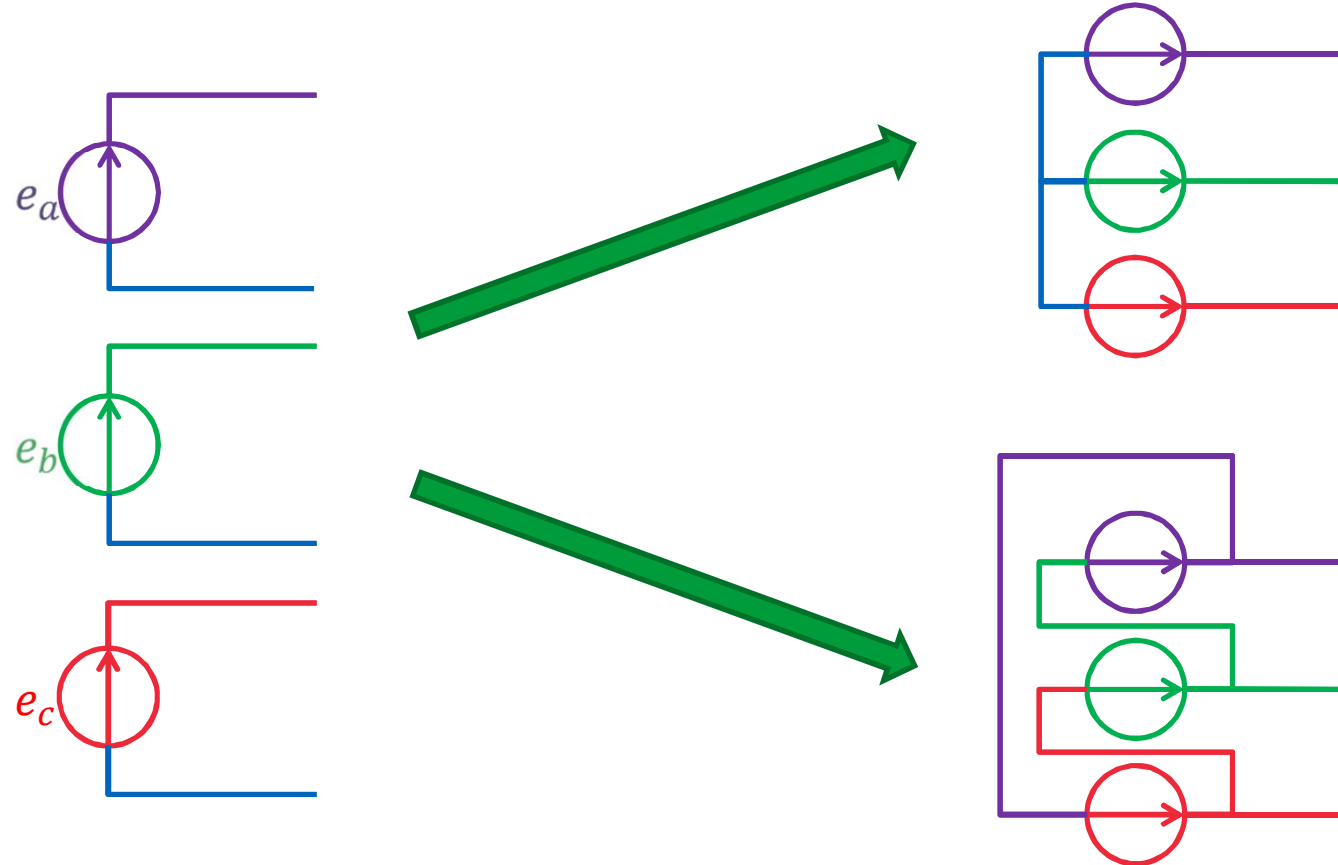- The potential difference is known but not the potentials !



Connecting the 3-phase voltages

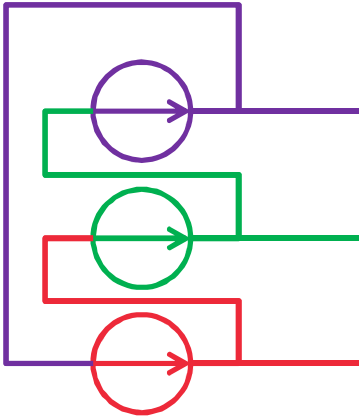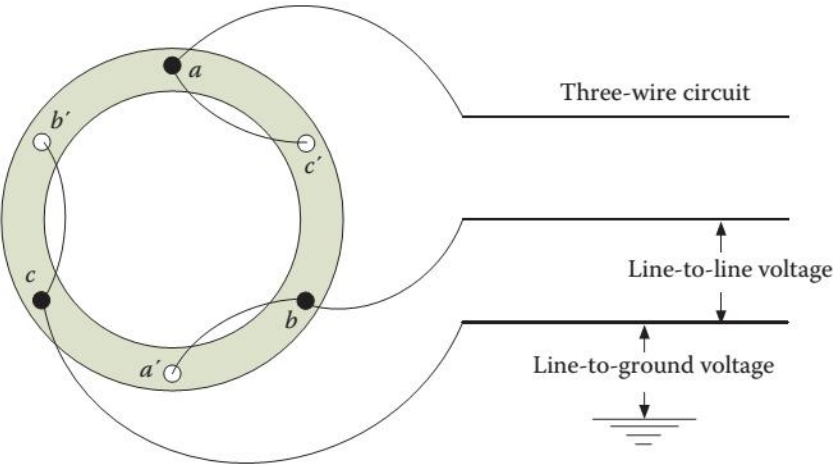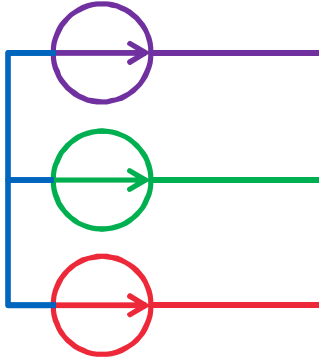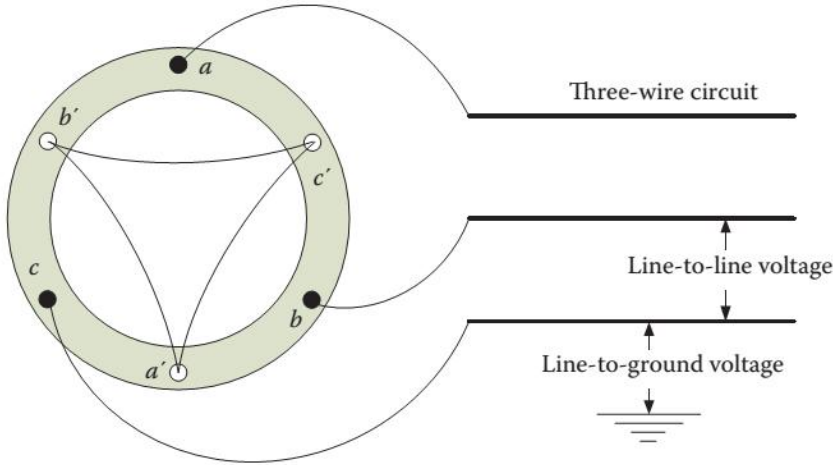


Anouar Belahcen

Line-to-line voltage
=
Pääjännitte




Connecting the source and load

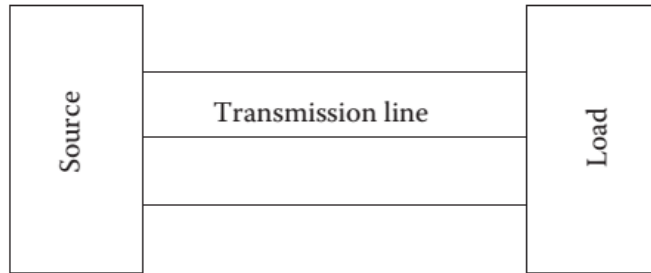- Only 3 wires are needed to connect the source and load



Wye connection (Y- tai tähtikytkentä)

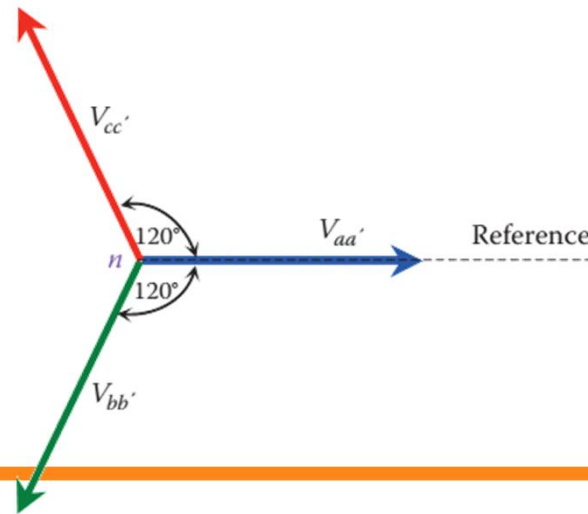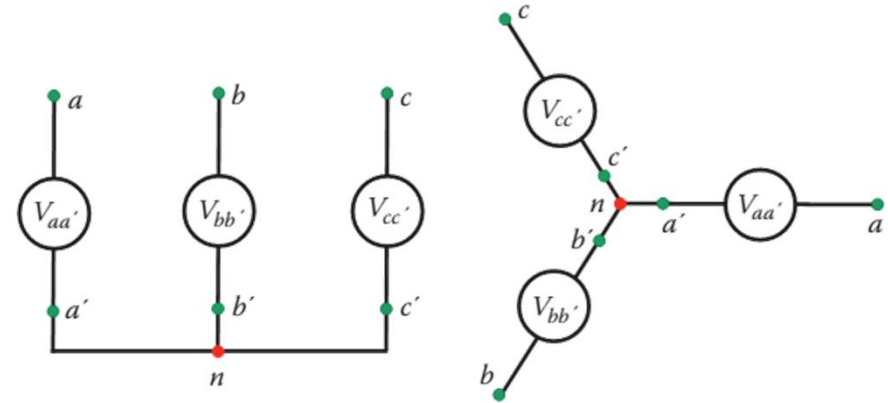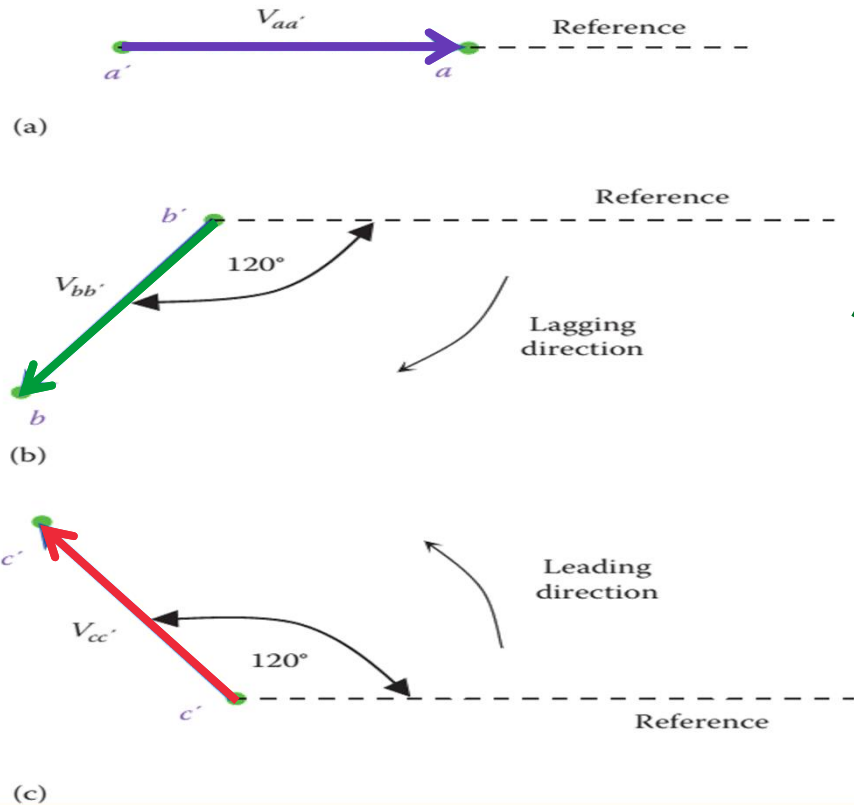- Three similar terminal of each coil connected to the same point called neutral or N




Anouar Belahcen

Wye connection (Y- tai tähtikytkentä)

- For balanced symmetrical three phase system:


$$V_{an} = V_{bn} = V_{cn} = V_{ph}$$

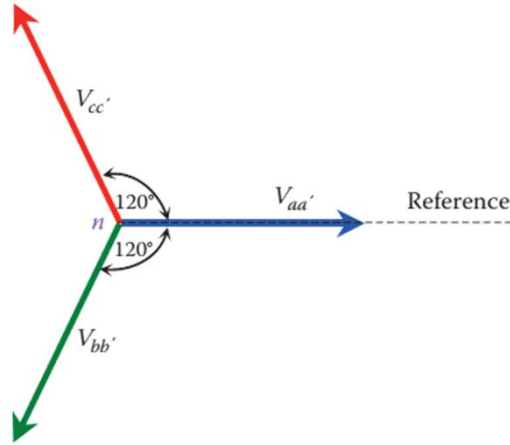

$$\bar{V}_{an} = V_{ph} \angle 0^\circ$$

$$\bar{V}_{bn} = V_{ph} \angle -120^\circ$$
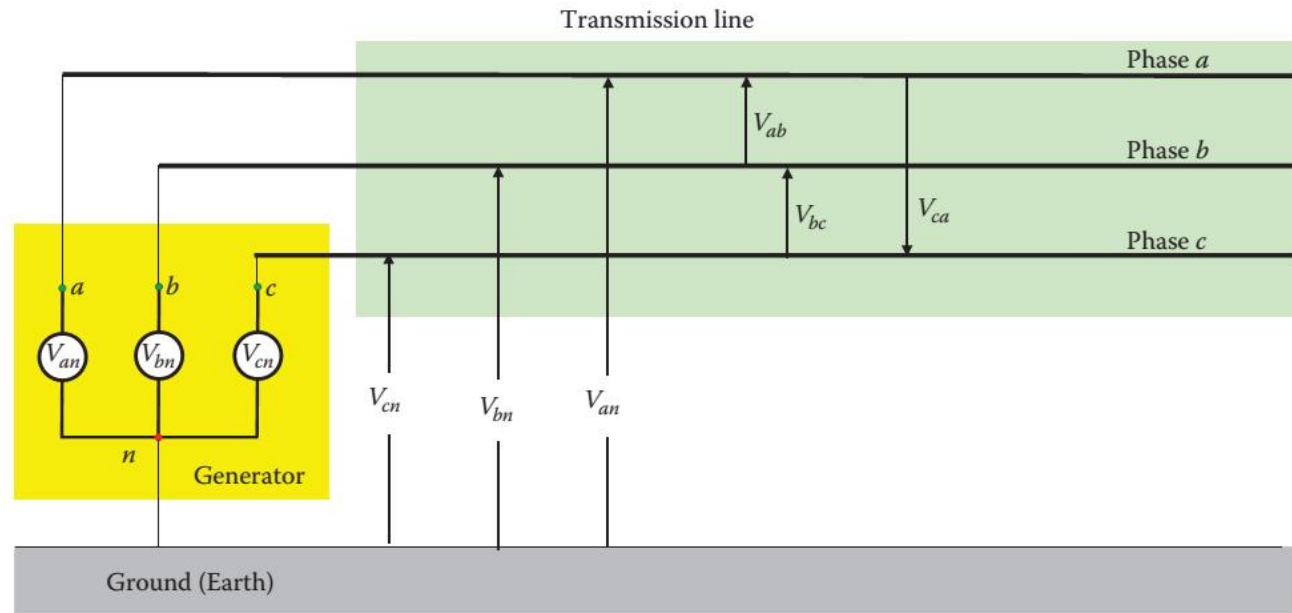
$$\bar{V}_{cn} = V_{ph} \angle 120^\circ$$



Line-to-line voltages in Wye connection

$$\bar{V}_{an} = V_{ph} \angle 0^\circ$$


$$\bar{V}_{bn} = V_{ph} \angle -120^\circ$$

$$\bar{V}_{cn} = V_{ph} \angle 120^\circ$$

$$\bar{V}_{ab} = \bar{V}_{an} - \bar{V}_{bn}$$

$$\begin{aligned}\bar{V}_{ab} &= V_{ph} \angle 0^\circ - V_{ph} \angle -120^\circ \\ &= \sqrt{3} V_{ph} \angle 30^\circ\end{aligned}$$

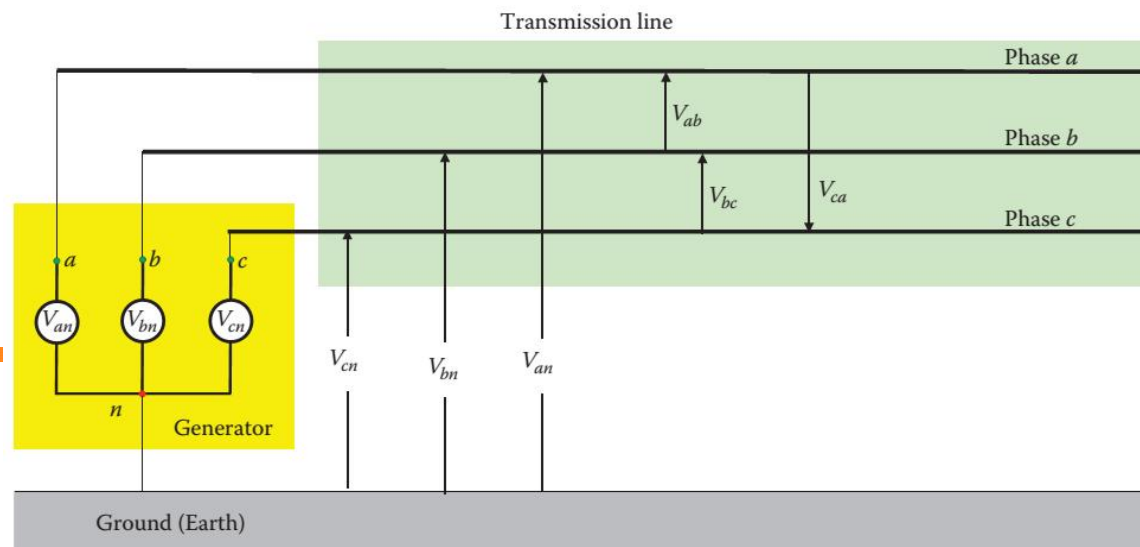
- Magnitude of line-to-line voltage \bar{V}_{ab} is larger than the magnitude of phase voltages \bar{V}_{an} by a factor of $\sqrt{3}$
- Line-to-line voltage \bar{V}_{ab} leads \bar{V}_{an} by 30°



Line-to-line voltages in Wye connection

$$\begin{aligned}\bar{V}_{bc} &= \bar{V}_{bn} - \bar{V}_{cn} \\ \bar{V}_{bc} &= V_{ph} \angle -120^\circ - V_{ph} \angle 120^\circ \\ &= \sqrt{3}V_{ph} \angle -90^\circ\end{aligned}$$

$$V_{ll} = \sqrt{3}V_{ph}$$

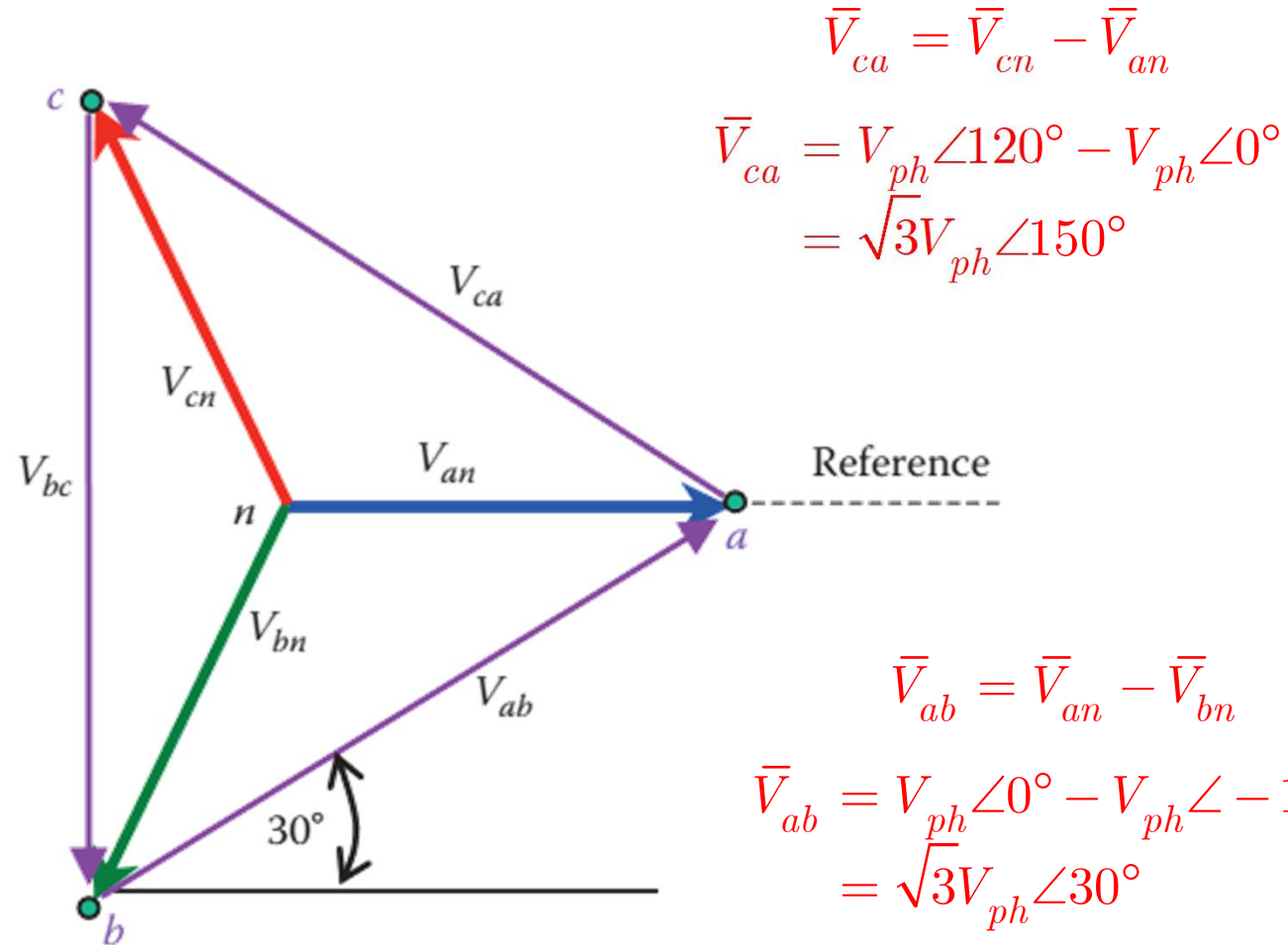

$$\bar{V}_{ca} = \bar{V}_{cn} - \bar{V}_{an}$$


$$\begin{aligned}\bar{V}_{ca} &= V_{ph} \angle 120^\circ - V_{ph} \angle 0^\circ \\ &= \sqrt{3}V_{ph} \angle 150^\circ\end{aligned}$$

$$\bar{V}_{ab} = \bar{V}_{an} - \bar{V}_{bn}$$

$$\begin{aligned}\bar{V}_{ab} &= V_{ph} \angle 0^\circ - V_{ph} \angle -120^\circ \\ &= \sqrt{3}V_{ph} \angle 30^\circ\end{aligned}$$

Delta connection (kolmiokytentä)

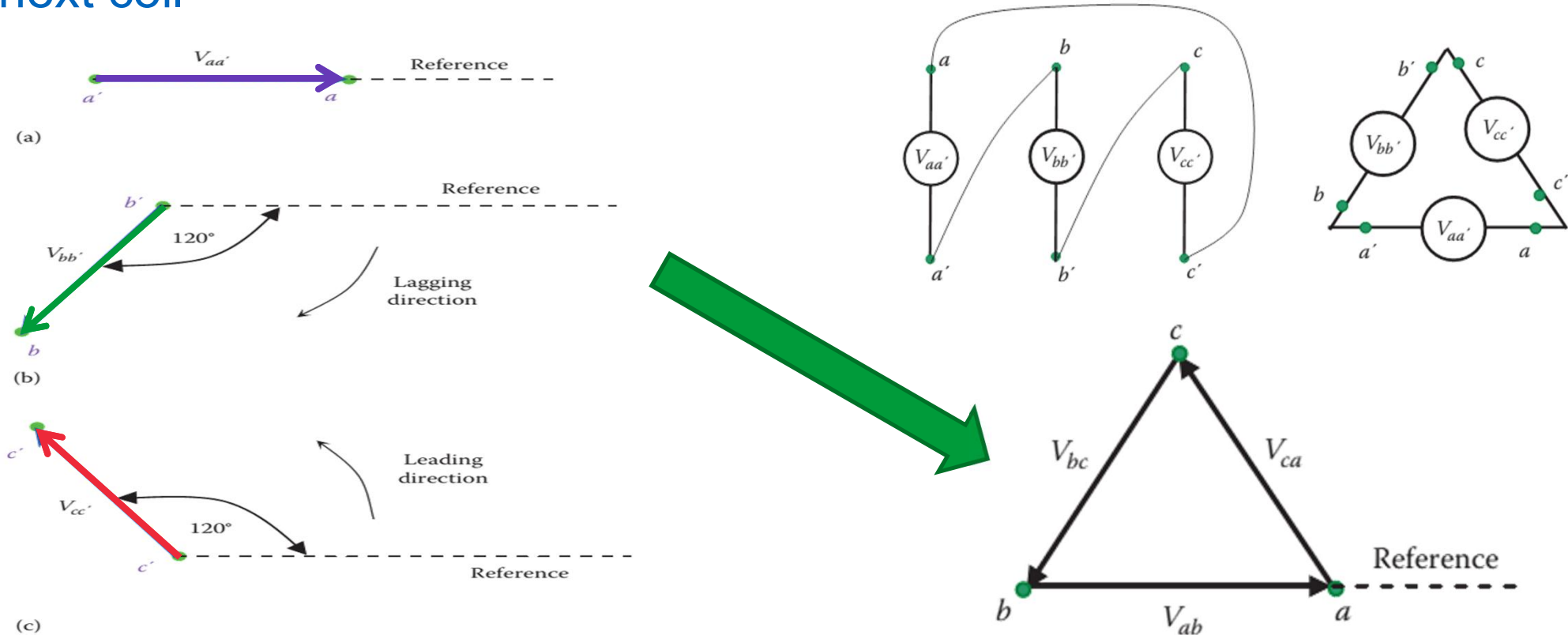- The entrance terminal of one coil is connected to the end terminal of the next coil




Delta connection

- Absence of a neutral point i.e. floating potentials
- Phase voltages are identical with line-to-line voltages

$$\bar{V}_{aa'} = \bar{V}_{ab}$$

$$\bar{V}_{bb'} = \bar{V}_{bc}$$

$$\bar{V}_{cc'} = \bar{V}_{ca}$$

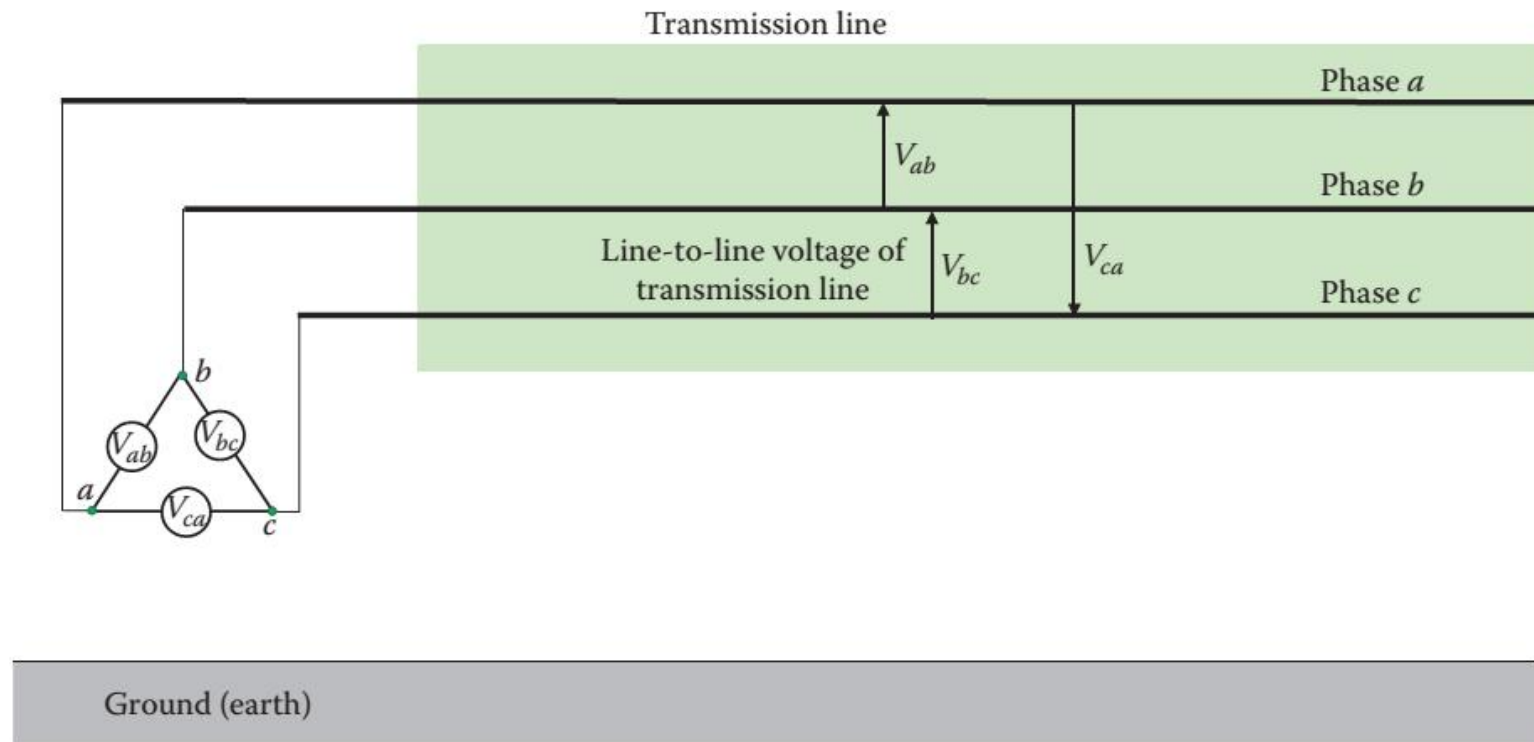

Single and three phases loads


- Residential loads are usually single phase loads (230 V)
- Industrial and commercial loads are mostly three phases loads (400 V)
- Clustered residential areas are powered by three phases
- Single houses might be powered by single phase
- Neutral point is grounded to ensure that all loads are powered regardless of fluctuations in current

Wye connected load

- Load impedances connected to a common neutral point from one terminal

$$\bar{Z}_{an} = \bar{Z}_{bn} = \bar{Z}_{cn} = \bar{Z}$$

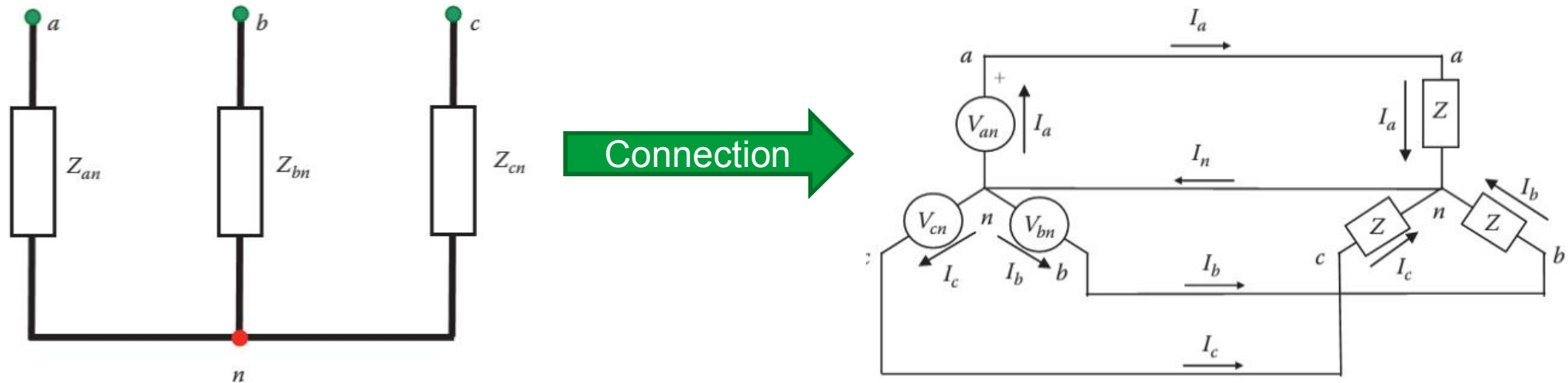- The load is powered by a three phases source




Wye connected load

- Phase currents

$$\bar{I}_a = \frac{\bar{V}_{an}}{\bar{Z}} = \frac{V_{ph} \angle \theta}{Z \angle \varphi} = \frac{V_{ph}}{Z} \angle (\theta - \varphi)$$

$$\bar{I}_b = \frac{\bar{V}_{bn}}{\bar{Z}} = \frac{V_{ph} \angle (\theta - 120)}{Z \angle \varphi} = \frac{V_{ph}}{Z} \angle (\theta - \varphi - 120)$$
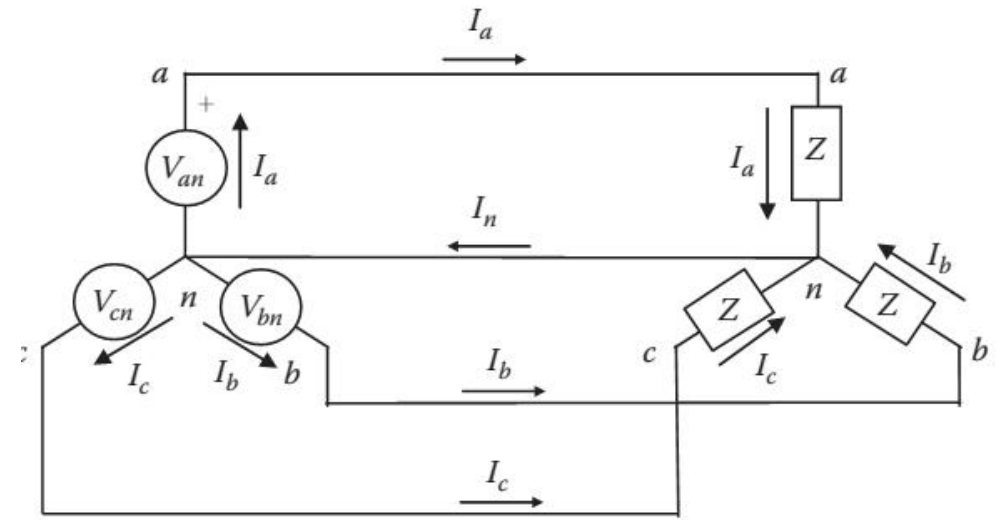
$$\bar{I}_c = \frac{\bar{V}_{cn}}{\bar{Z}} = \frac{V_{ph} \angle (\theta + 120)}{Z \angle \varphi} = \frac{V_{ph}}{Z} \angle (\theta - \varphi + 120)$$



- Equal magnitudes, 120 phase shifts




Wye connected load

- Neutral current

$$\bar{I}_n = \bar{I}_a + \bar{I}_b + \bar{I}_c$$

$$\bar{I}_n = \bar{I}_a + \bar{I}_a \angle -120 + \bar{I}_a \angle 120 = 0$$

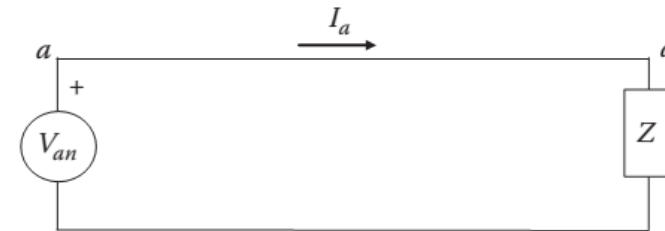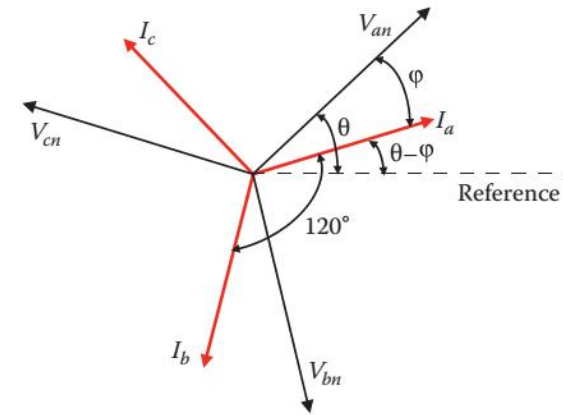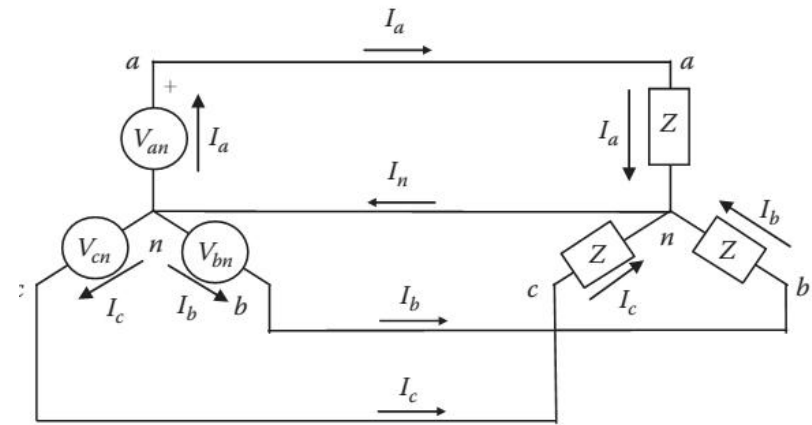- If source and loads are balanced the neutral current is zero
- In transmission this means no need for a neutral line




Delta-connected load

- Loads connected between two transmission lines
- Voltage across the single load is the line-to-line voltage

$$\bar{I}_{ab} = \bar{I}_a + \bar{I}_{ca}$$

$$\bar{I}_{bc} = \bar{I}_b + \bar{I}_{ab}$$
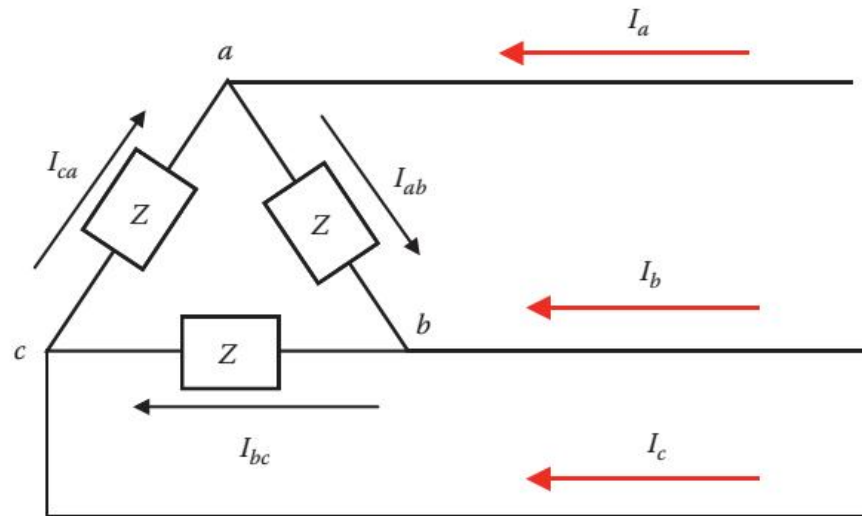
$$\bar{I}_{ca} = \bar{I}_c + \bar{I}_{bc}$$



$$\bar{I}_{ab} = \frac{\bar{V}_{ab}}{\bar{Z}}$$

$$\bar{I}_{bc} = \frac{\bar{V}_{bc}}{\bar{Z}}$$

$$\bar{I}_{ca} = \frac{\bar{V}_{ca}}{\bar{Z}}$$

- Balanced load and source  balanced currents

Delta-connected load

- If we choose \bar{I}_{ab} as reference

$$\bar{I}_{ab} = I \angle 0^\circ$$


$$\bar{I}_{bc} = I \angle -120^\circ$$

$$\bar{I}_{ca} = I \angle 120^\circ$$

$$\bar{I}_a = \sqrt{3}I \angle -30^\circ = \sqrt{3}\bar{I}_{ab} \angle -30^\circ$$



$$\bar{I}_b = \sqrt{3}I \angle -150^\circ = \sqrt{3}\bar{I}_{bc} \angle -30^\circ$$
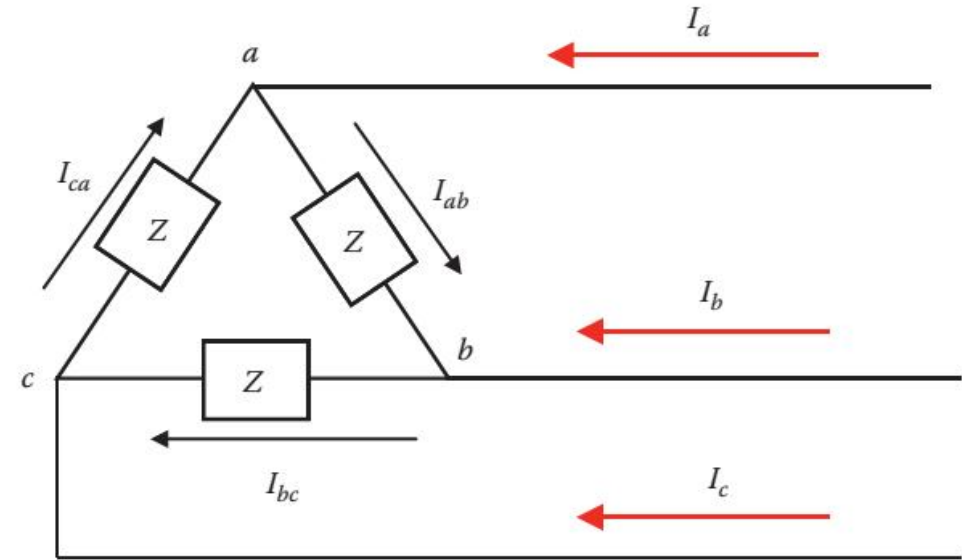
$$\bar{I}_c = I \angle 90^\circ = \sqrt{3}\bar{I}_{ca} \angle -30^\circ$$



Circuits with mixed connections


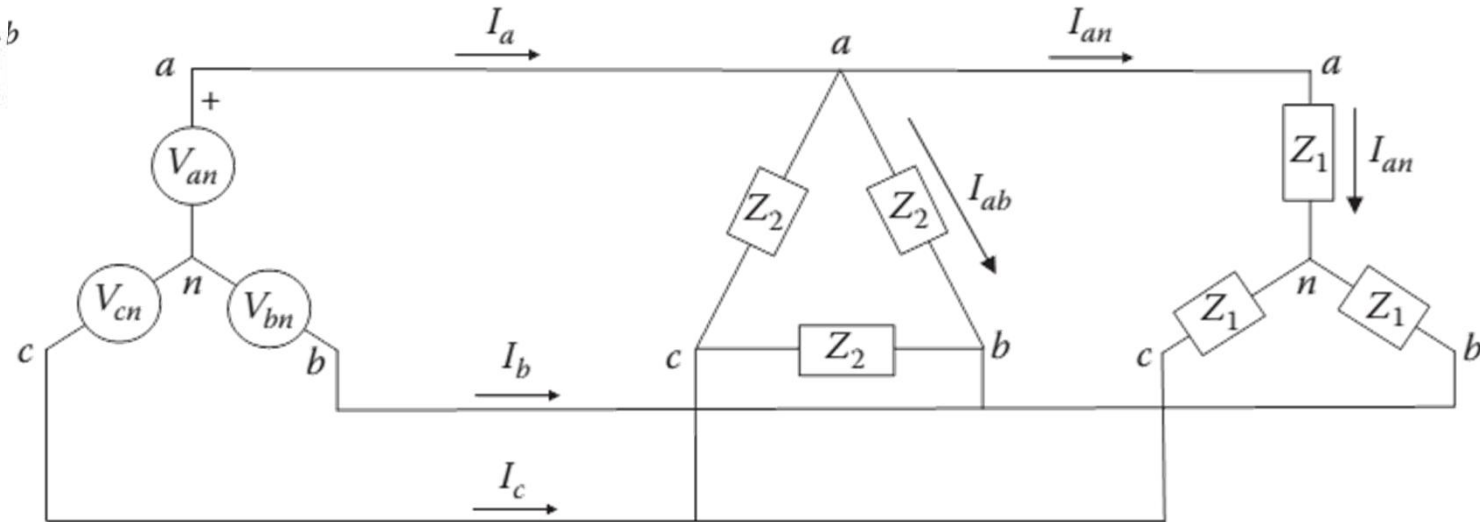
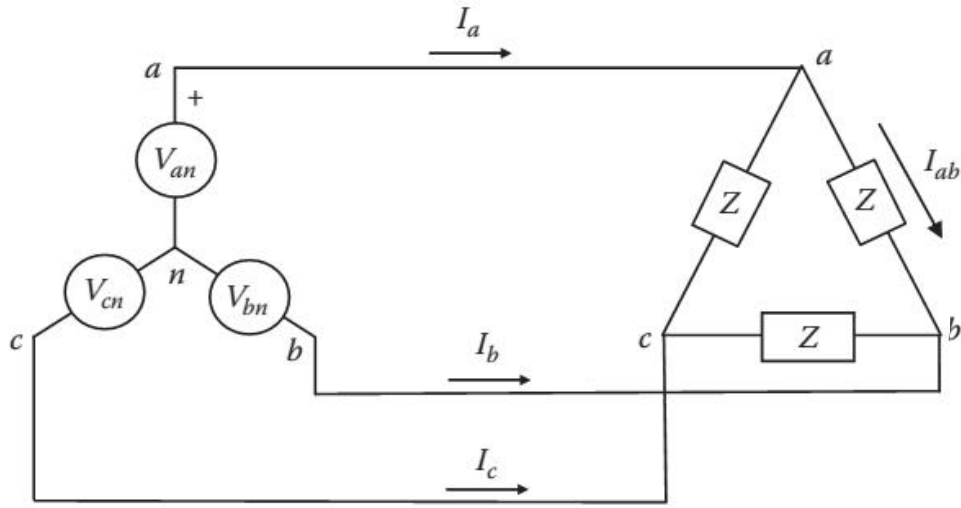
- In general circuits can be so that the source or the load or both are connected in Y-, Delta-, or any combination



Circuits with mixed connections


- Such circuits requires the load and source to be in the same connection

➔ Y-Delta transformation

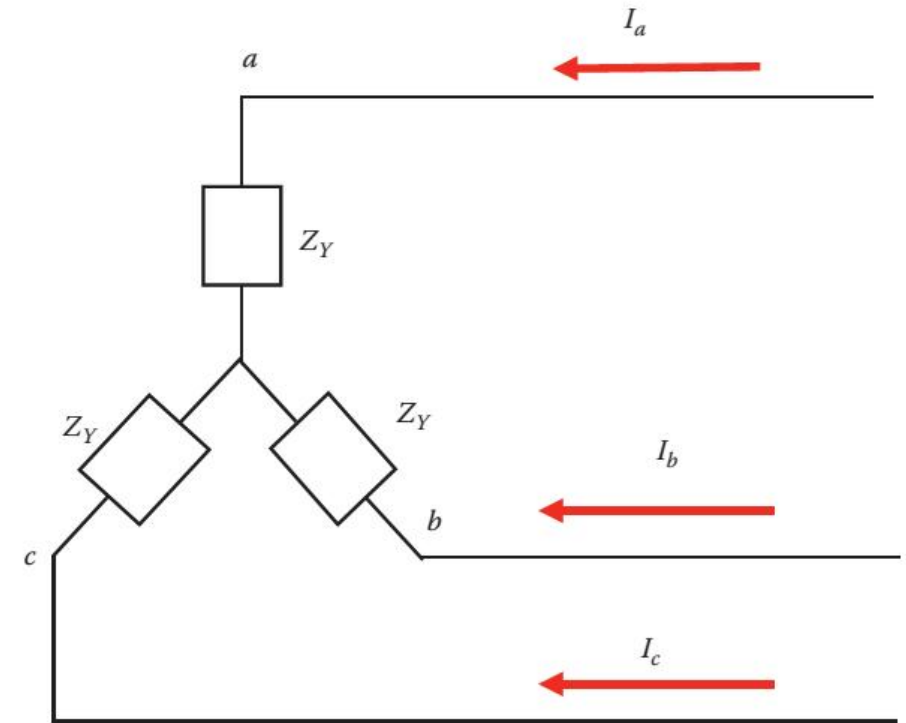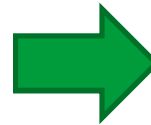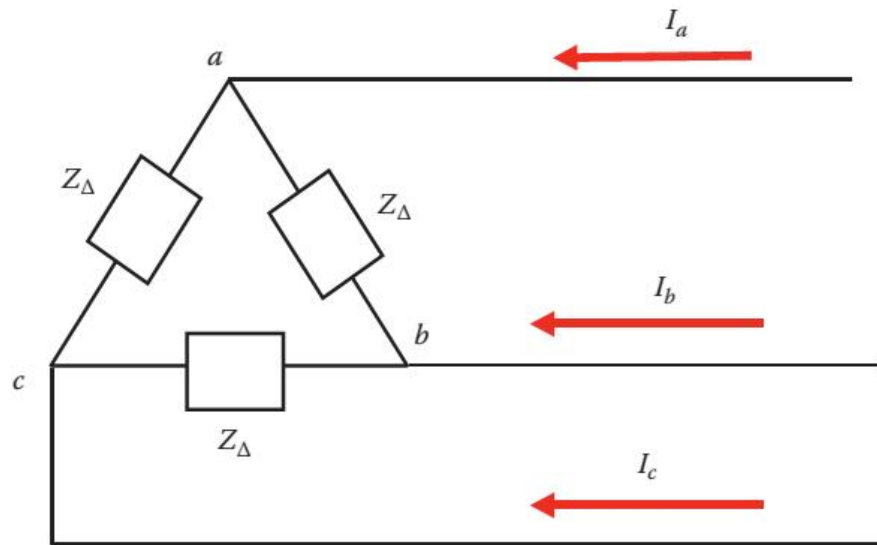


Y-Delta transformation

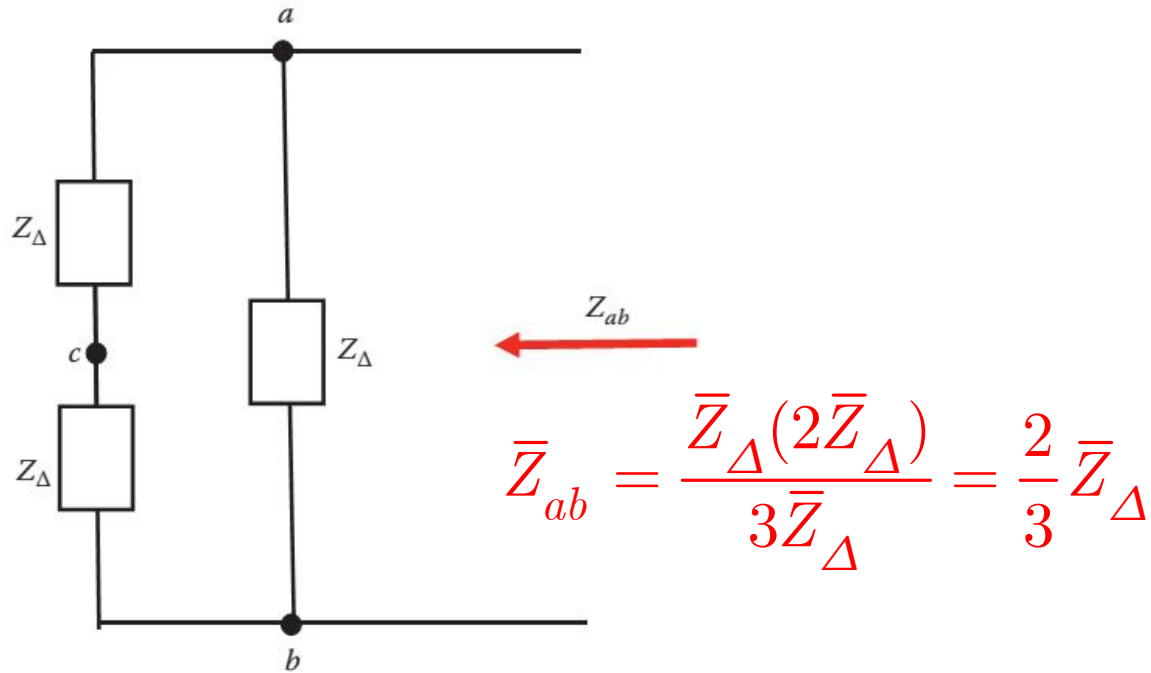- Consider the impedance seen by the source terminals



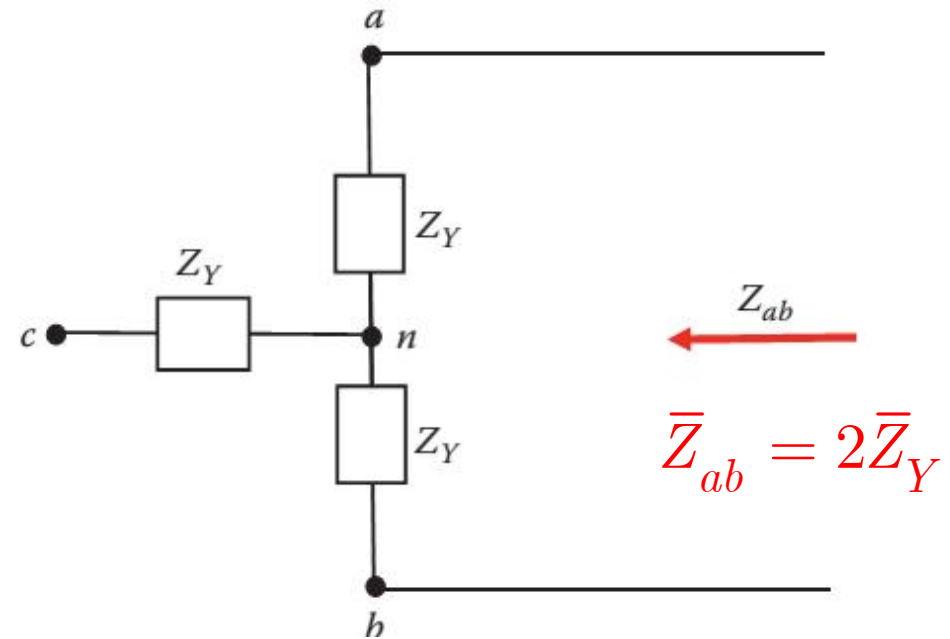- Transformation valid in both directions



$$\bar{Z}_Y = \frac{\bar{Z}_{\Delta}}{3}$$

Power of three phases system

- The power of a three phase load is the sum of the powers of each load (each phase)
- Phases related quantities are called phase quantities (phase current, phase voltage, phase power)

$$P_{ph} = V_{ph} I_{ph} \cos(\theta)$$

$$Q_{ph} = V_{ph} I_{ph} \sin(\theta)$$

$$P = 3P_{ph} = 3V_{ph} I_{ph} \cos(\theta)$$

$$Q = 3Q_{ph} = 3V_{ph} I_{ph} \sin(\theta)$$

Power of Y-connected three phases load

- Phase current equal to line current
- Phase voltage different

$$P = 3P_{ph} = 3V_{ph}I_{ph} \cos(\theta)$$


$$= \sqrt{3}V_{ll}I_l \cos(\theta)$$

$$Q = 3Q_{ph} = 3V_{ph}I_{ph} \sin(\theta)$$

$$= \sqrt{3}V_{ll}I_l \sin(\theta)$$

$$I_{ph} = I_l$$

$$V_{ph} = \frac{V_{ll}}{\sqrt{3}}$$

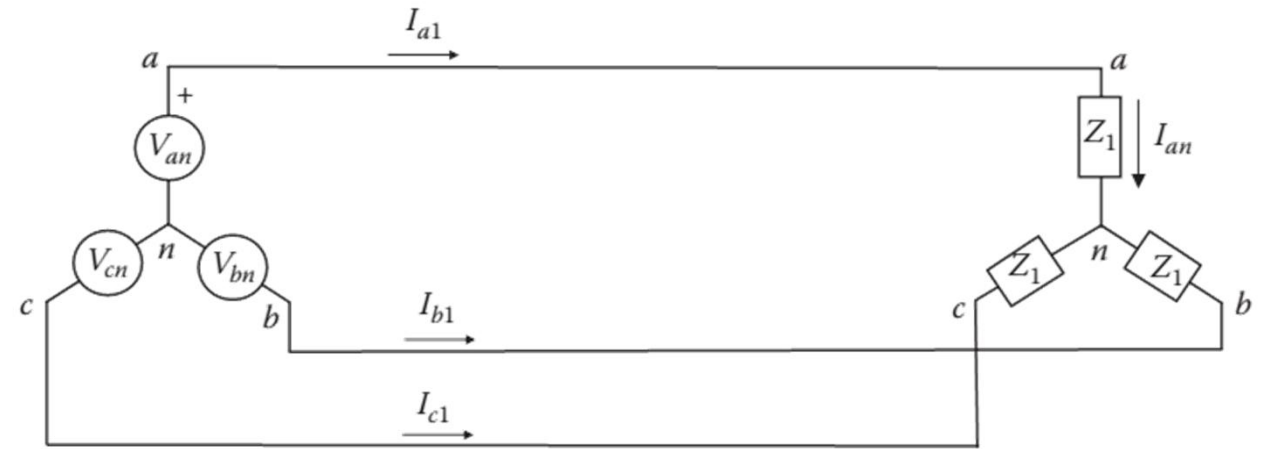

Power of Delta-connected load

- Phase voltage equal to line-to-line voltage
- Phase current different

$$P = 3P_{ph} = 3V_{ph}I_{ph} \cos(\theta)$$


$$= \sqrt{3}V_{ll}I_l \cos(\theta)$$

$$Q = 3Q_{ph} = 3V_{ph}I_{ph} \sin(\theta)$$

$$= \sqrt{3}V_{ll}I_l \sin(\theta)$$

$$V_{ph} = V_{ll}$$

$$I_{ph} = \frac{I_l}{\sqrt{3}}$$

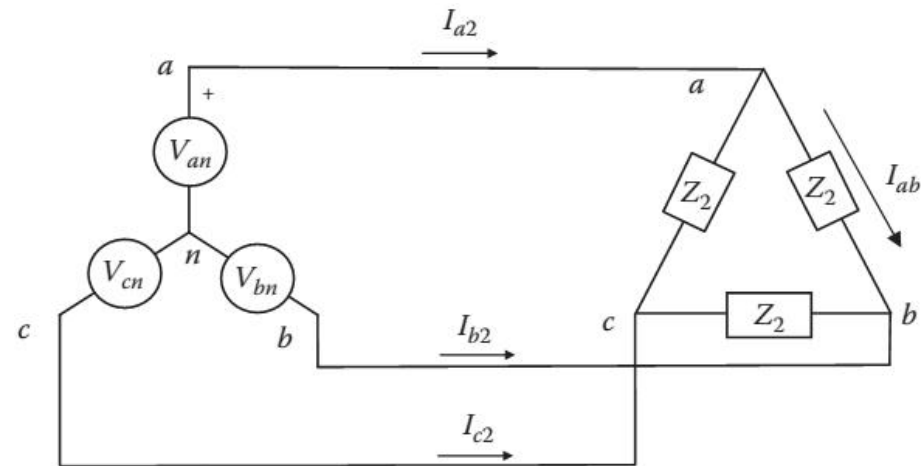

Summary of the lecture

- Three different coils shifted by 120 deg in space generate balanced three voltages
- The coils can be connected in Y or Delta
- Loads also can be connected in Y or Delta
- Basic equations for single phase system holds also for three phases system (remember the phase shifts)
- In y-connection, line current equals phase current
- In Delta-connection line-to-line voltage equals phase voltage
- Remember to divide by $\sqrt{3}$ for the other quantities.