

# Transformers


- Lecture outcomes (what you are supposed to learn):
  - Describe the construction of transformers
  - Explain the operation principle of the transformer
  - How to connect the windings of three phase transformer
  - Derive the equivalent circuit of the transformer
  - Analyze the transformer operation with the equivalent circuit

# Introduction

- Transformers are used to step up or step down the voltage in a circuit
- Large transformers are used in electrical energy transmission and distribution (three phase)
- Smaller transformers are used in electronic circuits and they are coupled to rectifiers for DC-voltage production (single phase)
- Transformer is a static electromagnetic energy conversion device
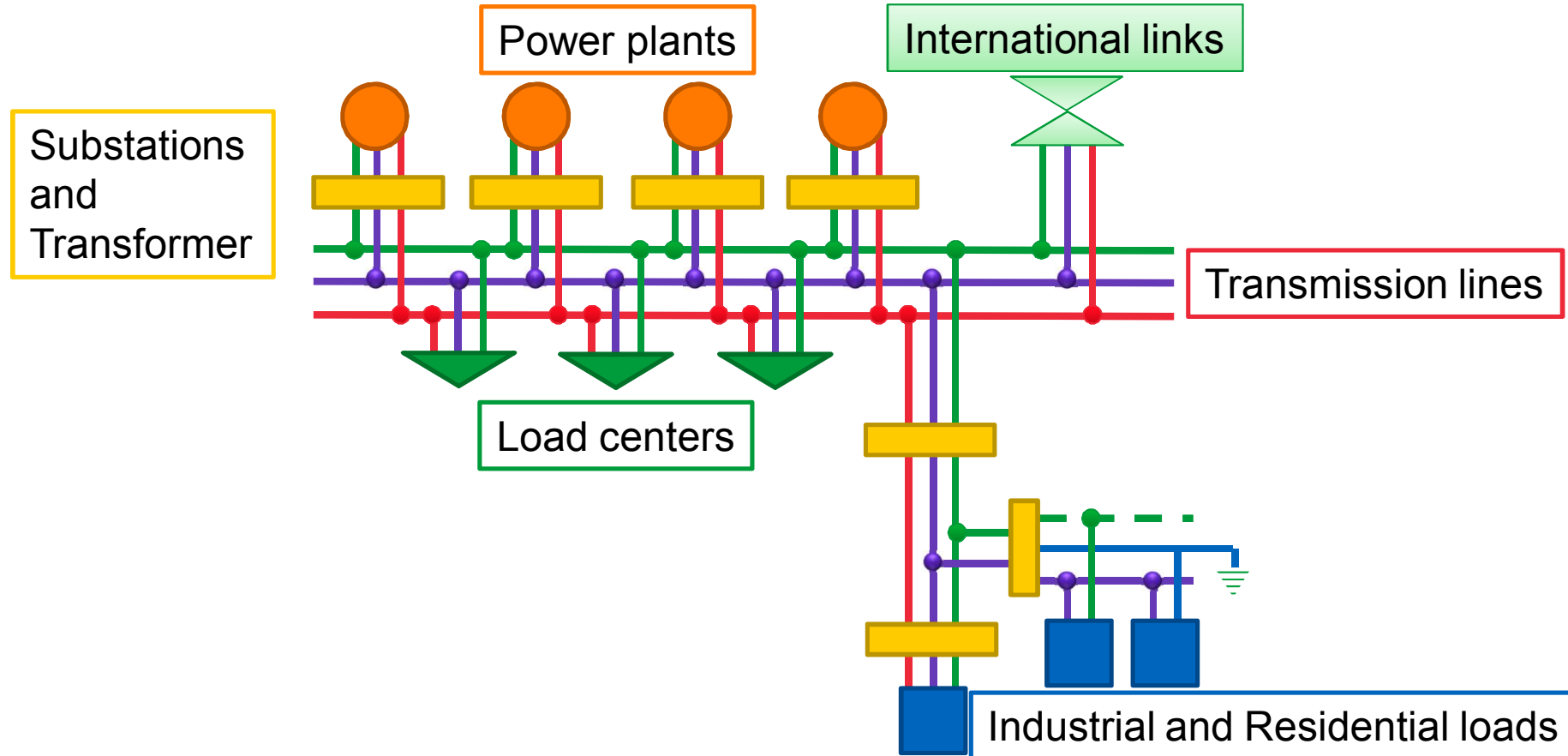
# Introduction

- Different kind of transformers are needed !



# Different types of transformers

Transmission transformer




Distribution transformer

Service transformer




Circuit transformer


# Transformer structure

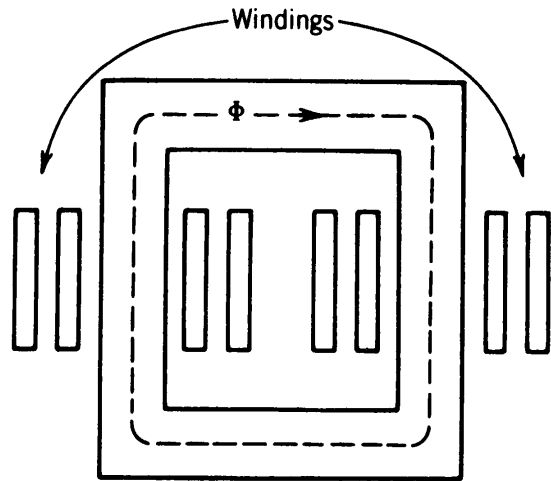

Core-type  
(Sydänmuuntaja)

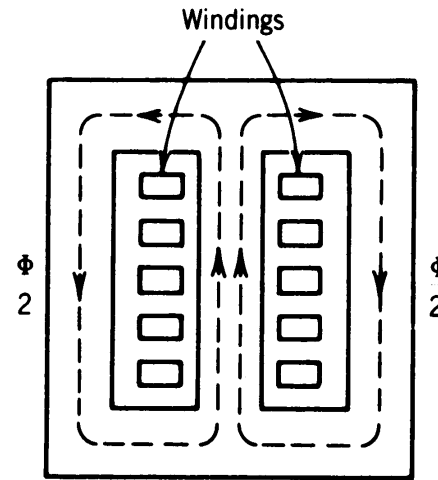


Shell-type  
(Vaippamuuntaja)

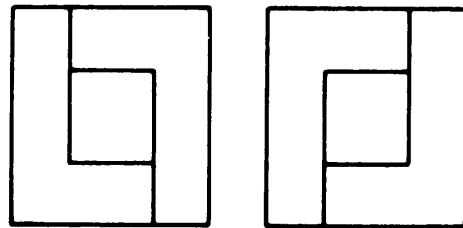

First layer

Second layer

L-shaped lamination

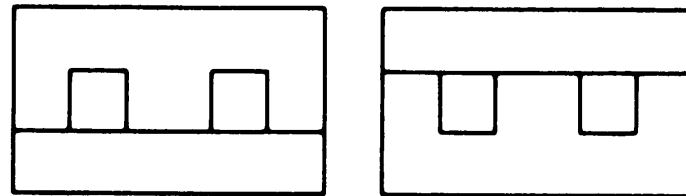

First layer



Second layer

E-shaped lamination


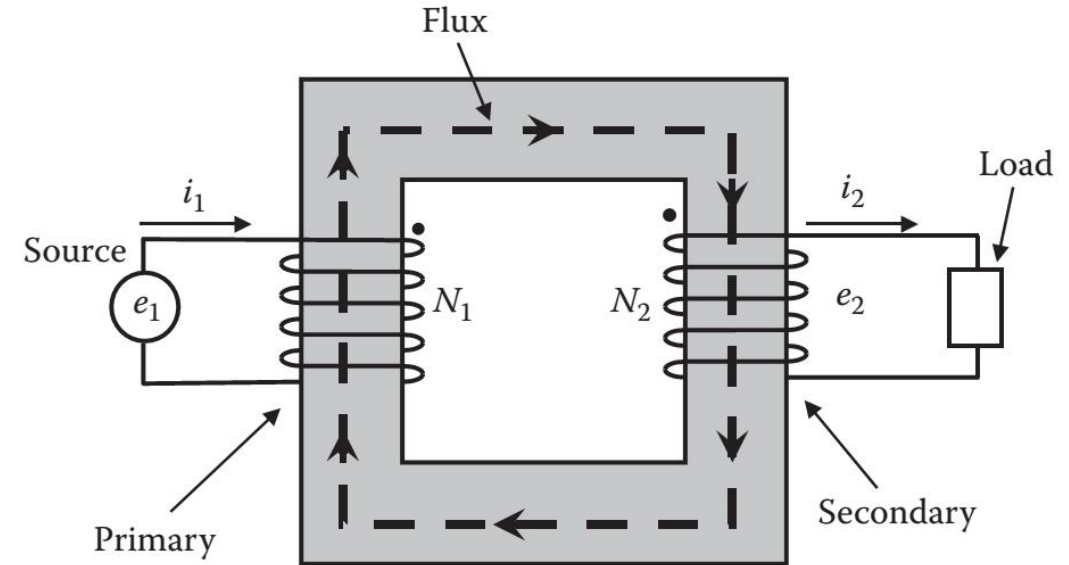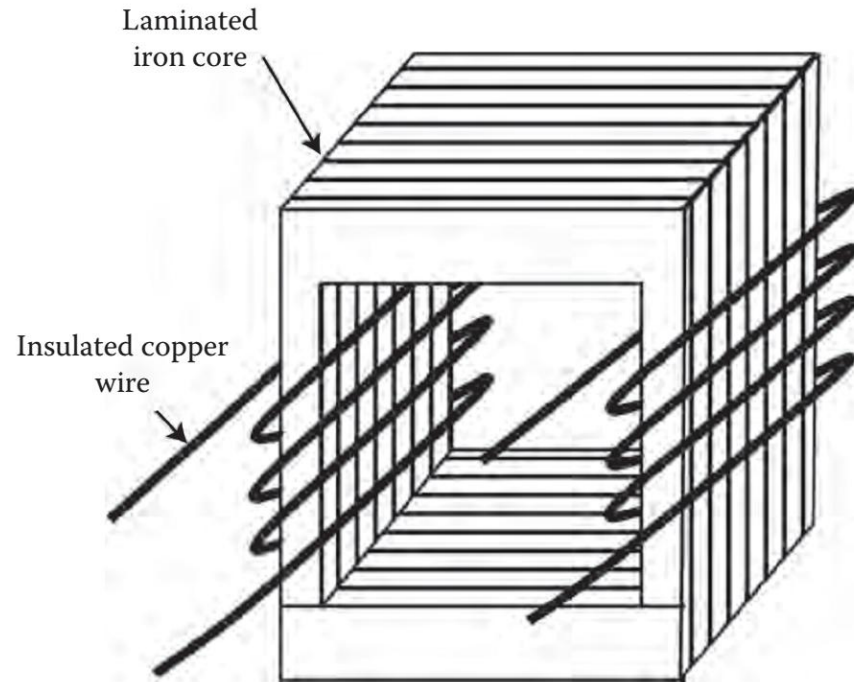
# Active components of transformers


- Iron core and at least two windings (coils)




- Alternating current produces flux, which induces voltage



# Basic operation of transformers

- Primary coil connected to voltage source  current
- Current magnetizes the core and produces flux
- Flux induces voltage in secondary coil
- Load connected to secondary voltage draws current
- Voltage also induced in core


 Eddy-current and other losses

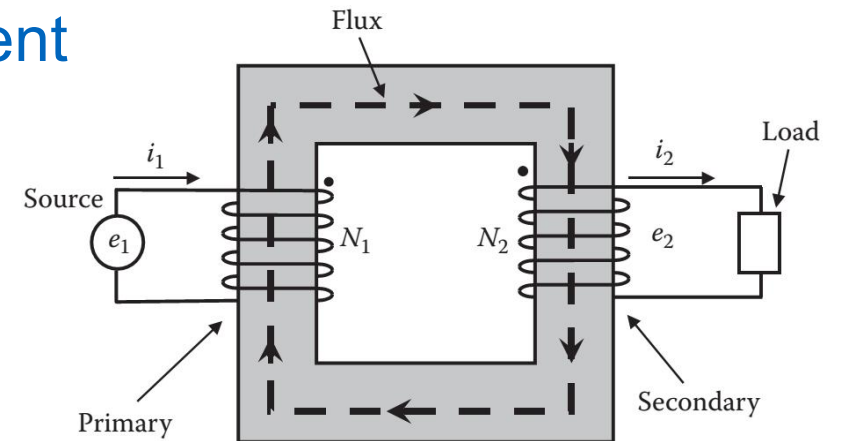
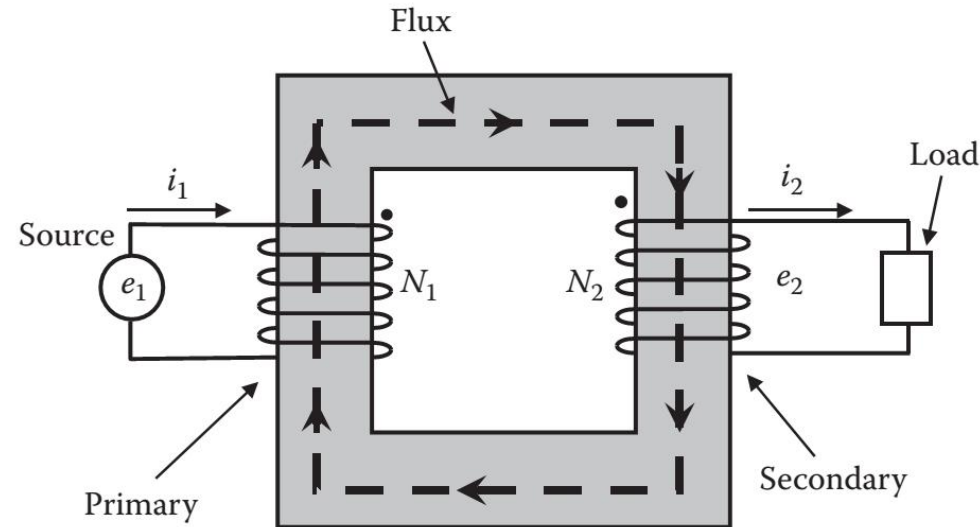
# Voltage ratio

- Faraday's law:

$$e_1 = -N_1 \frac{\partial \varphi}{\partial t} \quad \longrightarrow \quad \varphi = -\frac{1}{N_1} \int e_1 dt$$



$$e_2 = -N_2 \frac{\partial \varphi}{\partial t} \quad \longrightarrow \quad \frac{e_1}{N_1} = \frac{e_2}{N_2} = \frac{\partial \varphi}{\partial t} \quad \longrightarrow \quad \frac{E_1}{E_2} = \frac{N_1}{N_2}$$



# Current ratio


- Assume ideal transformer (no losses)

$$\begin{array}{l} \bar{S}_1 = \bar{E}_1 \bar{I}_1^* \\ \bar{S}_2 = \bar{E}_2 \bar{I}_2^* \end{array} \quad \bar{S}_1 = \bar{S}_2 \quad \longrightarrow \quad \frac{I_1}{I_2} = \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

- The quantity  $F = I_1 N_1 - I_2 N_2$  is called magnetomotive force
- Magnetomotive force is responsible of producing the flux
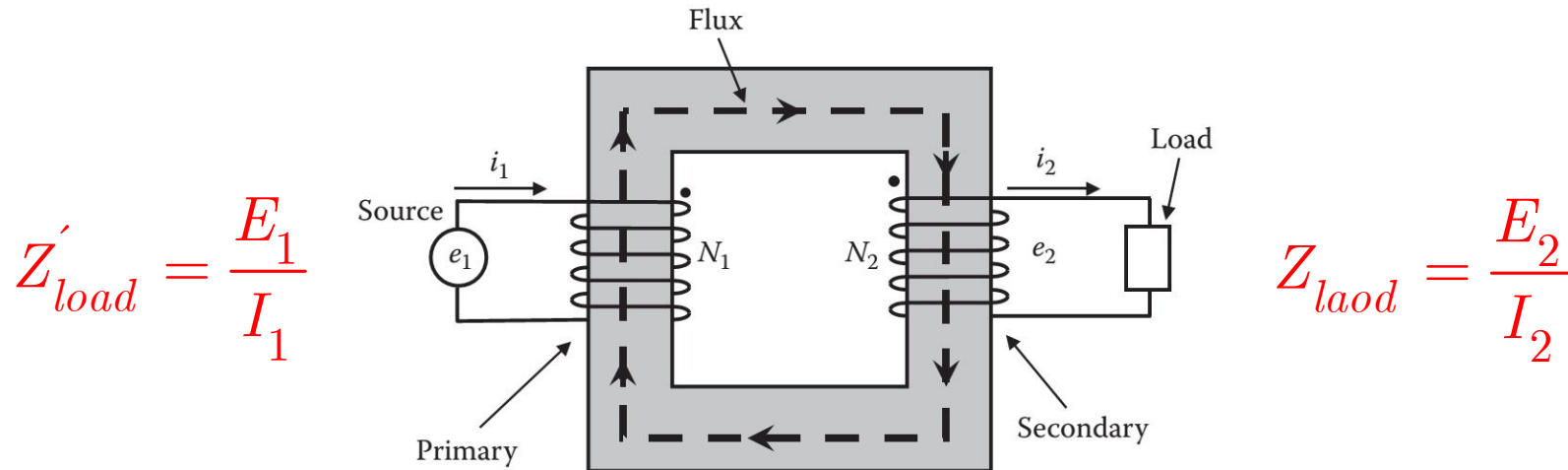
# Load Impedance seen by the primary

- Impedance connected to secondary is seen at the primary side.



$$Z'_{load} = \frac{E_1}{I_1}$$

$$Z_{load} = \frac{E_2}{I_2}$$

$$Z'_{load} = Z_{load} \left( \frac{N_1}{N_2} \right)^2$$

# Transformer ratings

- Mechanical ratings:
    - Thermal limits, dimensions, weight, volume, etc...
  - Electrical ratings
    - Voltages, currents, and power
  - Exceeding ratings can damage the transformer
    - Excessive voltages cause insulation failure
    - Excessive currents cause overheating, which results in melting
    - In both cases the result is internal short circuit
  - Nameplate “S, V1 / V2” e.g. “10kVA, 8kV / 240V)
-

# Main parameters from nameplate

- Nameplate: “10kVA, 8kV/240V)

– Voltage ratio: 
$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{8000}{240} = 33.33$$


– Rated primary current: 
$$I_1 = \frac{S}{E_1} = \frac{10000}{8000} = 1.25 A$$

– Rated secondary current: 
$$I_2 = \frac{S}{E_2} = \frac{10000}{240} = 41.67 A$$

– Rated load impedance: 
$$Z_{load} = \frac{E_2}{I_2} = \frac{240}{41.67} = 5.76 \Omega$$

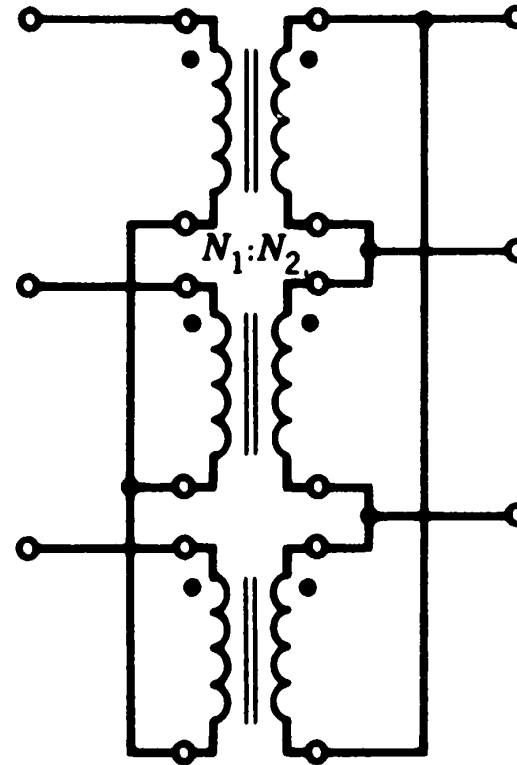
# Three-phase transformer

- Three similar single-phase transformers connected to form a three-phase transformer
- Four possible connection:  
Y- $\Delta$   $\Delta$ -Y  $\Delta$ - $\Delta$  Y-Y
- Some connections result in phase shift


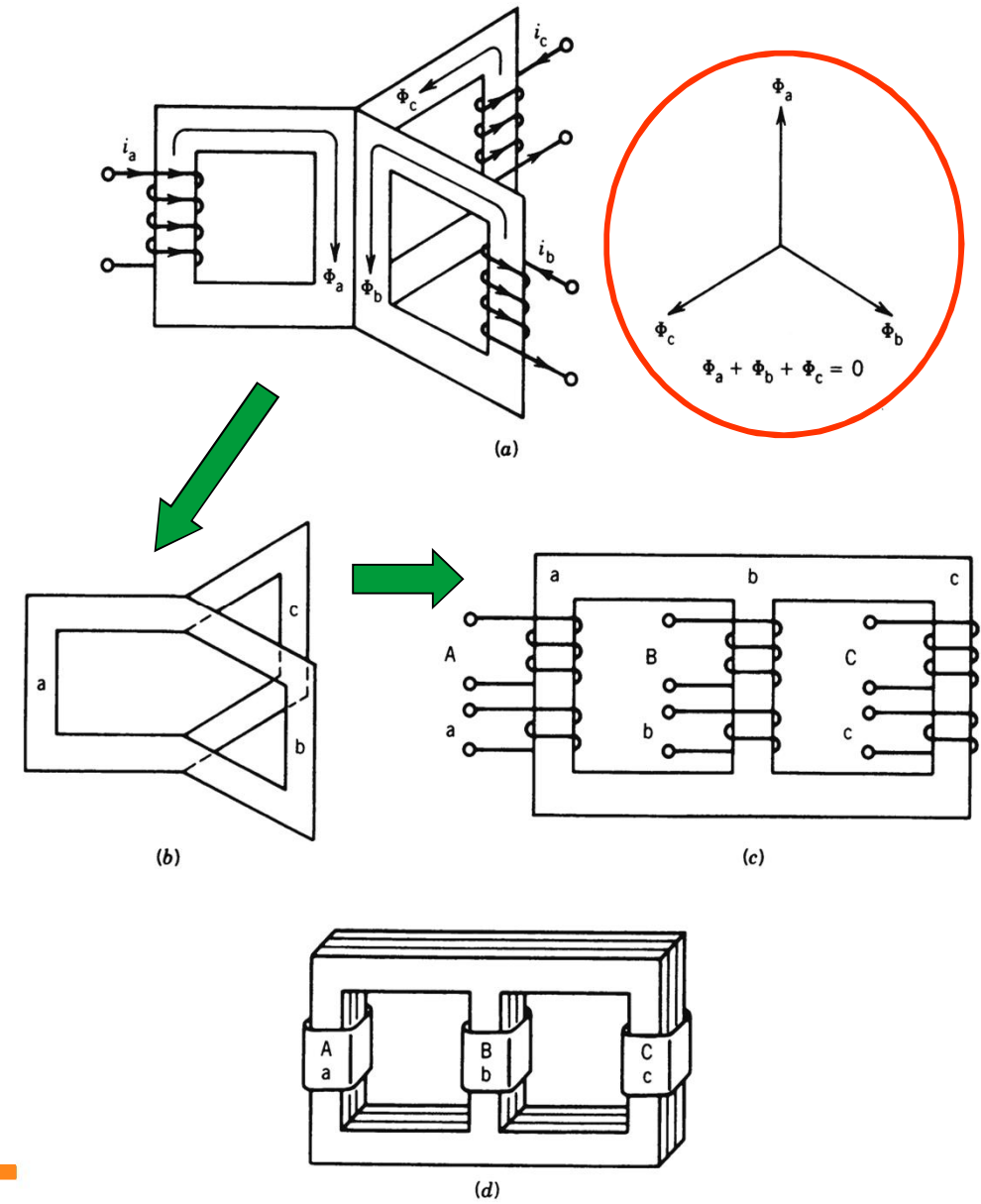
# Three-phase transformer unit

- Balanced three-phase voltage
- Balanced three-phase flux
- Return leg can be removed
- In-plan construction easy to manufacture





# Transformer structure





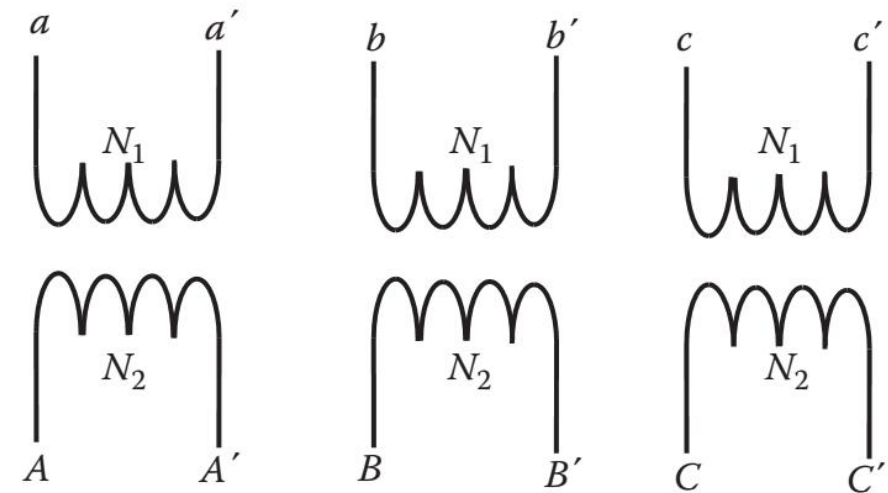
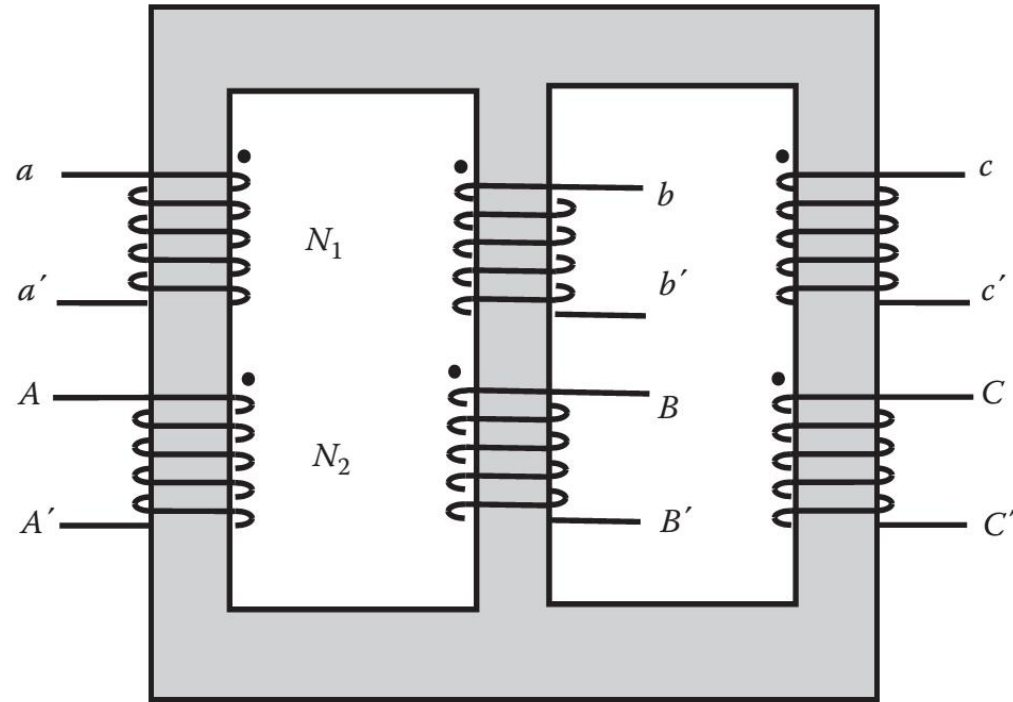
# Three-phase transformer

- Constructed from three legged core
- Nameplate: e.g. “60kVA, 8kV( $\Delta$ )/416(Y)”


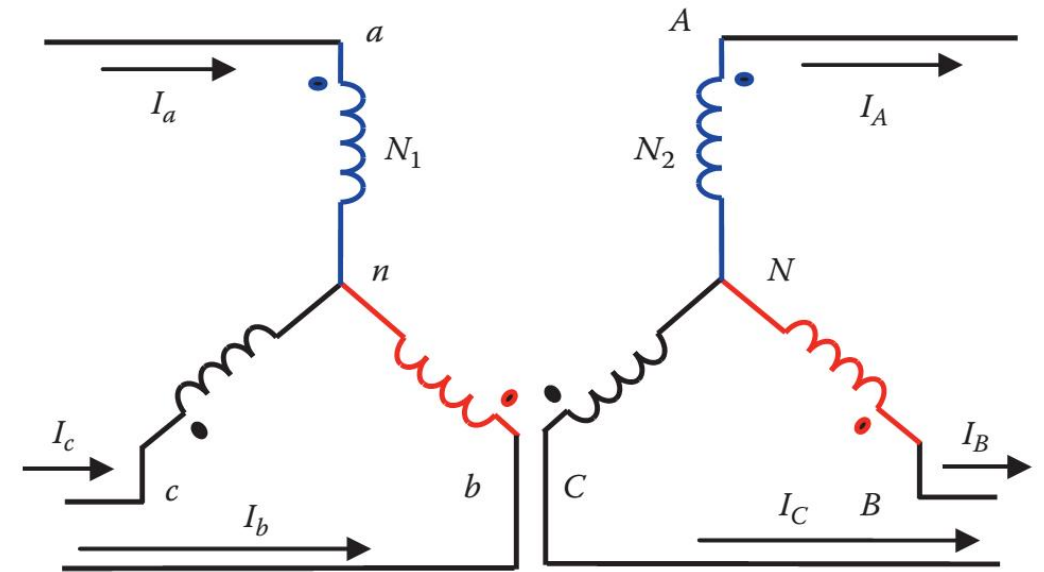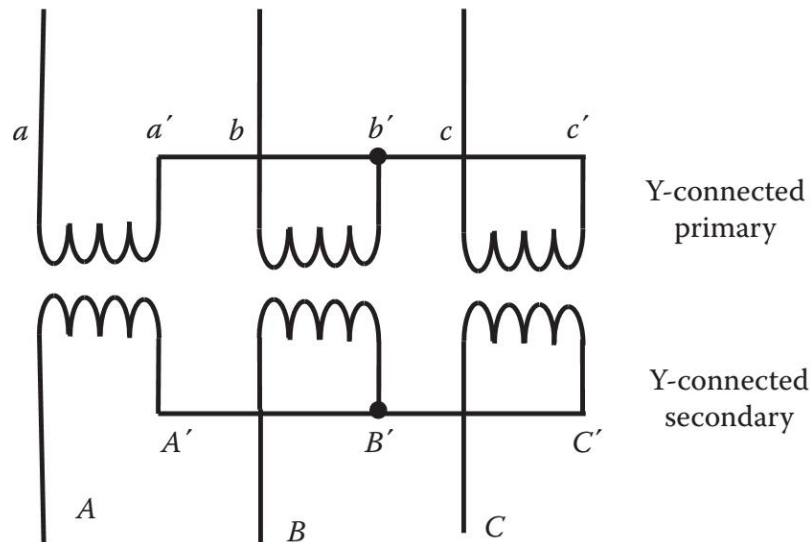
# Y-Y connection



- $a'$ ,  $b'$  and  $c'$  connected to the same point ( $n$ )
- $A'$ ,  $B'$ , and  $C'$  connected to the same point ( $N$ )
- Turn ratio equals voltage ratio equals current ratio



Anouar Belahcen

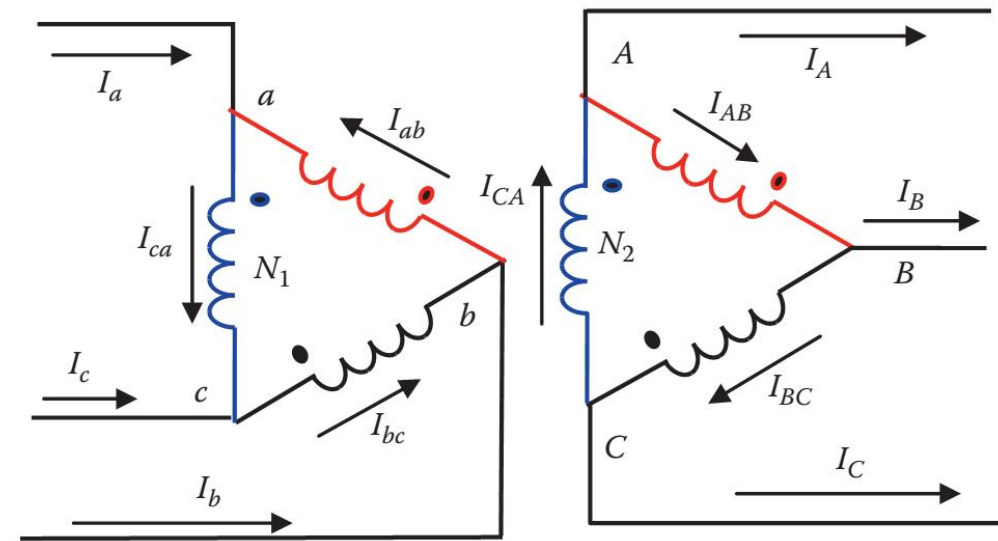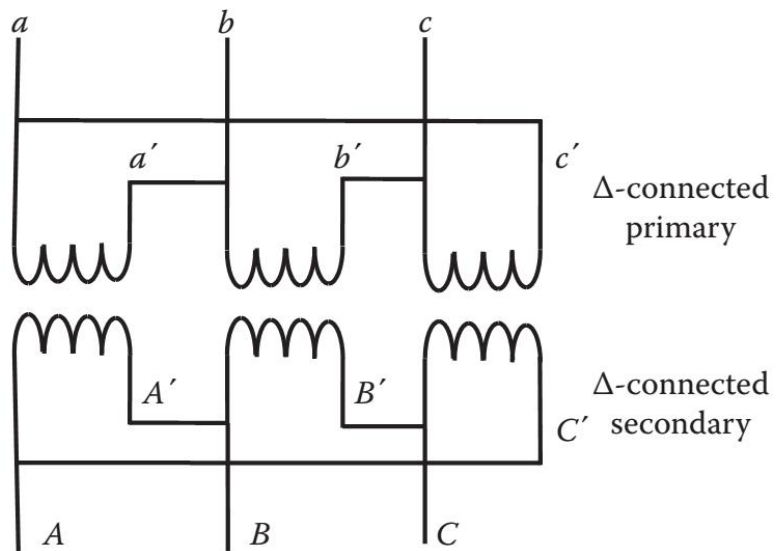
# $\Delta$ - $\Delta$ connection

- $a$ '- $b$ ,  $b$ '- $c$  and  $c$ '- $a$  connection. No neutral point
- $A$ '- $B$ ,  $B$ '- $C$ , and  $C$ '- $A$  connection. No neutral point
- Turn ratio equals voltage ratio equals current ratio



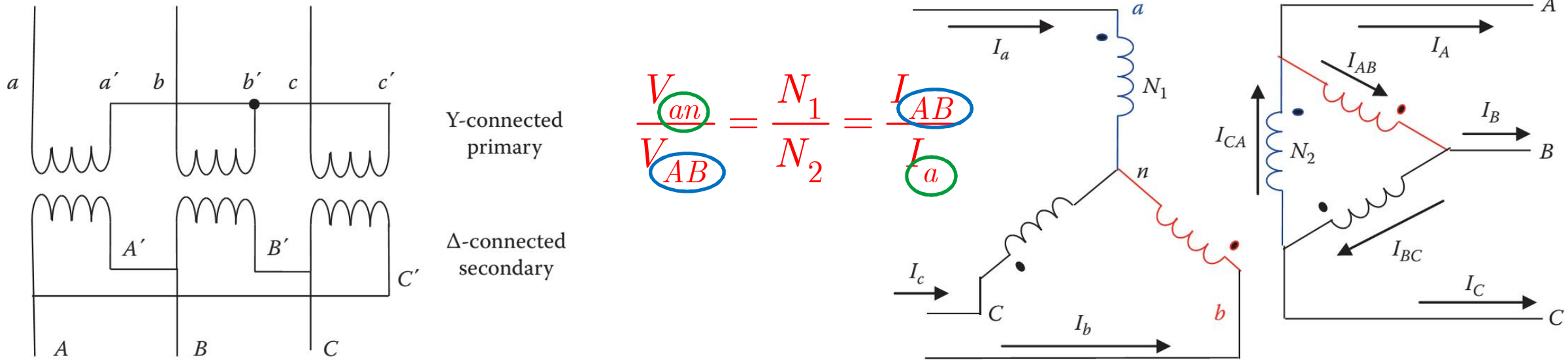
# Y- Δ connection (Δ-Y connection)

- a', b' and c' connected to the same point (n)
- A'-B, B'-C, and C'-A connection. No neutral point
- Pay attention to phase versus line-to-line quantities



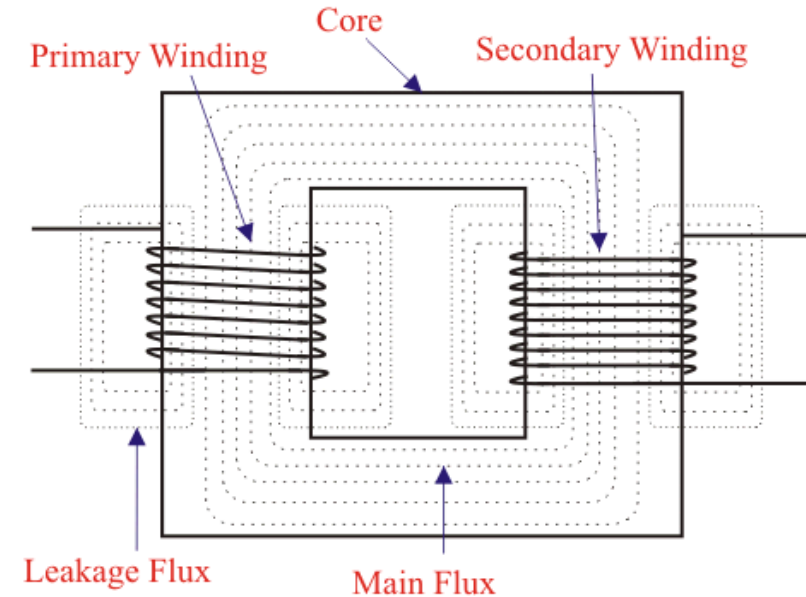
# Actual transformer

- In the previous slides we discussed ideal transformers
- Actual transformers present internal losses:
  - Resistive losses in the windings
  - Iron losses in the iron core
- Windings have inductances
- Iron core has finite permeability, thus requires magnetization current


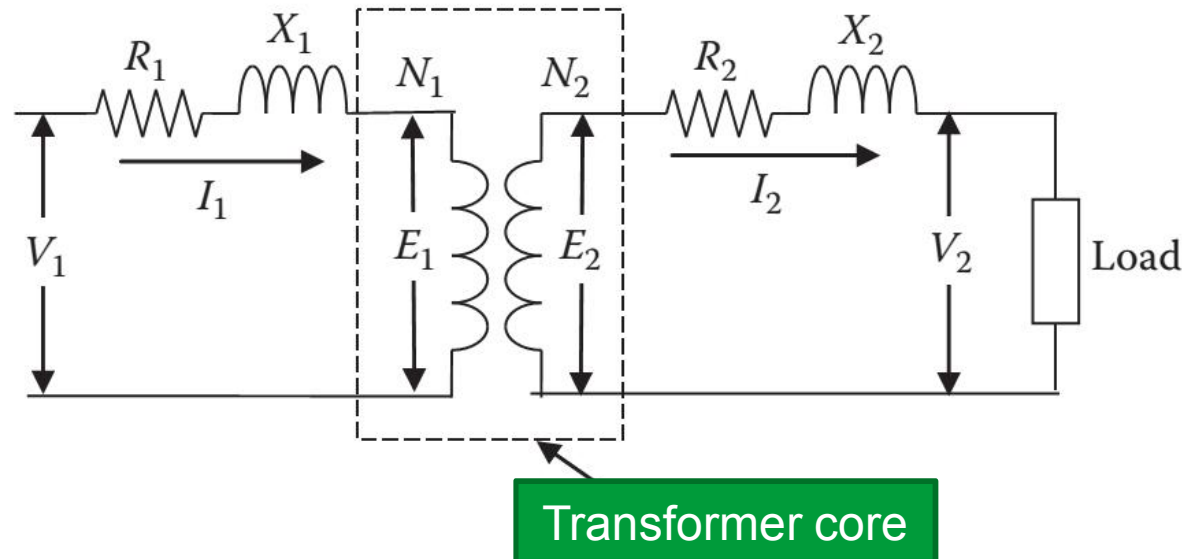
# Actual transformer


- Model of windings resistances and inductances
- Calculations with the ideal transformer are not handy
- Electromotive force different from terminal voltage



$$\frac{N_1}{N_2} = \frac{E_1}{E_2} \neq \frac{V_1}{V_2}$$

# Some concepts of magnetism

- Ampere and Faraday laws

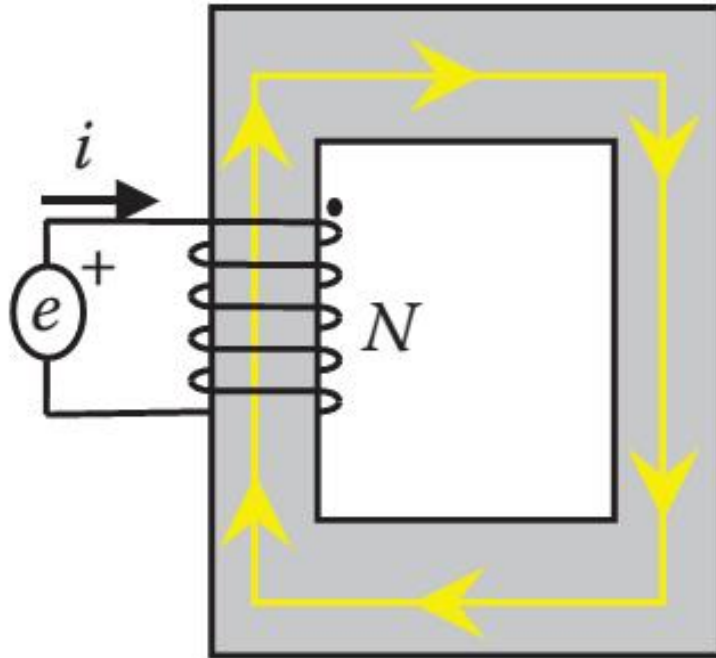



$$\oint H dl = \int J ds = Ni$$

$$e = -N \frac{\partial \psi}{\partial t} = -NA \frac{\partial B}{\partial t}$$



# Some concepts of magnetism

- Hysteresis

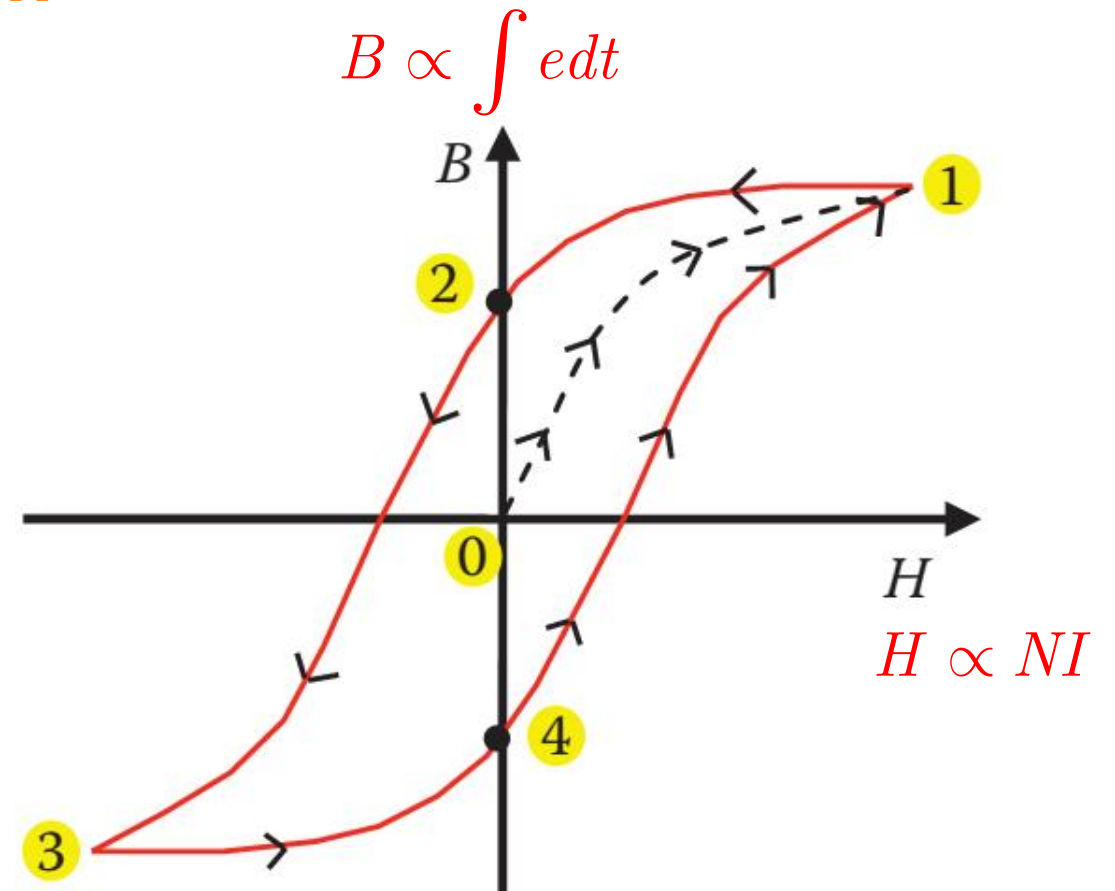
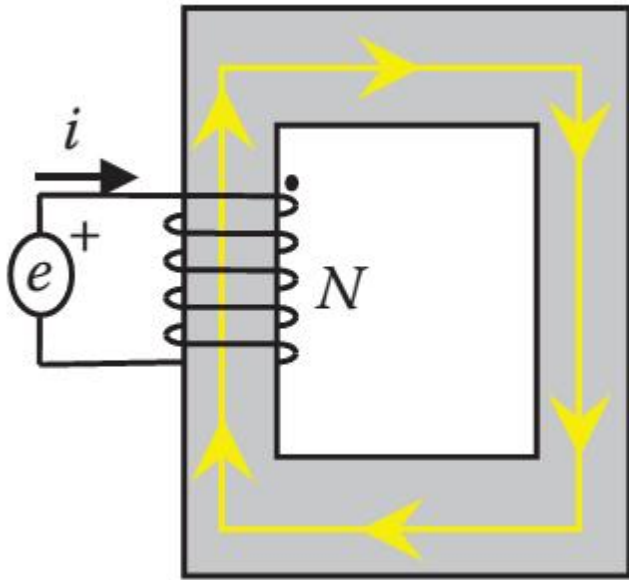


- Magnetic energy

$$W = \int H dB \quad \longrightarrow \quad P_{hys} \propto \hat{B}^2 f$$

# Some concepts of magnetism



- Eddy-current

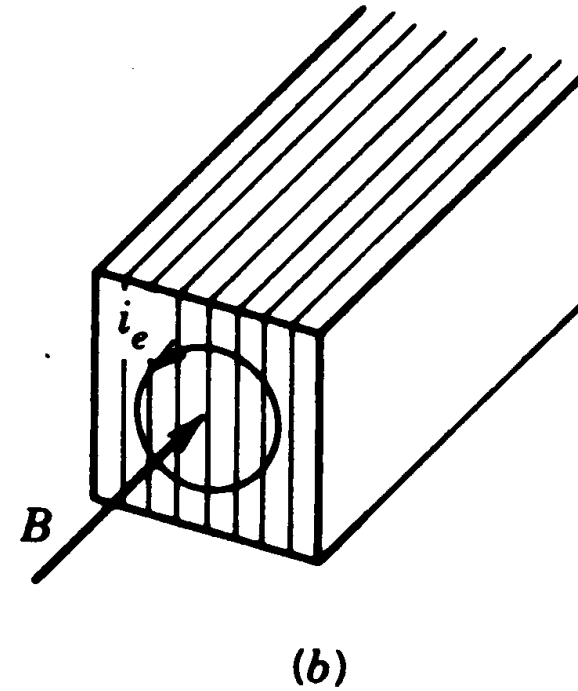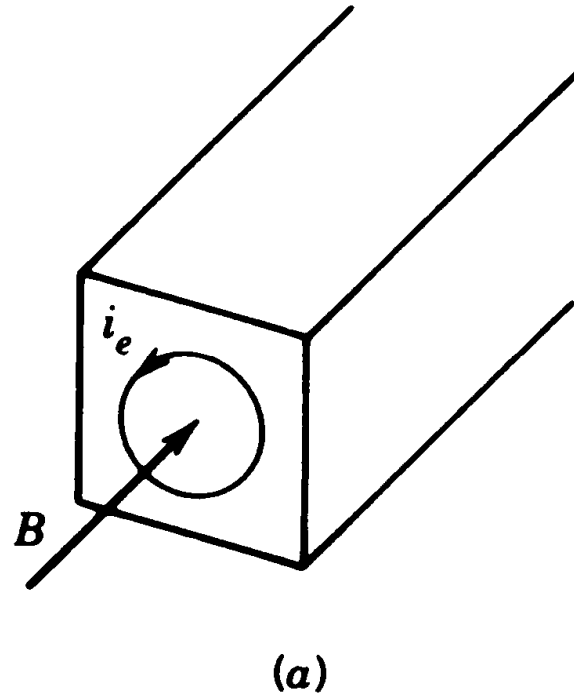

$$i_e \propto e \propto \frac{dB}{dt} \quad \longrightarrow \quad P_{eddy} \propto \hat{B}^2 f^2$$
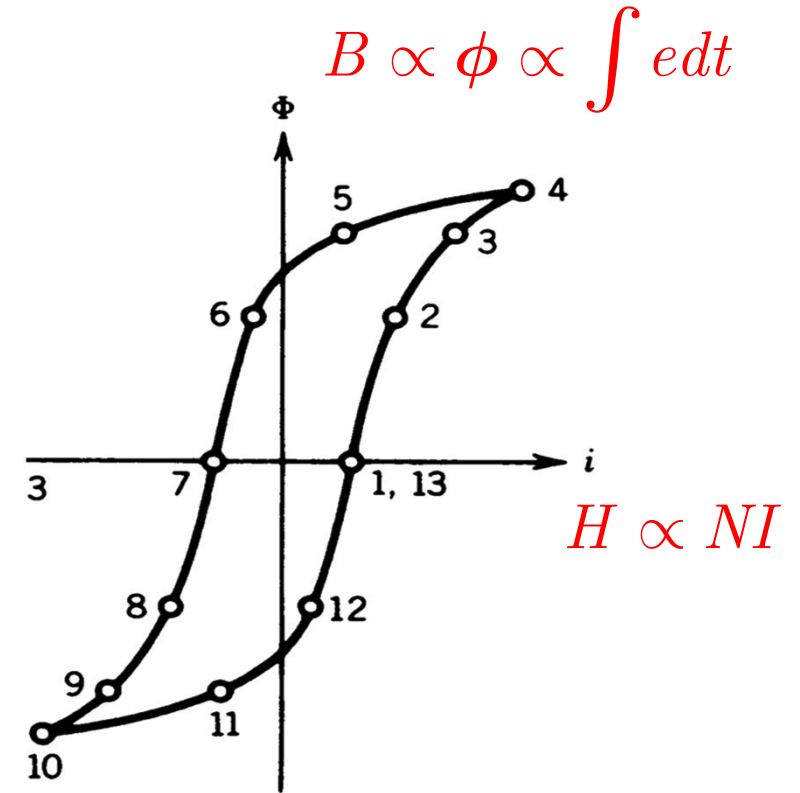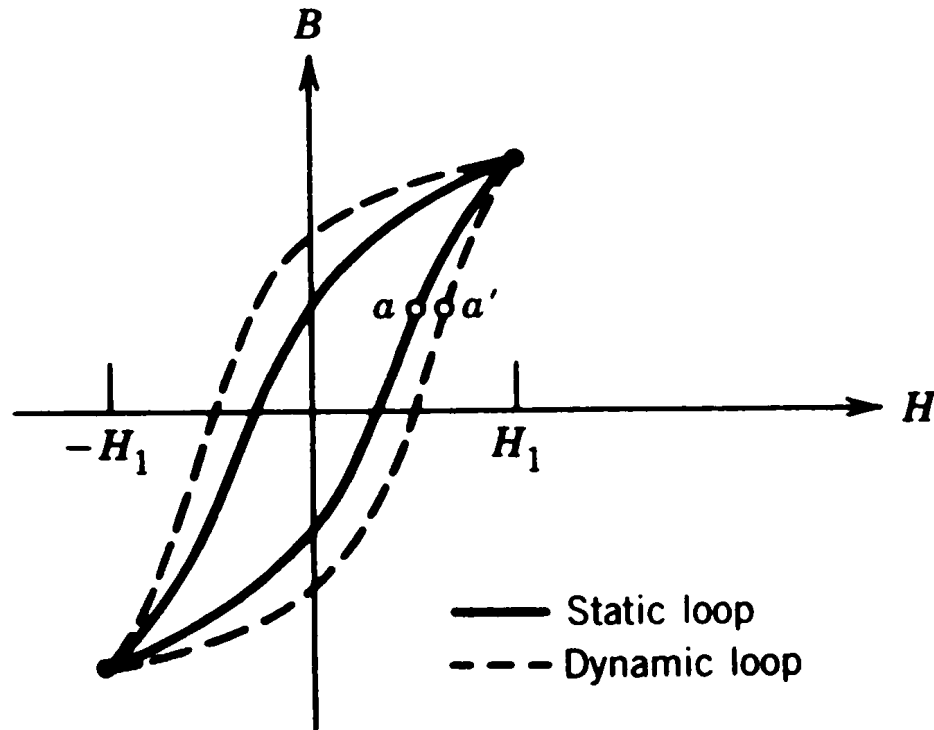
# Core losses

- Lumping of hysteresis and Eddy-current losses
- Shifting from BH to voltage and current




# Iron core as circuit element

- The behavior of iron core can be obtained by two circuit element:
  - Resistor to simulate loss

$$\int e dt = -\frac{E_{\max}}{\omega} \cos(\omega t)$$
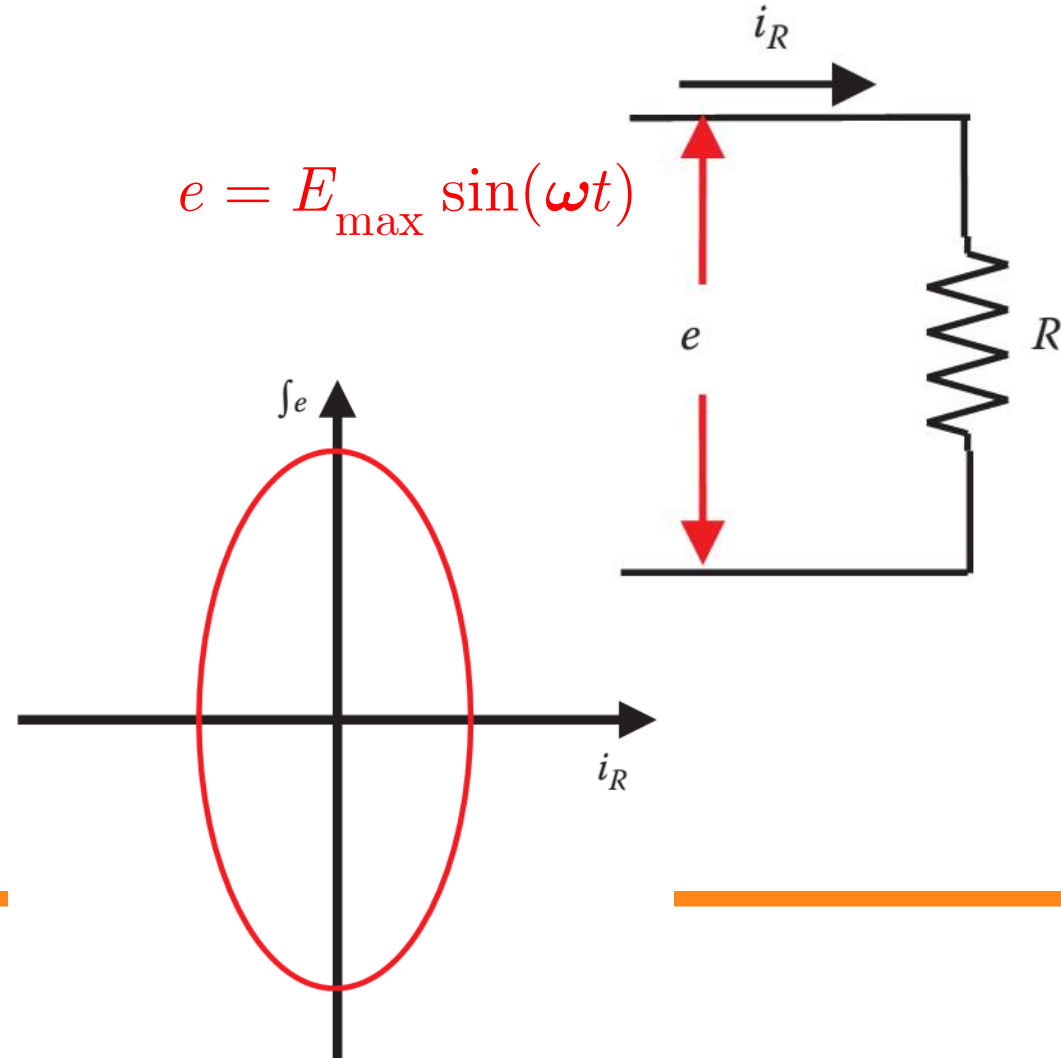
$$i_R = \frac{e}{R} = \frac{E_{\max}}{R} \sin(\omega t)$$





# Iron core as circuit element

- The behavior of iron core can be obtained by two circuit element:
  - Inductance to simulate phase shift


$$\int e dt = -\frac{E_{\max}}{\omega} \cos(\omega t)$$
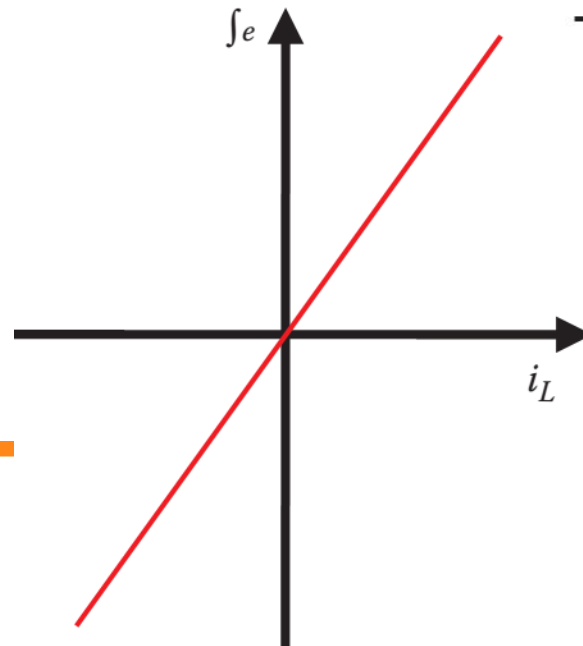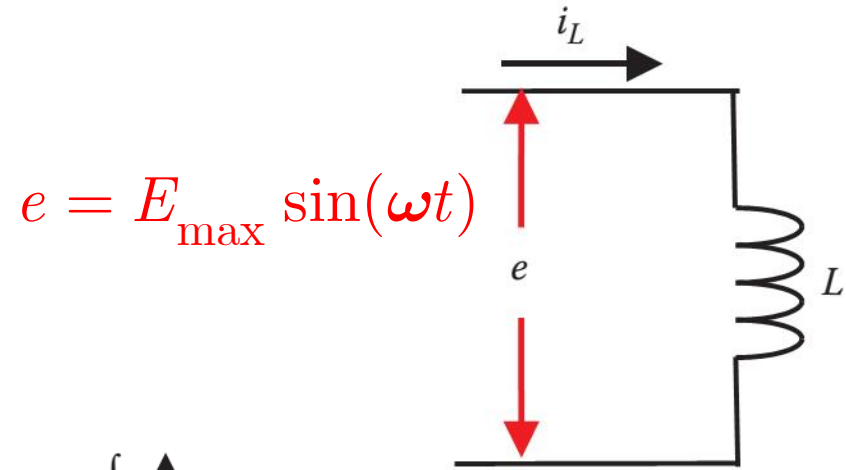
$$i_L = \frac{1}{L} \int e dt = -\frac{E_{\max}}{\omega L} \cos(\omega t)$$




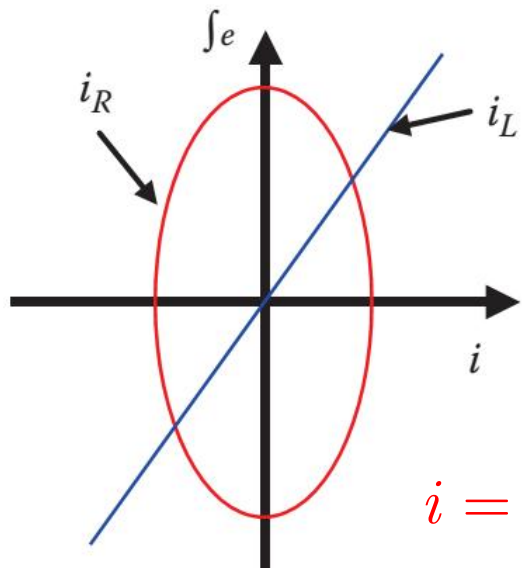
# Iron core as circuit element

- The behavior of iron core can be obtained by two circuit element:
  - Combine resistor and inductor




$$i = i_R + i_L$$

$$e = E_{\max} \sin(\omega t)$$

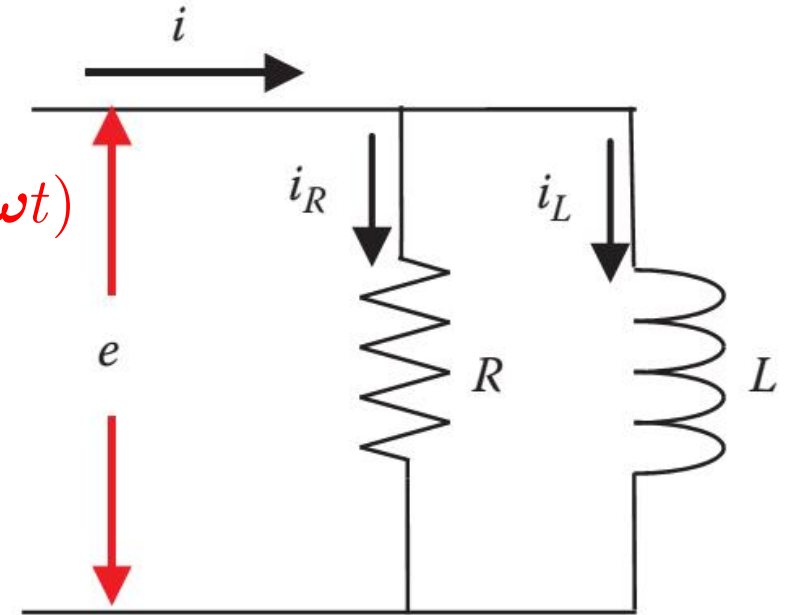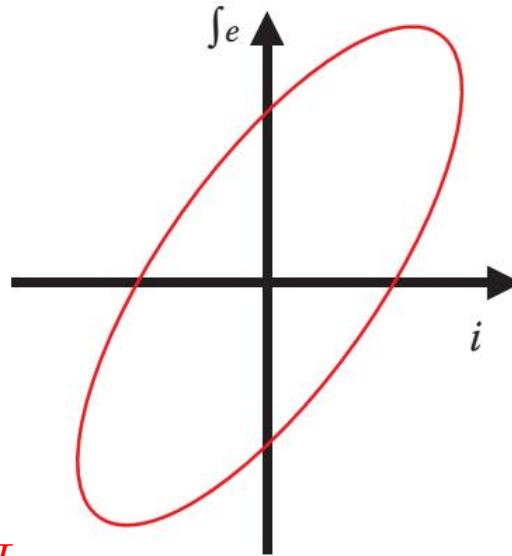


# Equivalent circuit of transformer

- Introduce the core on the primary side

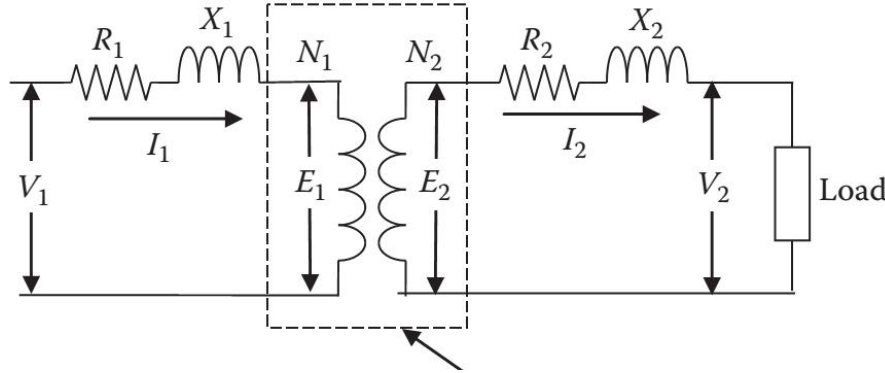
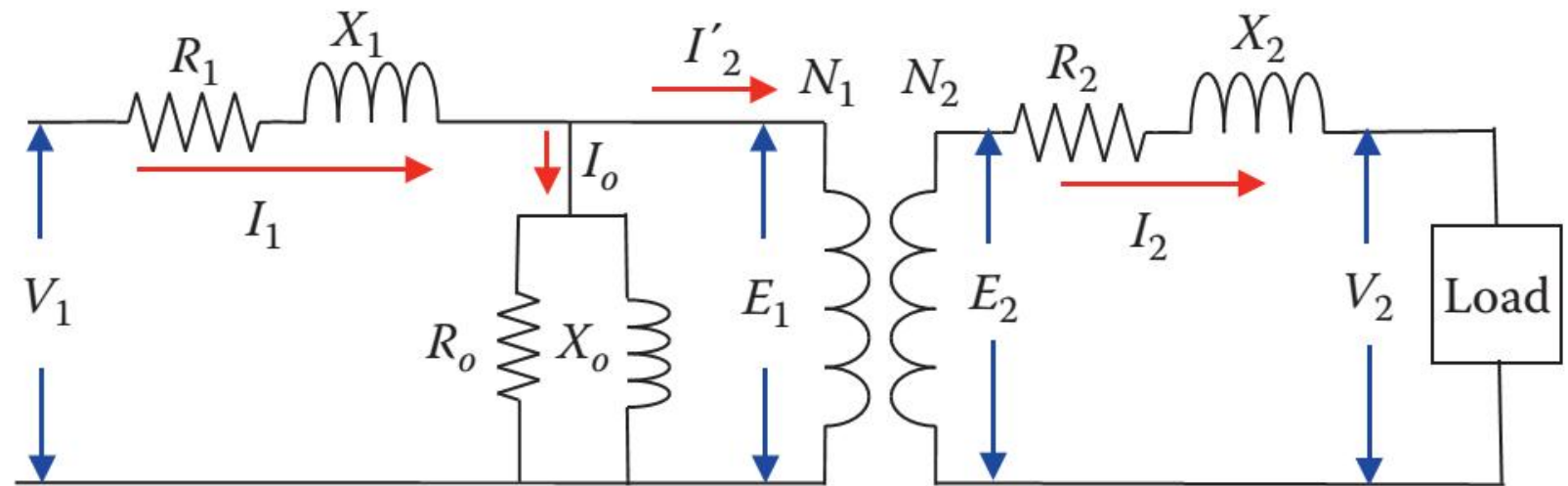
$$\bar{I}'_2 = \frac{N_2}{N_1} \bar{I}_2$$




Anouar Belahcen


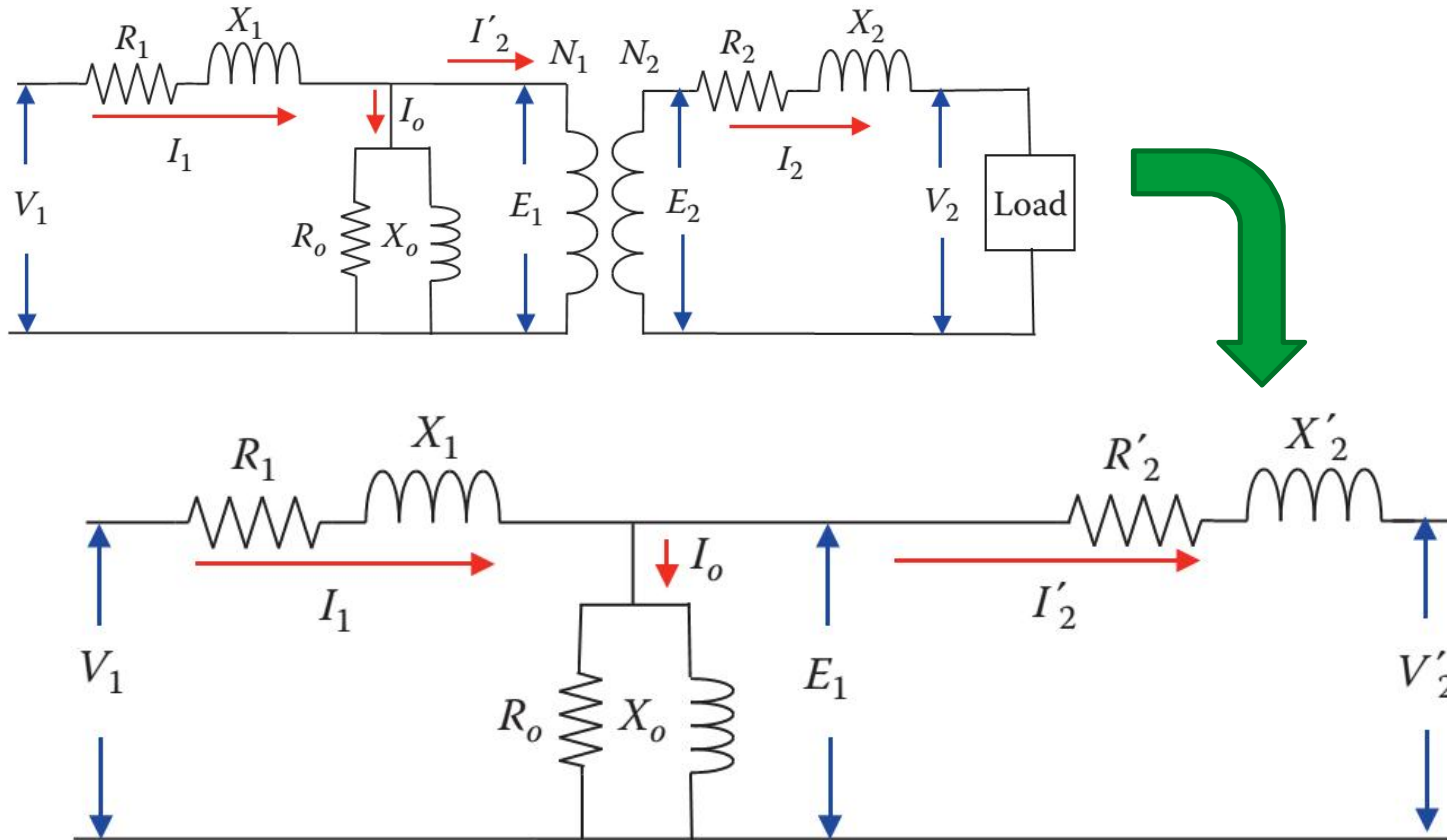
# Equivalent circuit of transformer

- Reduce the secondary side to the primary






$$\bar{V}'_2 = \frac{N_1}{N_2} \bar{V}_2$$

$$R'_2 = \left( \frac{N_1}{N_2} \right)^2 R_2$$

$$X'_2 = \left( \frac{N_1}{N_2} \right)^2 X_2$$

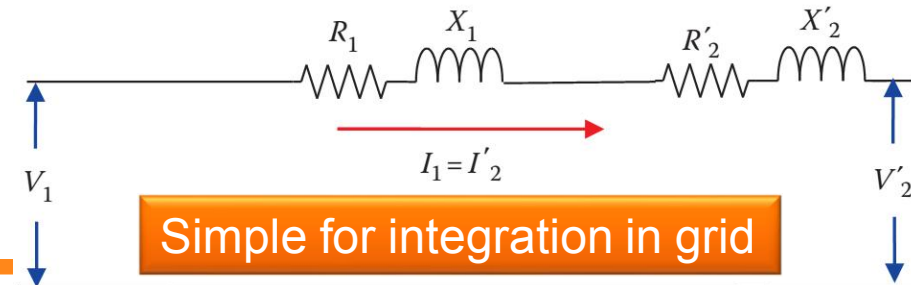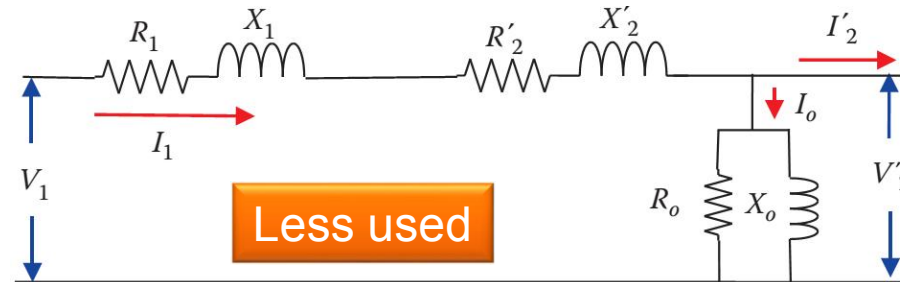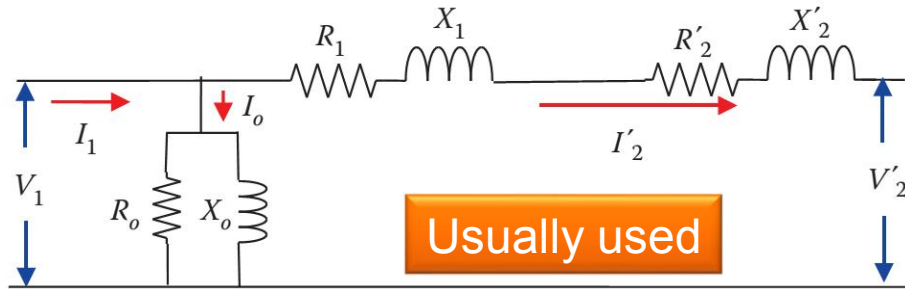
# Approximate equivalent circuit

- The magnetizing branch can be shifted to either side or removed!


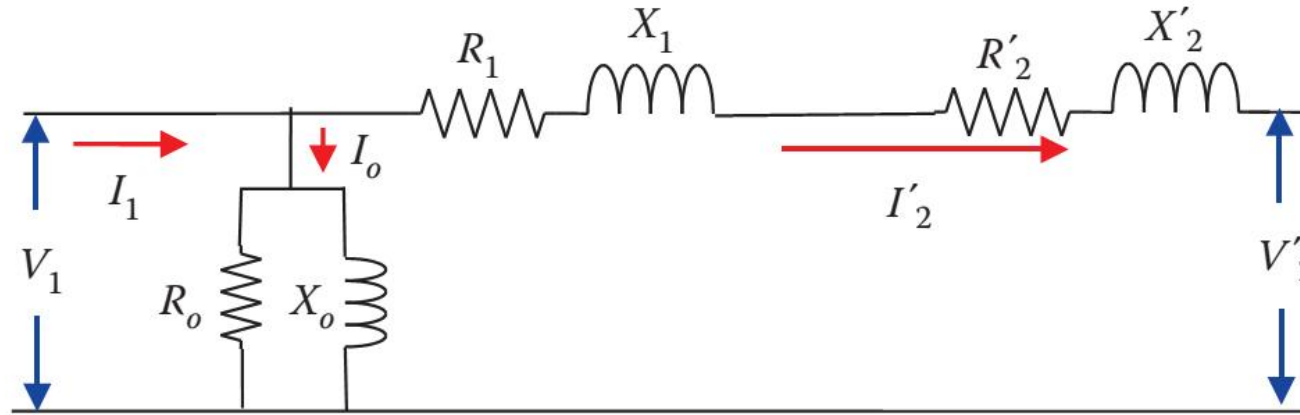
# Parameters of equivalent circuit


- Some measurements are needed for the extraction of the equivalent circuit parameters




- Standard measurements:
  - No-load test: gives magnetization characteristic
  - Short-circuit test: gives winding characteristics
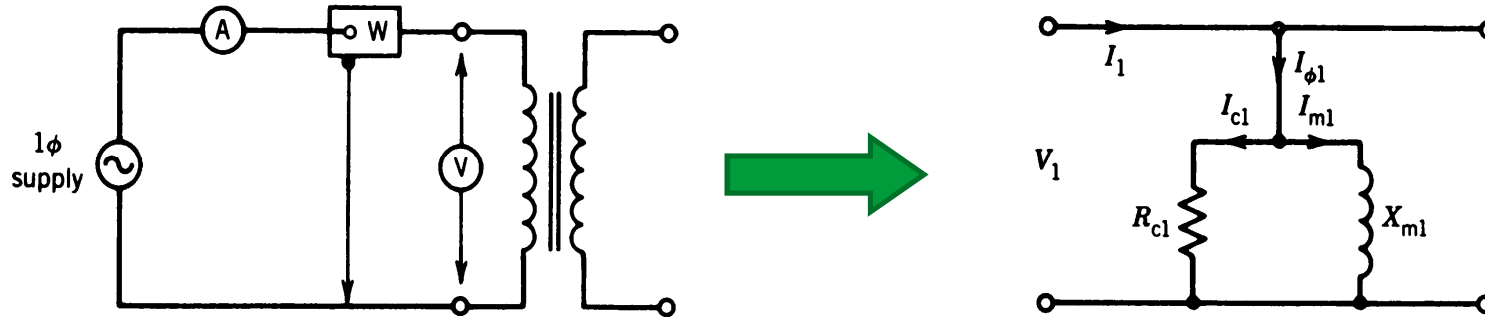
# Equivalent Circuit Parameters

- **No-load test:** rated voltage on one side, the other side is open



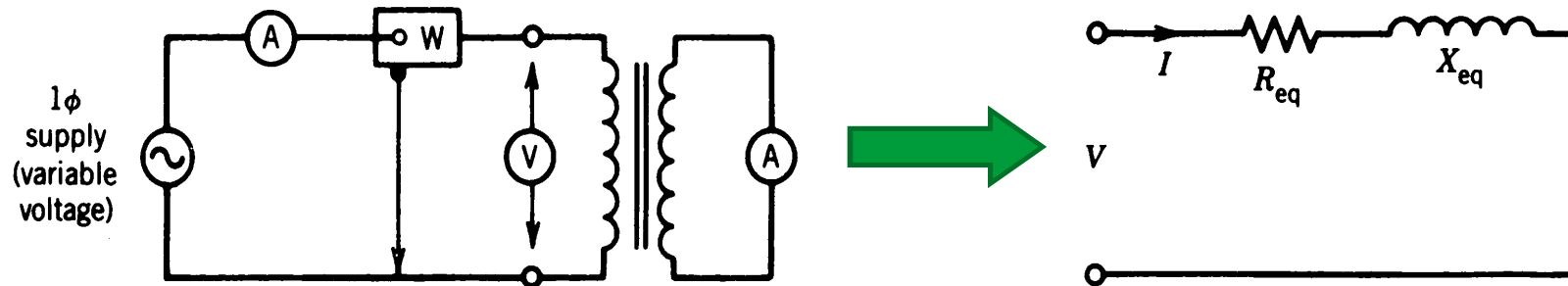- **Short-Circuit test:** rated current on one side, the other side is short-circuited



# Equivalent Circuit Parameters

- Calculation example: 10 kVA, 2200/220 V, 60 Hz
- Open-circuit done with rated voltage applied to low-voltage side of transformer
- Short-circuit test done with low voltage side shorted and the transformer is fed from high-voltage side

	Open-circuit test H-voltage side open	Short-circuit test L-voltage side shorted
Voltmeter	220 V	150 V
Ammeter	2,5 A	4,55 A
Wattmeter	100 W	215 W

# Equivalent Circuit Parameters

- Open-circuit results

$$R_{0L} = \frac{V_{oc}^2}{P_{oc}} = \frac{220^2}{100} = 484 \Omega$$

$$I_0 = \frac{V_{oc}}{R_{0L}} = \frac{220}{484} = 0.45 A$$


$$I_{X_0} = \sqrt{(I_{oc}^2 - I_{R_0}^2)} = \sqrt{(2.5^2 - 0.45^2)} = 2.46 A \quad X_{0L} = \frac{V_{oc}}{I_{X_0}} = \frac{220}{2.46} = 89.4 \Omega$$

- Short-circuit results

$$R_{eqH} = \frac{P_{sc}}{I_{sc}^2} = \frac{215}{4.55^2} = 10.4 \Omega$$



$$Z_{eqH} = \frac{V_{sc}}{I_{sc}} = \frac{150}{4.55} = 32.97 \Omega$$
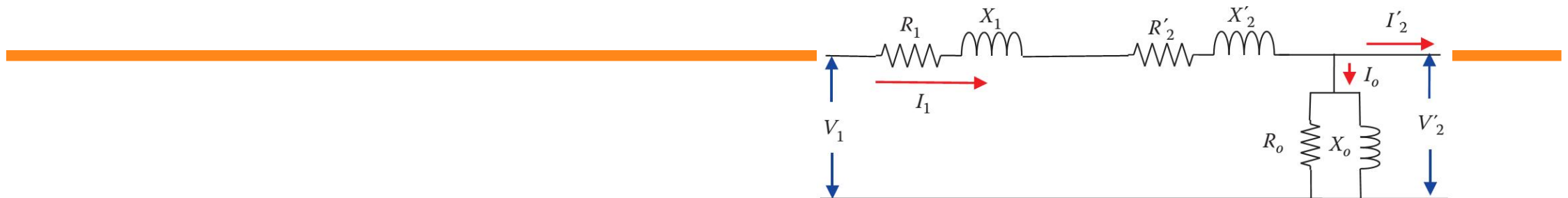
$$X_{eqH} = \sqrt{(Z_{eqH}^2 - R_{eqH}^2)} = \sqrt{(32.97^2 - 10.4^2)} = 31.3 \Omega$$


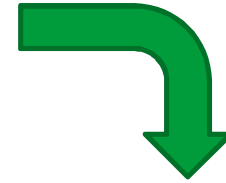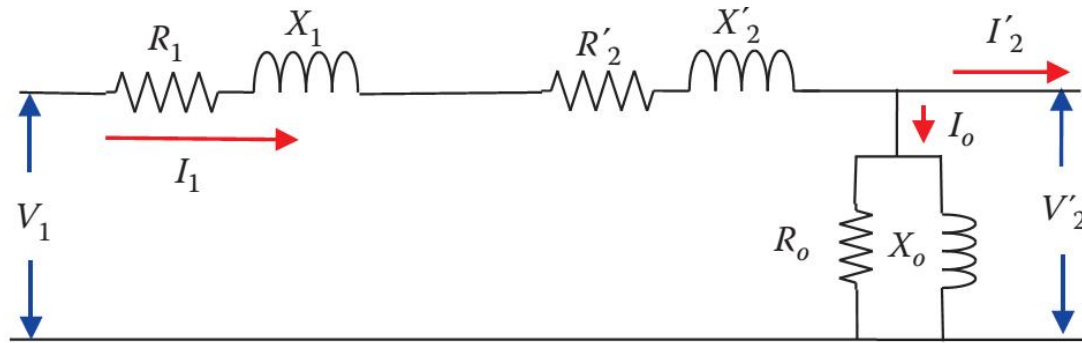
# Equivalent Circuit Parameters


- Move the magnetizing branch from low voltage side to high voltage side



$$a = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{2200}{220} = 10$$

$$R_{oH} = a^2 R_{oL} = 10^2 \times 484 = 48400 \Omega$$

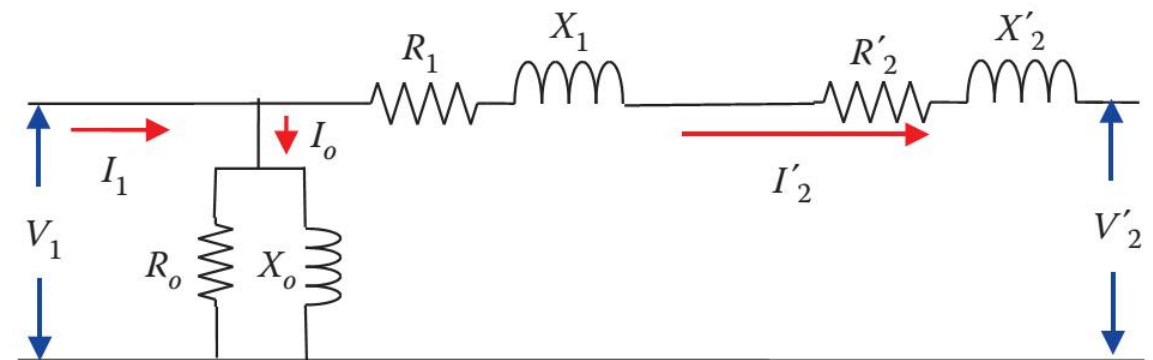
$$X_{oH} = a^2 X_{oL} = 10^2 \times 89.4 = 8940 \Omega$$


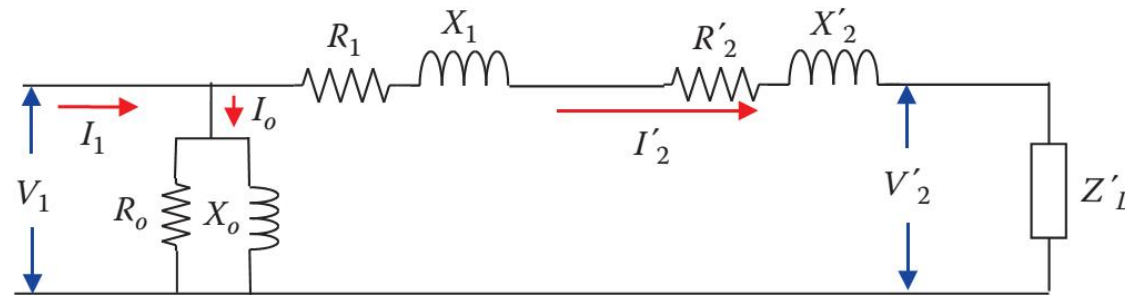
# Transformer analysis

- Transformer and load parameters:


$$\frac{N_1}{N_2} = 10 \quad R_{eq} = R_1 + R'_2 = 1 \Omega \quad R_0 = 1000 \Omega$$
$$X_{eq} = X_1 + X'_2 = 10 \Omega \quad X_0 = 5000 \Omega$$
$$\bar{Z}_L = 0.5 \angle 30^\circ \Omega$$



- The primary voltage is 1000 V, Compute load voltage



# Transformer analysis

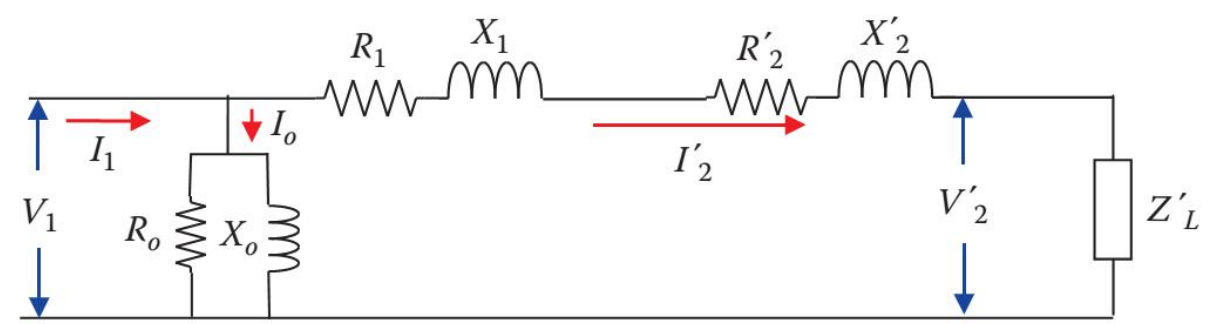

- Load

$$Z'_L = \left( \frac{N_1}{N_2} \right)^2 Z_L = 100 \times 0.5 = 50 \Omega$$

- Secondary current

$$\bar{I}'_2 = \frac{\bar{V}_1}{\left( R_{eq} + jX_{eq} \right) + \bar{Z}'_L} = \frac{1000 \angle 0^\circ}{(1 + j10) + 50 \angle 30^\circ} = 17.7 \angle -38.31^\circ \text{ A}$$

- Load voltage

$$\bar{V}'_2 = \bar{I}'_2 \bar{Z}'_L = (17.7 \angle -38.31^\circ)(50 \angle 30^\circ) = 885 \angle -8.31^\circ \text{ V}$$

$$V_2 = \frac{N_2}{N_1} V'_2 = 88.5 \text{ V}$$

# Transformer Efficiency

- Efficiency

$$\eta = \frac{\text{Output power}}{\text{Input power}} = \frac{\text{Output power}}{\text{Output power} + \text{losses}} = \frac{\text{Input power} - \text{losses}}{\text{Input power}}$$

- Output power

$$P_{out} = V_2 I_2 \cos(\theta_2) = V_2' I_2' \cos(\theta_2)$$

- Input power

$$P_{in} = V_1 I_1 \cos(\theta_1)$$


- Losses

- Copper losses


$$P_{Cu} = (I_2')^2 (R_1 + R_2')$$

- Iron losses

$$P_{iron} = \frac{V_1^2}{R_0}$$

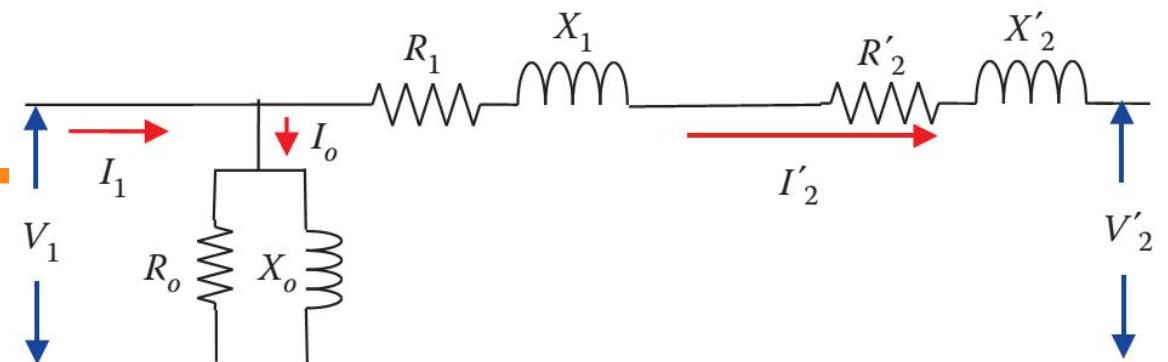

# Transformer Efficiency

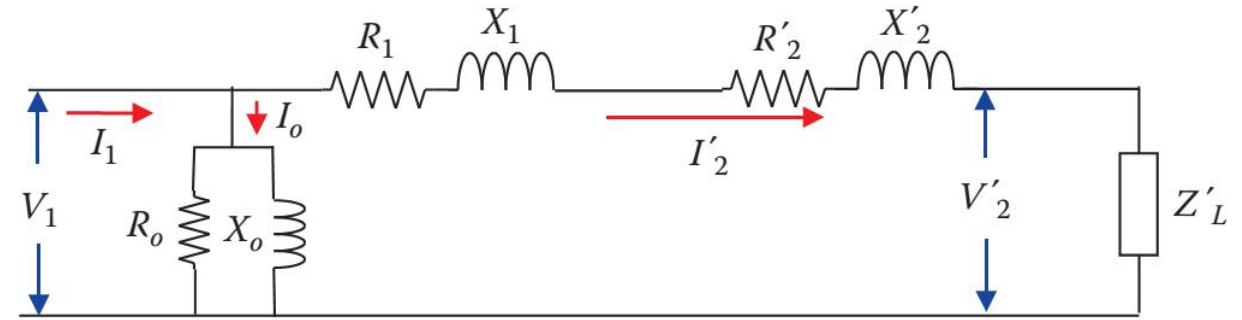

$$P_{Cu} = (I'_2)^2 R_{eq} = 17.7^2 \times 1 = 313.29 \text{ W}$$

$$P_{iron} = \frac{V_1^2}{R_0} = \frac{1000^2}{1000} = 1 \text{ kW}$$

$$P_{out} = V'_2 I'_2 \cos(\theta_2) = 885 \times 17.7 \times \cos 30 = 13.57 \text{ kW}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{Cu} + P_{iron}} = \frac{13570}{13570 + 313.29 + 1000} = 91.2\%$$