

Homework 7: Basic Components of Power system

Explain the calculation of real and reactive power in a three phase power system. Give an example of a load having both resistance and inductive reactance. Give the power factor of the load. How can reactive power be compensated?