

## Question 1:

A load is supplied by,

$$V(t) = 5 + 100 \cos(314t) + 6 \cos(2(314)t + 15^\circ) + 40 \cos(3(314)t + 30^\circ)$$

The current is given as,

$$i(t) = 8 + 50 \cos(314t + 30^\circ) + 6 \cos(2(314)t + 45^\circ) + 10 \cos(3(314)t + 65^\circ)$$

Find,

- a) RMS Voltage.
- b) RMS Current.
- c) THD of load current.



$$\mathbf{v(t)} = 5 + 100 \cos(314t) + 6 \cos(2(314)t + 15^\circ) + 40 \cos(3(314)t + 30^\circ)$$
$$\mathbf{i(t)} = 8 + 50 \cos(314t + 15^\circ) + 6 \cos(2(314)t + 30^\circ) + 10 \cos(3(314)t + 45^\circ)$$

### a) RMS Voltage:

Using the formula,

$$V_{rms} = \sqrt{V_0^2 + V_{1,rms}^2 + V_{2,rms}^2 + \dots}$$
$$V_{rms} = \sqrt{(5)^2 + \left(\frac{100}{\sqrt{2}}\right)^2 + \left(\frac{6}{\sqrt{2}}\right)^2 + \left(\frac{40}{\sqrt{2}}\right)^2}$$

$$V_{rms} = 76.40 \text{ V}$$

### b) RMS Current:

We know that,

$$I_{rms} = \sqrt{(8)^2 + \left(\frac{50}{\sqrt{2}}\right)^2 + \left(\frac{6}{\sqrt{2}}\right)^2 + \left(\frac{10}{\sqrt{2}}\right)^2}$$

$$I_{rms} = 37.17 \text{ A}$$

$$\mathbf{v(t)} = 5 + 100 \cos(314t) + 6 \cos(2(314)t + 15^\circ) + 40 \cos(3(314)t + 30^\circ)$$
$$\mathbf{i(t)} = 8 + 50 \cos(314t + 15^\circ) + 6 \cos(2(314)t + 30^\circ) + 10 \cos(3(314)t + 45^\circ)$$

### c) THD:

We have the formula,

$$THD = \sqrt{\frac{I_{rms}^2 - I_{1,rms}^2}{I_{1,rms}^2}}$$
$$THD = \sqrt{\frac{(37.17)^2 - \left(\frac{50}{\sqrt{2}}\right)^2}{\left(\frac{50}{\sqrt{2}}\right)^2}}$$
$$THD = 0.3244 = 32.44\%$$

## Question 2:

A non-linear load is supplied by a voltage,

$$V(t) = 300 \cos(2\pi 50t)$$

The resulting non-linear current is given as,

$$i(t) = 10 + 70 \cos(2\pi 50t + 20^\circ) + 40 \cos(6\pi 50t + 15^\circ) + 30 \cos(8\pi 50t + 25^\circ)$$

Find,

- a) Power absorbed by load.
- b) Power factor of load.
- c) THD of load current.



$$\mathbf{v(t)} = 300 \text{ Cos } (2\pi 50t)$$

$$\mathbf{i(t)} = 10 + 70 \text{ Cos } (2\pi 50t + 20^\circ) + 40 \text{ Cos } (6\pi 50t + 15^\circ) + 30 \text{ Cos } (8\pi 50t + 25^\circ)$$

## a) Power Absorbed by Load:

To find the power absorbed by load, we have the formula,

$$P = V_0 I_0 + \sum V_{rms} I_{rms} \text{ Cos } (\theta - \varphi)$$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$P = (0)(10) + \left(\frac{300}{\sqrt{2}}\right) \left(\frac{70}{\sqrt{2}}\right) \text{ cos } (0 - 20) + \left(\frac{0}{\sqrt{2}}\right) \left(\frac{40}{\sqrt{2}}\right) + \left(\frac{0}{\sqrt{2}}\right) \left(\frac{30}{\sqrt{2}}\right)$$

$$P = 9.86 \text{ kW}$$

## b) Power Factor:

We know that,

$$PF = \frac{P}{S} = \frac{P}{V_{in (rms)} I_{in (rms)}}$$

where,

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{300}{\sqrt{2}} = 212.13 \text{ V}$$



$$\mathbf{v(t)} = 300 \text{ Cos } (2\pi 50t)$$

$$\mathbf{i(t)} = 10 + 70 \text{ Cos } (2\pi 50t + 20^\circ) + 40 \text{ Cos } (6\pi 50t + 15^\circ) + 30 \text{ Cos } (8\pi 50t + 25^\circ)$$

and,

$$I_{rms} = \sqrt{(10)^2 + \left(\frac{70}{\sqrt{2}}\right)^2 + \left(\frac{40}{\sqrt{2}}\right)^2 + \left(\frac{30}{\sqrt{2}}\right)^2} = 61.64 \text{ A}$$

So,

$$PF = \frac{9866}{212.13 \times 61.64} = 0.75$$

### c) THD of Load Current:

For THD, we have the formula,

$$THD = \sqrt{\frac{I_{rms}^2 - I_{1,rms}^2}{I_{1,rms}^2}} = \sqrt{\frac{(61.64)^2 - \left(\frac{70}{\sqrt{2}}\right)^2}{\left(\frac{70}{\sqrt{2}}\right)^2}}$$

$$THD = 0.7421 = 74.21\%$$

### Question 3:

The voltage across a  $10\Omega$  resistor is

$$v(t) = 170 \sin(377t)$$

Determine,

- a) Instantaneous power.
- b) Average power.
- c) Peak power.



$$\mathbf{v(t)} = 170 \text{ Sin}(377t)$$

## a) Instantaneous Power:

We have the formulas for instantaneous power,

$$p(t) = v(t) i(t)$$

where,

$$i(t) = \frac{v(t)}{R}$$
$$i(t) = \frac{170 \text{ Sin}(377t)}{10} = 17 \text{ Sin}(377t)$$

So,

$$p(t) = 170 \text{ Sin}(377t) \times 17 \text{ Sin}(377t)$$
$$p(t) = 2890 \text{ Sin}^2(377t) \text{ W}$$

## b) Average Power:

For average power, we have the formula,

$$P = \frac{1}{T} \int_0^T p(t) dt$$





$$P = \frac{1}{2\pi} \int_0^{2\pi} 2890 \sin^2(377t) dt$$

$$P = \frac{2890}{2\pi} \int_0^{2\pi} \frac{1 - \cos 2(377)t}{2} dt$$

$$P = \frac{2890}{4\pi} \int_0^{2\pi} 1 - \cos (754)t dt$$

$$P = \frac{2890}{4\pi} \left[ t - \frac{\sin 754t}{754} \right]$$

$$P = \frac{2890}{4\pi} \left[ (2\pi - 0) - \left( \frac{\sin 754 * 2\pi}{754} - \frac{\sin 754 * 0}{754} \right) \right]$$

$$P = \frac{2890}{4\pi} [6.27] = 1444.74 W$$

$$\sin^2 t = \frac{1 - \cos 2t}{2}$$

### c) Peak Power:

From the instantaneous power, we have

$$\text{Peak Power} = 2890 W$$

## Question 4:

The voltage and current of a circuit is given by,

$$v(t) = 3 + 5 \cos(2\pi 60t + 15^\circ) + 2 \cos(4\pi 60t)$$

$$i(t) = 2 + 7 \cos(2\pi 60t + 45^\circ) + 3 \cos(6\pi 60t + 25^\circ)$$

Find,

- RMS voltage and current.
- Power absorbed by the circuit.
- Power factor.

$$\mathbf{v(t)} = 3 + 5 \cos(2\pi 60t + 15^\circ) + 2 \cos(4\pi 60t)$$

$$\mathbf{i(t)} = 2 + 7 \cos(2\pi 60t + 45^\circ) + 3 \cos(6\pi 60t + 25^\circ)$$

### a) RMS Voltage and Current:

The RMS voltage and current is given as,

$$V_{rms} = \sqrt{(3)^2 + \left(\frac{5}{\sqrt{2}}\right)^2 + \left(\frac{2}{\sqrt{2}}\right)^2} = 4.85 \text{ V}$$

$$I_{rms} = \sqrt{(2)^2 + \left(\frac{7}{\sqrt{2}}\right)^2 + \left(\frac{3}{\sqrt{2}}\right)^2} = 5.74 \text{ A}$$

### b) Power Absorbed by Load:

$$P = V_0 I_0 + \sum V_{rms} I_{rms} \cos(\theta - \varphi)$$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$P = (3)(2) + \left(\frac{5}{\sqrt{2}}\right)\left(\frac{7}{\sqrt{2}}\right)\cos(15 - 45) + \left(\frac{2}{\sqrt{2}}\right)(0) + (0)\left(\frac{3}{\sqrt{2}}\right)$$

$$P = 21.15 \text{ W}$$

### c) Power Factor:

We know that PF is give as,

$$PF = \frac{P}{S} = \frac{P}{V_{in (rms)} I_{in (rms)}}$$

$$PF = \frac{21.15}{4.85 \times 5.74}$$

$$PF = 0.7597$$

$$V_{rms} = 4.85 V$$
$$I_{rms} = 5.74 A$$