

Question 1:

For a half wave rectifier, the source voltage is 120 V-RMS at 60

Hz. The load resistance is 5 Ω . Find,

- Average load current.
- Average power absorbed by load.
- Power factor.

a) Average Load Current:

We know that,

$$\begin{aligned}I_o (avg) &= \frac{V_o (avg)}{R} \\ \therefore V_o (avg) &= \frac{V_m}{\pi} \\ I_o (avg) &= \frac{V_m}{\pi R} \\ I_o (avg) &= \frac{V_{rms} \times \sqrt{2}}{\pi R} = \frac{120 \times \sqrt{2}}{\pi \times 5} = 10.8 \text{ A}\end{aligned}$$

b) Average Power Absorbed by Load:

We have,

$$P_{out} = \frac{V_o^2 (rms)}{R}$$

where,

$$V_o (rms) = \frac{V_m}{2} = \frac{120 \times \sqrt{2}}{2} = 84.9 \text{ V}$$

$$P_{out} = \frac{(84.9)^2}{5} = 1441 \text{ W}$$

c) Power Factor:

We have,

$$PF = \frac{P}{S} = \frac{P}{V_{in(rms)} I_{in(rms)}}$$

for $I_{in(rms)}$,

$$P_{out} = I_{(rms)}^2 \times R$$
$$I_{in(rms)} = \sqrt{\frac{P_{out}}{R}} = \sqrt{\frac{1441}{5}} = 16.9 \text{ A}$$

So,

$$PF = \frac{1441}{120 \times 16.97} = 0.7$$

Question 2:

A half wave rectifier is supplied with a voltage of 600 V-RMS at a frequency of 50 Hz. The load resistance is 50 Ω . Find,

- Average load current.
- Power absorbed by load
- Apparent power supplied by source.
- Power factor.

a) Average Load Current:

We know that,

$$I_o (avg) = \frac{V_o (avg)}{R}$$

$$I_o (avg) = \frac{V_m}{\pi R}$$

$$I_o (avg) = \frac{V_{rms} \times \sqrt{2}}{\pi R} = \frac{600 \times \sqrt{2}}{\pi \times 50} = 5.4 \text{ A}$$

b) Power Absorbed by Load:

$$P_{out} = I_o^2 (rms) \times R$$

where,

$$I_o (rms) = \frac{V_o (rms)}{R} = \frac{V_m}{2R} = \frac{600 \times \sqrt{2}}{2 \times 50} = 8.4 \text{ A}$$

So,

$$P_{out} = (8.4)^2 \times 50 = 3600 \text{ W}$$

c) Apparent Power Supplied by Source:

We have,

$$S = V_{in (rms)} \times I_{in (rms)}$$

$$S = 600 \times 8.4$$

$$S = 5088 \text{ VA}$$

d) Power Factor:

$$PF = \frac{P}{S}$$

$$PF = \frac{3600}{5088}$$

$$PF = 0.7$$

Question 3:

For a half wave rectifier with RL load, $V_m=100 \text{ V}$, $R=100 \Omega$,

$L=0.1\text{H}$ and $\beta=3.5$, $\omega=377$. Find,

- a) Current expression.
- b) Average current.
- c) RMS current.
- d) Power absorbed by load.
- e) Power factor.

a) Current Expression:

The current expression is given as,

$$i(t) = \frac{V_m}{\sqrt{R^2 + (L\omega)^2}} \sin(\omega t - \theta) + A e^{-\omega t / \frac{L\omega}{R}}$$

and,

$$\theta = \tan^{-1} \frac{L\omega}{R}$$

$$\theta = \tan^{-1} \frac{0.1 \times 377}{100} = 20.6^\circ = 0.36 \text{ rad}$$

and,

$$\sqrt{R^2 + (L\omega)^2} = \sqrt{100^2 + (0.1 \times 377)^2} = 106.87$$

and,

$$A = \frac{V_m \sin \theta}{\sqrt{R^2 + (L\omega)^2}}$$

So, we have

$$i(\omega t) = \frac{100}{106.87} \sin(\omega t - 0.36) + \frac{100 \sin(0.36)}{106.87} e^{-\omega t / \frac{L\omega}{R}}$$

$$i(\omega t) = 0.93 \sin(\omega t - 0.36) + 0.33 e^{-\omega t / \frac{L\omega}{R}} \quad \text{For } 0 \leq \omega t \leq 3.5$$

$$i(\omega t) = 0 \quad \text{For } 3.5 < \omega t \leq 2\pi$$

b) Average Current:

$$i(\omega t) = \frac{1}{T} \int_0^T i(\omega t) d\omega t$$

$$i(\omega t) = \frac{1}{2\pi} \left[\int_0^{3.5} i(\omega t) d\omega t + \int_{3.5}^{2\pi} i(\omega t) d\omega t \right]$$

$$i(\omega t) = \frac{1}{2\pi} \int_0^{3.5} \left(0.936 \sin(\omega t - 0.36) + 0.33 e^{-\omega t / \frac{L\omega}{R}} \right) d\omega t$$