

Exercise no.4

Question 1:

A controlled half wave rectifier has an AC source of 340 V (peak) at 60 Hz. The load resistance is $R = 60 \Omega$. Determine,

- Delay angle such that the average load current is 1 A.
- Find power absorbed by load.
- Power factor.

Solution:

a) We have,

$$V_{o,avg} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$
$$\Rightarrow \cos \alpha = \frac{V_{o,avg} \times 2\pi}{V_m} - 1$$

and,

$$V_{o,avg} = I_{o,avg} \times R$$
$$= 1 \times 60$$
$$= 60V$$

So,

$$\cos \alpha = \frac{60 \times 2\pi}{340} - 1$$
$$\alpha = \cos^{-1} \left(\frac{60 \times 2\pi}{340} - 1 \right)$$
$$\alpha = 1.46 \text{ rad}$$

b) Power Absorbed by load.

We have,
$$P = \frac{V_{o,rms}^2}{R}$$

and,

$$V_{o,rms} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}}$$

$$V_{o,rms} = \frac{340}{2} \sqrt{1 - \frac{1.46}{\pi} + \frac{\sin(2 \times 1.46)}{2\pi}}$$

$$V_{o,rms} = 128.3 \text{ V}$$

So,

$$P = \frac{(128.3)^2}{60} = 274.30 \text{ W.}$$

c) Power factor

$$PF = \frac{P}{S} = \frac{P}{V_{in,rms} \times I_{in,rms}}$$

$$PF = \frac{P}{\frac{V_m}{\sqrt{2}} \times \frac{V_{o,rms}}{R}}$$

$$PF = \frac{274.30}{\frac{340}{\sqrt{2}} \times \frac{128.30}{60}}$$

$$PF = 0.536$$

Question 2:

A single-phase full wave rectifier with resistive load of 20Ω and AC source of 230 V-RMS. Find the following,

a) Average, peak and RMS currents in load and each diode.

b) Peak reverse voltage across each diode.

Solution:

a) Average, Peak and RMS Currents:

Average Current (Load):


We know that,

$$i_o (avg) = \frac{V_o (avg)}{R} = \frac{2V_m}{\pi R}$$
$$i_o (avg) = \frac{2 \times 230 \times \sqrt{2}}{3.14 \times 20} = 10.35 \text{ A}$$

Average Current (Diode):

We have,
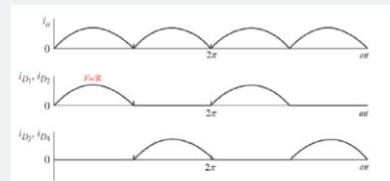
$$i_D (avg) = \frac{i_o (avg)}{2}$$
$$i_D (avg) = \frac{10.35}{2} = 5.17 \text{ A}$$



Peak Current (Load and Diode):

The peak current in load and diode is same for full wave rectifier, we have

$$i_o (peak) = i_D (peak) = \frac{V_m}{R}$$
$$i_o (peak) = i_D (peak) = \frac{230 \times \sqrt{2}}{20} = 16.26 \text{ A}$$

RMS Current (Load):

For RMS load current we have,

$$i_o (RMS) = \frac{V_o (RMS)}{R} = \frac{V_m}{\sqrt{2}R} = \frac{230 \times \sqrt{2}}{\sqrt{2} \times 20} = 11.50 \text{ A}$$

RMS Current (Diode):

For RMS diode current we have,

$$i_D (RMS) = \frac{i_o (RMS)}{\sqrt{2}} = \frac{V_m}{2R} = \frac{230 \times \sqrt{2}}{2 \times 20} = 8.13 \text{ A}$$

b) Peak Reverse Voltage:

When the diode is reverse biased the voltage across it is equal to the supply voltage, so we can say that,

$$\begin{aligned}V_D &= V_M = V_{RMS} \times \sqrt{2} \\V_D &= 230 \times \sqrt{2} \\V_D &= 325.26 \text{ V}\end{aligned}$$

Question 3:

A single-phase full wave rectifier with an AC source of $200 \sin(377t)$ and resistive load of 20Ω . Find,

- Average current in load and each diode.
- Peak reverse voltage across each diode.
- Power factor.

Solution:

a) Average Current in Load and Diode:

Average Current (Load):

We have,

$$\begin{aligned}i_{0(avg)} &= \frac{V_{0(avg)}}{R} \\i_{0(avg)} &= \frac{2V_m}{\pi R} = \frac{2 \times 200}{3.14 \times 20} = 6.36 \text{ A}\end{aligned}$$

Average Current (Diode):

We have,

$$\begin{aligned}i_{0(avg)} &= \frac{i_{0(avg)}}{2} \\i_{0(avg)} &= \frac{6.36}{2} = 3.18 \text{ A}\end{aligned}$$

b) Peak Reverse Voltage across Diode:

We know that it is equal to the supply voltage,

$$V_{d (peak)} = V_m = 200 V$$

c) Power Factor:

We have the power factor formula,

$$PF = \frac{P}{S} = \frac{i_o^2 (rms) \times R}{V_{in (rms)} \times i_{in (rms)}}$$

Where,

$$i_o (rms) = \frac{V_o (rms)}{R} = \frac{V_m}{\sqrt{2} \times R} = \frac{200}{\sqrt{2} \times 20} = 7.07 A$$

So,

$$PF = \frac{(7.07)^2 \times 20}{\frac{200}{\sqrt{2}} \times 7.07} = 0.99$$

Question 4:

A single-phase full wave rectifier has a 60 Hz AC source with minimum voltage of 100 V. It is to supply a load that requires a DC voltage of 100 V and will draw 0.4 A current. Find the value of filter capacitance required to limit the peak-to-peak output voltage ripples to 1% of DC output.

Solution:

To find the value of capacitance we have,

$$\Delta V_o = \frac{V_m}{2fRC}$$

For R,

$$V = IR$$
$$R = \frac{V}{I} = \frac{100}{0.4} = 250 \Omega$$

So,

$$C = \frac{V_m}{2fR\Delta V_o}$$
$$C = \frac{100}{2 \times 60 \times 250 \times (0.01)(100)}$$
$$C = 3333 \mu F$$