

Exercise no.6 with solution

Question 1:

The input and output of a buck converter is 6 V and 1.5 V, respectively. The resistance is 3 Ω , inductance is 5 μH , capacitance is 10 μF and the switching frequency is 400k Hz. Find,

- Duty ratio.
- Average and peak inductor current.
- Average source current.
- Peak and average diode current.

a) Duty Ratio:

For the buck converter we have,

$$D = \frac{V_o}{V_s} = \frac{1.5}{6} = 0.25$$

b) Average and Peak Inductor Current:

Average Inductor Current:

$$i_{L(avg)} = \frac{V_o}{R} = \frac{1.5}{3} = 0.5 A$$

Peak Inductor Current:

$$i_{L(max)} = V_o \times \left[\frac{1}{R} + \frac{1-D}{2Lf} \right]$$
$$i_{L(max)} = 1.5 \times \left[\frac{1}{3} + \frac{1-0.25}{2 \times 5 \times 10^{-6} \times 400 \times 10^3} \right] = 0.78 A$$

c) Average Source Current:

Let us assume ideal converter,

Input Power = Output Power

$$V_{in} \times i_{in} = \frac{V_o^2}{R}$$

$$i_{in} = \frac{V_o^2}{R \times V_{in}}$$

$$i_{in} = \frac{(1.5)^2}{3 \times 6} = 0.12 A$$

d) Peak and Average Diode Current:

The average diode current is given as,

$$i_{D(avg)} = i_{L(avg)} \times [1 - D]$$

$$i_{D(avg)} = 0.5 \times (1 - 0.25) = 0.37 \text{ A}$$

The maximum diode current is given as,

$$i_{D(max)} = i_{L(max)} = 0.78 \text{ A}$$

Question 2:

An input of 100 V is applied to buck converter and the output is 50 V. The switching frequency is 100 kHz and the output power to load resistance is 165 W. Determine,

- Duty ratio.
- Value of inductance to limit the maximum inductor current to 6.25 A.
- The minimum inductor current.

a) Duty Ratio:

For the buck converter we have,

$$D = \frac{V_0}{V_s} = \frac{50}{100} = 0.5$$

b) Value of Inductor:

Average Inductor Current:

$$i_{L(max)} = V_0 \times \left[\frac{1}{R} + \frac{1-D}{2Lf} \right]$$
$$i_{L(max)} = \left[\frac{V_0}{R} + \frac{V_0(1-D)}{2Lf} \right]$$

$$i_{L(max)} - \frac{V_0}{R} = \frac{V_0(1-D)}{2Lf}$$

$$L = \frac{V_0(1-D)}{2f \left(i_{L(max)} - \frac{V_0}{R} \right)}$$

For R,

$$P_{out} = \frac{V_o^2}{R}$$

$$R = \frac{V_o^2}{P_{out}} = \frac{(50)^2}{165} = 15 \Omega$$

So,

$$L = \frac{50(1-0.5)}{2 \times 100 \times 10^3 \left(6.25 - \frac{50}{15} \right)} = 42.8 \mu H$$

c) Minimum Inductor Current:

We have the formula,

$$i_{L(min)} = V_0 \times \left[\frac{1}{R} - \frac{1-D}{2Lf} \right]$$

$$i_{L(min)} = 50 \times \left[\frac{1}{15} - \frac{1-0.5}{2 \times 42.8 \times 10^{-6} \times 100 \times 10^3} \right]$$

$$i_{L(min)} = 0.412 A$$

