

Exercise No.5 with solution

Question 1:

The controlled full wave rectifier has  $18 \Omega$  resistive load and a 120 V-RMS 60 Hz source. The delay angle is 45 degrees. Find,

- a) Average load current.
- b) RMS load current.
- c) RMS source current.
- d) Power factor.

**a) Average Load Current:**

The average load current is given as,

$$i_o (avg) = \frac{V_o (avg)}{R} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$
$$i_o (avg) = \frac{120 \times \sqrt{2}}{3.14 \times 18} (1 + \cos 45^\circ) = 5.12 A$$

**b) RMS Load Current:**

The RMS load current is given as,

$$i_o (rms) = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}}$$
$$i_o (rms) = \frac{120 \times \sqrt{2}}{18} \sqrt{\frac{1}{2} - \frac{0.785}{2\pi} + \frac{\sin 2 \times 0.785}{4\pi}} \quad \alpha = 45^\circ = 0.785 \text{ rad}$$
$$i_o (rms) = 6.35 A$$

**c) RMS Source Current:**

We know that input and output RMS currents are same,

$$i_{in} (rms) = i_o (rms) = 6.35 A$$

**d) Power Factor:**

We have,

$$PF = \frac{P}{S} = \frac{i_o^2 (rms) \times R}{V_{in} (rms) \times i_{in} (rms)}$$
$$PF = \frac{(6.35)^2 \times 18}{120 \times 6.35}$$
$$PF = 0.95$$

\*\*\*\*\*

Question 2:

A load of  $50 \Omega$  is connected to an AC source of 60 Hz, 230 V-RMS. Full wave-controlled rectifier has a delay angle of 45 degrees. Calculate the average load current, power absorbed by the load, and the source VA.

For Average Load Current, we have

$$V_o (avg) = \frac{V_m}{\pi} (1 + \cos \alpha)$$
$$V_o (avg) = \frac{230 \times \sqrt{2}}{3.14} (1 + \cos 45) = 176.8 V$$

So,

$$i_o (avg) = \frac{V_o (avg)}{R}$$
$$i_o (avg) = \frac{176.8}{50} = 3.53 A$$

For Power Absorbed by Load, we have

$$P = i_o^2 (rms) \times R$$

where,

$$i_o (rms) = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}}$$
$$i_o (rms) = \frac{230 \times \sqrt{2}}{50} \sqrt{\frac{1}{2} - \frac{0.785}{2\pi} + \frac{\sin 2 \times 0.785}{4\pi}} = 3.99 A$$

So, we have the power absorbed,

$$P = (3.99)^2 \times 50 = 798.11 W$$

For Source VA, we have,

$$S = V_{in} (rms) \times i_{in} (rms)$$
$$S = 230 \times 3.99$$
$$S = 917.7 VA$$

\*\*\*\*\*