

Exercise No 08 with solution.

Question 1:

A square wave inverter has a DC source of 100 V, and the output frequency is 50 Hz. The RL series load of 10 ohm and 30 mH is connected to the output.

Find,

- Expression of the load current.
- RMS load current.
- Average source current.

a) Expression of the Load Current:

As we know that the expression for load current is given as,

$$i_o(t) = \frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-\frac{t}{\tau}} \quad \text{for } 0 \leq t \leq \frac{T}{2}$$
$$i_o(t) = \frac{-V_{in}}{R} + \left(I_{max} + \frac{V_{in}}{R} \right) e^{-\frac{(t-T/2)}{\tau}} \quad \text{for } \frac{T}{2} \leq t \leq T$$

Where,

$$T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ sec}$$

$$\tau = \frac{L}{R} = \frac{30 \times 10^{-3}}{10} = 0.003$$

$$\frac{T}{2\tau} = \frac{0.02}{2 \times 0.003} = 3.33$$

$$I_{max} = -I_{min} = \frac{V_{in}}{R} \left(\frac{1 - e^{-\frac{T}{2\tau}}}{1 + e^{-\frac{T}{2\tau}}} \right) = \frac{100}{10} \left(\frac{1 - e^{-3.33}}{1 + e^{-3.33}} \right) = 9.30A$$

Now,

$$i_o(t) = \frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-\frac{t}{\tau}}$$

$$i_o(t) = \frac{100}{10} + \left(-9.30 - \frac{100}{10} \right) e^{-\frac{t}{0.003}}$$

$$i_o(t) = 10 - 19.3e^{-\frac{t}{0.003}} \quad \text{for } 0 \leq t \leq \frac{1}{100}$$

and,

$$i_o(t) = \frac{-V_{in}}{R} + \left(I_{max} + \frac{V_{in}}{R} \right) e^{-\frac{(t-T/2)}{\tau}}$$

$$i_o(t) = \frac{-100}{10} + \left(9.30 + \frac{100}{10} \right) e^{-\frac{(t-0.02/2)}{0.003}}$$

$$i_o(t) = -10 + 19.3 e^{-\frac{(t-0.01)}{0.003}} \quad \text{for } \frac{1}{100} \leq t \leq \frac{1}{50}$$

$$I_{max} = -I_{min} = \frac{V_{in}}{R} \left(\frac{1 - e^{-\frac{T}{2\tau}}}{1 + e^{-\frac{T}{2\tau}}} \right) = \frac{100}{10} \left(\frac{1 - e^{-3.33}}{1 + e^{-3.33}} \right) = 9.30A$$

Now,

$$i_o(t) = \frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-\frac{t}{\tau}}$$

$$i_o(t) = \frac{100}{10} + \left(-9.30 - \frac{100}{10} \right) e^{-\frac{t}{0.003}}$$

$$i_o(t) = 10 - 19.3e^{-\frac{t}{0.003}} \quad \text{for } 0 \leq t \leq \frac{1}{100}$$

and,

$$i_o(t) = \frac{-V_{in}}{R} + \left(I_{max} + \frac{V_{in}}{R} \right) e^{-\frac{(t-T/2)}{\tau}}$$

$$i_o(t) = \frac{-100}{10} + \left(9.30 + \frac{100}{10} \right) e^{-\frac{(t-0.02/2)}{0.003}}$$

$$i_o(t) = -10 + 19.3 e^{-\frac{(t-0.01)}{0.003}} \quad \text{for } \frac{1}{100} \leq t \leq \frac{1}{50}$$

b) RMS Load Current:

For RMS value, we have the formula,

$$I_{RMS} = \sqrt{\frac{1}{T} \left(\int_0^T [i_o(t)]^2 dt \right)}$$

$$I_{RMS} = \sqrt{\frac{2}{T} \left(\int_0^{T/2} \left[\frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-\frac{t}{\tau}} \right]^2 dt \right)}$$

$$I_{RMS} = \sqrt{\frac{2}{0.02} \left(\int_0^{0.01} \left[10 - 19.3 e^{-\frac{t}{0.003}} \right]^2 dt \right)}$$

$$I_{RMS} = \sqrt{100 \times 0.44133}$$

$$I_{RMS} = 6.643 \text{ A}$$

c) Average Source Current:

As we know that,

$$P = VI$$
$$I_{in} = \frac{P_{in}}{V_{in}}$$

Where,

$$P_{in} = I_{rms}^2 \times R$$

$$P_{in} = (6.643)^2 \times 10$$

$$P_{in} = 441.33 \text{ W}$$

and,

$$I_{in} = \frac{441.33}{100} = 4.41 \text{ A}$$

Question 2:

A square-wave inverter has a dc input of 150 V and supplies a series RL load with $R=20\Omega$ and $L=40$ mH. The output frequency is 60 Hz.

- a) Determine an expression for steady state load current.
- b) Determine the peak current in each switch component.
- c) What is the maximum voltage across each switch?

Assume ideal components

Solution:

$$T = \frac{1}{f} = \frac{1}{60} = 0.0167 \text{ s}$$

$$\tau = \frac{L}{R} = \frac{0.040}{20} = 0.002$$

$$\frac{T}{2\tau} = \frac{0.0167}{2 \cdot 0.002} = 4.175$$

Part (a):

$$I_{max} = -I_{min} = \frac{V_{in}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right) = \frac{150}{20} \left(\frac{1 - e^{-4.175}}{1 + e^{-4.175}} \right) = 7.27 \text{ A}$$

$$\begin{aligned} i_o(t) &= \frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-t/\tau} = 7.5 + (-7.27 - 7.5)e^{-t/0.002} \\ &= 7.5 - 14.77e^{-t/0.002} \quad 0 \leq t \leq \frac{1}{120} \end{aligned}$$

$$\begin{aligned} i_o(t) &= \frac{-V_{in}}{R} + \left(I_{max} + \frac{V_{in}}{R} \right) e^{-(t-\frac{T}{2})/\tau} = -7.5 + (7.27 + 7.5)e^{-(t-0.0084)/0.002} \\ &= -7.5 + 14.77e^{-(t-0.0084)/0.002} \quad \frac{1}{120} \leq t \leq \frac{1}{60} \end{aligned}$$

Part (c): the peak current in each switch component is equal to the peak output current,

$$I_{max} = \frac{V_{in}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right) = \frac{150}{20} \left(\frac{1 - e^{-4.175}}{1 + e^{-4.175}} \right) = 7.27 \text{ A}$$

Part (d):

The maximum voltage across each switch is $V_{in} = 150 \text{ V}$