

Assignment No. 2 Solution.

Q# 01

$$V_{rms} = 400 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$R_L = 100 \Omega$$

$$C = 350 \mu\text{F}$$

$$\alpha = 0.49 \text{ rad}$$

a) $\Delta V = ?$

Sol:.

$$\Delta V_o = V_m (1 - \sin \alpha)$$

$$\Delta V_o = 400 \times \sqrt{2} (1 - \sin(0.49))$$

$$\Delta V_o = 299.768 \text{ V}$$

b)
$$\Delta V_o = \frac{V_m}{2fRC}$$

$$\Rightarrow C = \frac{V_m}{2fR\Delta V_o}$$

$$C = \frac{400 \times \sqrt{2}}{2 \times 50 \times 100 \times 1.5}$$

$$C = 0.037 \approx 37 \times 10^{-3} \text{ F}$$

Q#03

$$V_{\text{rms}} = 230 \text{ V}$$

$$\alpha = 25^\circ$$

$$R_L = 250 \Omega$$

Q) $I_{\text{avg}} = ?$

$$I_{\text{avg}} = \frac{V_{\text{avg}}}{R}$$

So for V_{avg} .

$$V_{\text{avg}} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$= \frac{230 \sqrt{2}}{3.14} (1 + \cos 25^\circ)$$

$$= 196.78 \text{ V.}$$

So.

$$I_{avg} = \frac{196.78}{250} = 0.787 A.$$

(b) P_{abs}

$$P_{abs} = I_{o,rms}^2 \times R$$

$$I_{o,rms} = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}}$$

$$= \frac{230 \times \sqrt{2}}{250} \sqrt{0.5 - \frac{0.436}{2 \times 3.14} + \frac{\sin 2(0.436)}{4 \times 3.14}}$$

$$= 1.3 \times 0.60$$

$$= 0.78 A.$$

$$P = (0.78)^2 \times 250 = 152.1 W.$$

(c) Source VA.

$$S = V_{in,rms} \times I_{in,rms}$$

$$S = 230 \times 0.78 = 179.4 VA$$

$$(d) PF = \frac{P}{S} = \frac{152.1}{179.4} = 0.84$$

a4.

$$V_{rms} = 230 V$$

$$R = 150 \Omega$$

④ I_{peak} , i_{avg} & rms i .

$$i_{avg} = \frac{V_{o,avg}}{R} = \frac{2V_m}{\pi R} = \frac{2 \times 230 \times \sqrt{2}}{\pi \times 150}$$
$$= \frac{650.44}{471} = 1.38 A$$

$$i_{d,avg} = \frac{i_{avg}}{2} = \frac{1.38}{2} = 0.69 A$$

$$i_{o,peak} = \frac{V_m}{R} = \frac{230 \times \sqrt{2}}{150} = 2.16 A$$

$$i_{d,peak} = i_{o,peak} = 2.16 A$$

$$i_{o,rms} = \frac{V_{o,rms}}{R} = \frac{V_m}{\sqrt{2} \times R} = \frac{230 \times \sqrt{2}}{\sqrt{2} \times 150}$$
$$= 1.53 A$$

$$i_{d,rms} = \frac{i_{o,rms}}{\sqrt{2}} = 1.084 A$$

③ Peak reverse Voltage

$$V_d = V_m = 230 \times \sqrt{2} = 325.22 \text{ V}$$

Question 2 solution

From the parameters given,

$$V_m = 120\sqrt{2} = 169.7 \text{ V}$$

$$\omega RC = (2\pi 60)(500)(10)^{-6} = 18.85$$

The angle θ is

$$\theta = -\tan^{-1}(18.85) + \pi = 1.62 \text{ rad} = 93^\circ$$

$$V_m \sin \theta = 169.5 \text{ V}$$

The angle α is

$$\sin(1.62)e^{-(\pi + \alpha - 1.62)/18.85} - \sin \alpha = 0$$

$$\alpha = 1.06 \text{ rad} = 60.6^\circ$$

(a) Peak-to-peak output voltage

$$\Delta V_o = V_m(1 - \sin \alpha) = 169.7[1 - \sin(1.06)] = 22 \text{ V}$$

(b) With the ripple limited to 1 percent, the output voltage will be held close to V_m and the approximation of Eq. (4-13) applies.

$$\frac{\Delta V_o}{V_m} = 0.01 \approx \frac{1}{2fRC}$$

Solving for C ,

$$C \approx \frac{1}{2fR(\Delta V_o/V_m)} = \frac{1}{(2)(60)(500)(0.01)} = 1670 \text{ } \mu\text{F}$$