



Aalto University
School of Electrical
Engineering

ELEC-E3540 Digital Microelectronics II

Writing synthesizable VHDL

Vishnu Unnikrishnan
vishnu.unnikrishnan@aalto.fi

25.03.2019

Logic synthesis

- **Logic synthesis** = the process of turning a behavioral model of a digital circuit (i.e. VHDL) into a design implementation in terms of logic gates (AND, OR, ...)
- The circuit manufacturer provides the library of “standard cells”
 - each standard cell implements an elementary logic function
 - each cell is usually available in a multitude of driving strengths
- Synthesis is a highly automated task!

What is synthesizable VHDL?

- During the 6 exercises, you are learning the basics of VHDL coding and simulation
- However, not all VHDL constructs can be understood by the synthesis tool
- In addition, there are some “good practices” that will produce a better synthesis outcome

RTL

coding style


RTL coding style

- RTL (Register Transfer Level) is the standard design abstraction used to model synchronous digital circuits with hardware description languages (Verilog, VHDL)
- **Learning the RTL coding style is mandatory in order to pass this course!**
 - exercises 4-6 and the final assignment will **not** be accepted, unless they follow the RTL style
 - even though everything seems to work!

RTL coding style

- RTL = describe a digital design in terms of

 - registers (memory elements) and
- the flow/transformation of data between them (combinational logic)



- Only the registers have memory
- Only the registers are triggered by the clock signal
- Combinational logic only calculates outputs when inputs change
- FSM-like implementation


RTL coding style

- In simple words, RTL is all about this:

REGISTERS


VS

EVERYTHING ELSE

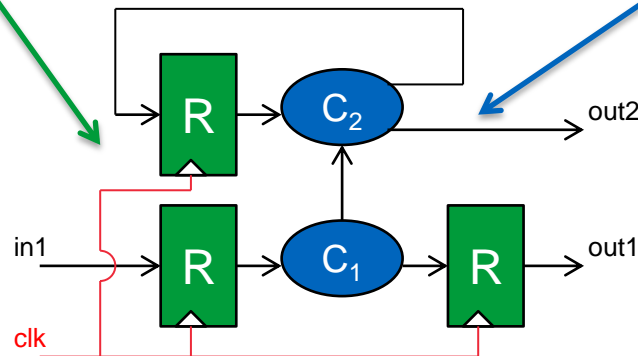

How to model a register

- Simple edge-triggered D flip-flop

 

- With a process:


```
DFF: process(clk)
begin
    if rising_edge(clk) then
        Q <= D;
    end if;
end process;
```

- Without a process (*concurrent signal assignment*):

```
Q <= D when rising_edge(clk);
```


How to model a register


- D flip-flop with *asynchronous* reset

 

```
DFF_arst: process(rst, clk)
begin
  if rst = '1' then
    Q <= (others => '0');
  elsif rising_edge(clk) then
    Q <= D;
  end if;
end process;
```

How to model a register


- D flip-flop with *synchronous* reset

 

```
DFF_srst: process(clk)
begin
    if rising_edge(clk) then
        if rst = '1' then
            Q <= (others => '0');
        else
            Q <= D;
        end if;
    end if;
end process;
```

How to model a register

 
- D flip-flop with synchronous write enable



```
DFF_en: process(clk)
begin
    if rising_edge(clk) then
        if en = '1' then
            Q <= D;
        end if;
    end if;
end process;
```

How to model a register

 
- The basic constructs shown in the previous slides can be combined to build more complex registers
- Example: D flip-flop with asynchronous reset and synchronous write enable



```
DFF_arst_en: process(rst, clk)
begin
    if rst = '1' then
        Q <= (others => '0');
    elsif rising_edge(clk) then
        if en = '1' then
            Q <= D;
        end if;
    end if;
end process;
```

How to model combinational logic

 - Typically with a process which is sensitive to **all input signals** to the logic block
- In VHDL-2008, reserved word “all” can be used to replace a complete sensitivity list



```
comb_logic: process(in1, in2, in3)
    -- optional declarations
begin
    -- your VHDL code
end process;
```


```
comb_logic: process(all)
    -- optional declarations
begin
    -- your VHDL code
end process;
```

How to model combinational logic

- **IMPORTANT: all outputs of a combinational logic block must be assigned some unique value, for every value of the inputs!**
- Otherwise the circuit has *memory* → it is no longer purely combinational
- Violation of this rule will result in “latch inferred” warnings during the elaboration phase of logic synthesis

How to model combinational logic

 - Example 1: output not assigned under certain conditions




out2 not assigned when in2 = '0'

```
comb_logic_wrong: process(all)
begin
  if in1 = '1' then
    out1 <= in2 and in3;
    out2 <= in2 or in3;
  else
    out1 <= in2 xor in3;
  end if;
end process;
```

How to model combinational logic

 - Example 1: output not assigned under certain conditions




Solution #1:
assign a value for out2 in all cases

```
comb_logic_correct1: process(all)
begin
  if in1 = '1' then
    out1 <= in2 and in3;
    out2 <= in2 or in3;
  else
    out1 <= in2 xor in3;
    out2 <= (others => '0');
  end if;
end process;
```


How to model combinational logic

 - Example 1: output not assigned under certain conditions




Solution #2:
initialize out2 before the if-statement

```
comb_logic_correct2: process(all)
begin
  out2 <= (others => '0');
  if in1 = '1' then
    out1 <= in2 and in3;
    out2 <= in2 or in3;
  else
    out1 <= in2 xor in3;
  end if;
end process;
```

How to model combinational logic

 - Example 2: incomplete conditional statement




not defined what happens when in1 = "11" →

```
comb_logic_wrong: process(all)
begin
  case in1 is
    when "00" =>
      out1 <= in2 + in3;
      out2 <= in2 * in3;
    when "01" =>
      out1 <= in2 - in3;
      out2 <= in2 & in3;
    when "10" =>
      out1 <= in2;
      out2 <= some_function(in2, in3);
  end case;
end process;
```

How to model combinational logic

 - Example 2: incomplete conditional statement



Solution: terminate conditional statements with else, when others to include all possible cases

```
comb_logic_correct: process(all)
begin
  case in1 is
    when "00" =>
      out1 <= in2 + in3;
      out2 <= in2 * in3;
    when "01" =>
      out1 <= in2 - in3;
      out2 <= in2 & in3;
    when "10" =>
      out1 <= in2;
      out2 <= some_function(in2, in3);
    when others =>
      out1 <= in2;
      out2 <= (others => '0');
  end case;
end process;
```

Other useful hints

Read the book!

- Before starting the final assignment work, it is strongly recommended that you read:
 1. P. J. Ashenden, **The designer's guide to VHDL**, *3rd ed.*
 - Chapter 21 - Design for synthesis
 2. H. Bhatnagar, **Advanced ASIC chip synthesis** (*PDF in MyCourses*)
 - Chapter 5 - Partitioning and coding styles

Think “hardware”!

- When writing VHDL, have always in mind what you want the synthesis tool to implement!
- If you have no idea how your VHDL is going to be implemented, most likely the synthesis tool has no idea as well :-)
- Remember: the synthesis tool is stupid (and the static verification tool is even more stupid)

Avoid unessential features

- The simpler your VHDL code
 - the smaller the area and power consumption
 - the easier your life
 - the better your VHDL will be understood by the synthesis tool
- Ideally, your VHDL code should achieve the desired functionality with the minimum possible complexity!

Variables vs signals

- Students are usually tempted to make extensive use of variables within processes
 - similarity with software-oriented programming languages
- **However, try not to abuse variables**
- Reason: variables are abstract, signals are real (i.e. physical wires in your chip)
- Using too many variables
 - is in contrast with the “think hardware” guideline given earlier
 - will cause troubles, because you don’t understand how they are mapped to a physical circuit

“After” statements

- Statements like **after**, **wait for** and similar are meaningless for the synthesis tool
 - don't waste your time with those
- VHDL should describe the ideal logic behavior of your circuit
 - timing is taken into account during synthesis and P&R
- P.S. = The simulation testbench must contain wait statements! This is not a problem, as the testbench will not be synthesized

Initial values

- Initial values (e.g. in signal declarations) are ignored by the synthesis tool
 - again, you can still use them in the simulation testbench
- If you want to be sure that your memory and/or registers are initialized to 0, you must include a RESET signal
 - either synchronous or asynchronous

Naming

- The synthesized netlist is written in VERILOG
- In your VHDL, avoid using names that are reserved words for VERILOG
 - examples: “input”, “output” can be used in VHDL, but they will cause problems in VERILOG
- As a general rule, use your common sense
 - avoid any potentially dangerous words :-)

Dealing with numbers

- Simple arithmetic operations are well supported by synthesis tools

- package `ieee.numeric_std`

- Correct way to implement an addition:

```
sum <= STD_LOGIC_VECTOR(UNSIGNED(a) + UNSIGNED(b));
```

- Correct way to address a memory cell:

```
sel      <= to_integer(UNSIGNED(addr));  
RAM_out <= RAM_array(sel);
```

- Don't implement e.g. the internal adder architecture by yourself! Let the synthesis tool do this for you

A couple of words on TCL

Tool Command Language

- Tool Command Language (TCL) is the scripting language used to control all tools needed for the digiflow
 - QuestaSim, Design Compiler, Formality, Encounter, PrimeTime
- Every operation performed through the GUI corresponds to one or many TCL commands
 - the inverse is not necessarily true :-)
- Worth learning at least the very basics of the language
 - if you want to learn more, use google!

Command invocation

- A TCL script consists of several command invocations:

```
command1 arg11 arg12 ... arg1N  
command2 arg21 arg22 ... arg2N  
...
```

- The list of valid command names and arguments can be found in each tool's text reference manual

Command substitution

- Square brackets [] allow to execute commands in a nested fashion
 - the command inside brackets is executed first, and its result is used as argument to another command
- Example (Design Compiler):

set_load 0.017 [all_outputs]



Variables

- Variable declaration:
`set varname varvalue`
- Variable substitution (i.e. using the variable's content):
`$varname`
`${varname}`
- All variables are manipulated as strings!
- Example:
`set loadvalue 0.017`
`set_load $loadvalue [all_outputs]`

Quotes

- Quotes are used to group many space-separated words into a single argument
 - for example, to create lists

- Two types of quotes used in TCL
 - double quotes " ": substitution **does** take place within them
 - curly braces { }: substitution does **not** take place within them

Quotes

- Example:

```
set var1 value1
```

```
command1 "$var1 [command2]"
```

```
command1 {$var1 [command2]}
```

- Assume that executing `command2` returns `value2`
 - the line with double quotes uses string `value1 value2` as first argument of `command1`
 - the line with curly braces uses string `$var1 [command2]` as first argument of `command1` (no substitution!)