

ONLINE EXAM

Question 1

In a Buck converter output voltage $U_o = 5$ V, supply voltage $U_d = 40$ V, output power $P_o = 5$ W, and switching frequency $f_s = 50$ KHz. Output filter components (L and C) are so large that output current of the converter is ideal dc. Harmonic currents of the supply voltage source are limited, and the switching frequency component can in maximum be 0,2 mA. What is the maximum allowed resonance frequency of the input filter?

Question 2

In a Flyback converter output voltage $U_o = 5$ V, supply voltage 12 V $\leq U_d \leq 24$ V, output power 6 W $\leq P_o \leq 60$ W, switching frequency $f_s = 200$ KHz, and $N_1:N_2 = 1$. Calculate the maximum value of the magnetizing inductance of the Flyback transformer so that the converter is always in the complete demagnetization area.

Question 3

In a Forward converter output voltage $U_o = 12$ V, supply voltage 210 V $\leq U_d \leq 325$ V, output power 15 W $\leq P_o \leq 50$ W and switching frequency $f_s = 50$ KHz. The transformer is built from ferrite 3C8 with ETD 34 core. Its volume is 7640 mm³, effective area $97,1$ mm² and the smallest surface area of the core is $A_{c,min} = 86,6$ mm². Copper filling factor is assumed to be 0,6 and saturation flux density at 100 °C is 0,32 T. Calculate the number of turns in the transformer when demagnetization winding $N_3 = N_1$. Remanence flux density can be assumed to be zero. Primary inductance of the transformer is 10 mH, calculate the needed airgap length.


Question 4

Efficiency is important in switched mode power supplies. One part of the losses are the switching losses of the power semiconductor devices. What kind of methods can be used to reduce the losses created by these switches in SMPS.

Question 5


What kind of methods can be used to implement current-mode control in SMPS? What are the advantages of current-mode control when compared to the voltage-mode control (PWM duty ratio control)?

Question 1

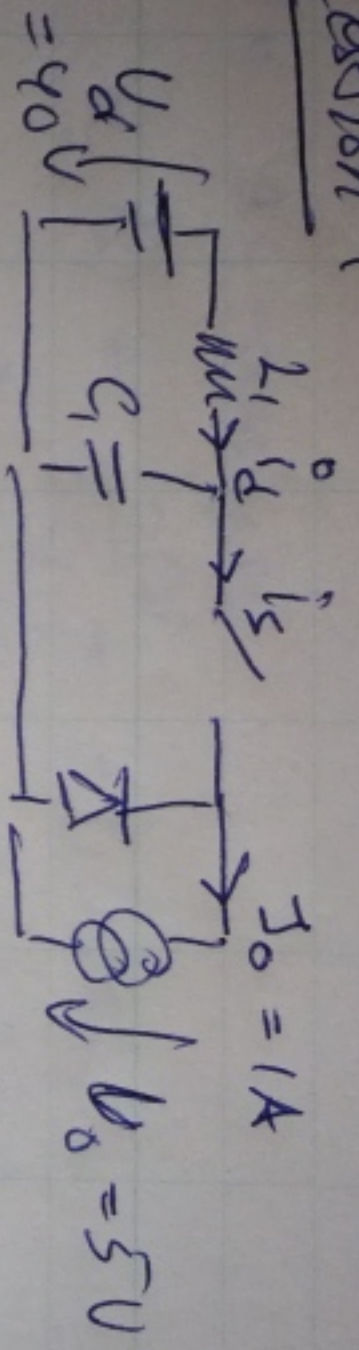

$$U_o = 0.125 U_s \Rightarrow D = \frac{5}{40} = 0.125$$

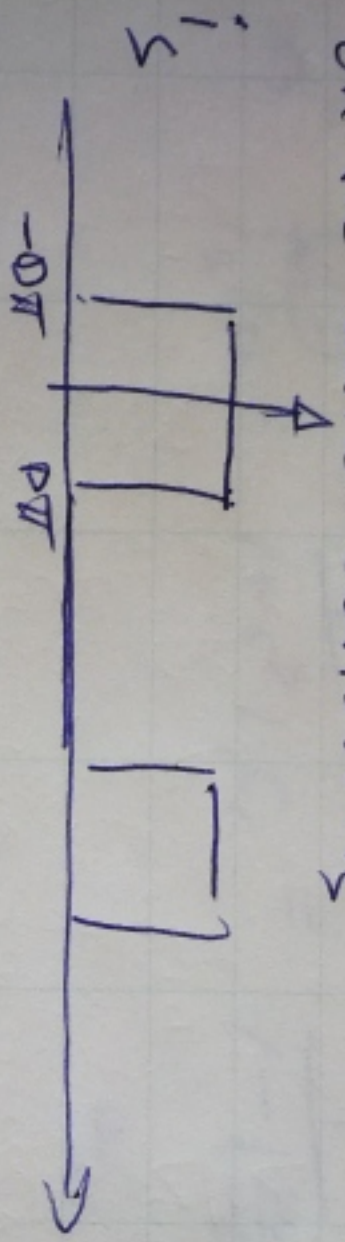Current from the supply U_s depends on the switch current i_s




Fourier series of i_s

$$i_s(x) = 0.125 + \frac{2.50}{\pi} \sum_{n=1}^{\infty} \frac{1}{n} \sin(nD\pi) \cos(nx)$$

largest value is $n=1$
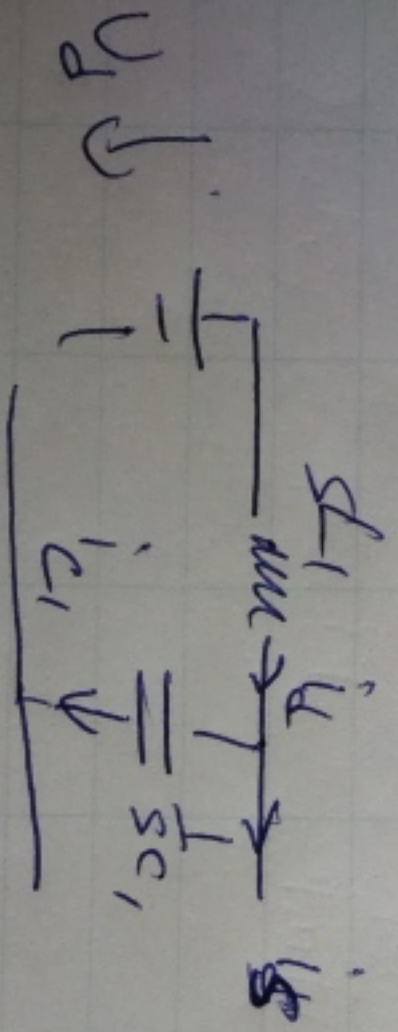
$$i_{s1} = \frac{2.50}{\pi} \sin(0.125\pi) = 0.243 \text{ A}$$



In ac-analysis

$$u_s(s) = \frac{i_{c1}(s)}{sC_1} = -i_j(s) sL_1$$

$$\Rightarrow i_{c1}(s) = -i_j(s) s^2 L_1 C_1$$

For currents

$$i_u(s) = i_s(s) + i_{c1}(s) = i_s(s) - i_j(s) s^2 L_1 C_1$$

$$\Rightarrow \frac{i_u(s)}{i_s(s)} = \frac{1}{1 + s^2 L_1 C_1} = \frac{1}{1 - \left(\frac{\omega}{\omega_{01}}\right)^2}$$

$$\omega_{01} = \underline{\underline{\omega_0}}$$

For the absolute values of $b=1$

$$\frac{|i_{D1}|}{|i_s|} = \left| \frac{1}{1 - \left(\frac{\omega}{\omega_{01}}\right)^2} \right| = \left| \frac{1}{\left(\frac{\omega}{\omega_{01}}\right)^2 - 1} \right|$$

$$\omega_{01} = \omega_s \sqrt{1 + \frac{L_1}{100}} \approx 8998 \text{ rad/s}$$

Question 2

In exercise 1 question 2 it has been shown that in the decreasing area of Flyback

$$\frac{V_o}{V_i} = D \int \frac{R}{2Lmfs} \quad \text{where } R = \frac{V_o}{I_o}$$

In CCM of Flyback

$$\frac{V_o}{V_i} = \frac{N_2}{N_1} \cdot \frac{D}{1-D} \quad D = \frac{1}{\frac{N_2}{N_1} \frac{V_o}{V_i} + 1}$$

and in the buck-boost both coming

$$D \sqrt{\frac{R}{2Lmfs}} = \frac{N_2}{N_1} \cdot \frac{D}{1-D} \Rightarrow L_m = \frac{R(1-D)^2}{2fs} \quad \text{when } N_2 = N_1$$

Highest value of L_m is that with highest load $R = \frac{V_o}{I_o}$. However, with duty cycle it is a bit different, if we calculate with D_{min} (V_o max) then L_m would be larger and it would not be OCM with V_{min}

$$D_{max} = \frac{1}{\frac{12}{25} + 1} = 0,19 \text{ and } L_m \approx 0,5 \mu H$$

Question 3

In forward converter duty cycle ratio is limited due to the demagnetization time needed.

$$D_{max} = \frac{f_{L3}}{f_{s1}} = \frac{1}{2}$$

In forward magnetization is only in one quadrant and therefore

$$A_{B_{max}} = \frac{B_{sat}}{2}$$

Here input voltage can change and saturation should not occur even with the highest voltage \Rightarrow

$$B_{ac} = \frac{B_{sat}}{2} \cdot \frac{V_{Umh}}{V_{max}} = \frac{0,32}{2} \cdot \frac{210}{325} = 0,103T$$

$$G = \mu \frac{d\varphi}{dt} \Rightarrow \mu = \frac{G \frac{d\varphi}{dt}}{2 A_{umh} \cdot B_{ac}}$$

$$\approx \frac{117,7}{108} \Rightarrow N_1 = 108 \quad V_1 = V_{Umh}$$

In forward converter

$$\frac{V_o}{V_d} = \frac{N_2}{N_1} D$$

$$\Rightarrow N_2 = \frac{V_o}{V_d} \cdot \frac{N_1}{D} = \frac{12}{210} \cdot \frac{118}{0,5} = 13,5 = 14$$

$$L = \frac{\mu_0^2}{R} \quad \text{where } R = \frac{l}{\mu A} \quad \text{and}$$

with air gap

$$R = R_m + R_g = \frac{l_e}{\mu_e A_e} + \frac{l_g}{\mu_0 A_g} = \frac{\mu_0^2}{L}$$

$$\Rightarrow l_g = \frac{\mu_0^2 \mu_e A_e}{L} - \frac{l_e}{\mu_e} \quad A_g \approx A_e$$

$$A_e = 97,1 \text{ mm}^2, \quad N = 118, \quad l_e = \frac{V_e}{A_e} = \frac{7600}{97,1} \text{ mm}$$

$$l = 10 \text{ with}$$

$$\mu_0 = 4 \times \pi \times 10^{-7} \text{ H/m}$$

μ_r = relative permeability of 3C8
 which was not given in the paper but
 can be as in Exercise 11

$$\mu = \mu_r \mu_0 = 5,58 \text{ is}^{-3} \frac{\text{Vs}}{\text{Am}} \Rightarrow \mu_r = 4448$$

$$\Rightarrow l_g \approx 0,15 \text{ mm}$$