

Exercise 1

The voltages and current in the boost converter of figure 1 are $U_d = 12V$, $U_o = 24V$, $I_o = 1A$ and the value of the components are $L = 150\mu H$, $C = 470\mu F$ and the switching frequency is $f_s = 20kHz$. Calculate the variation in the output voltage ΔU_o .

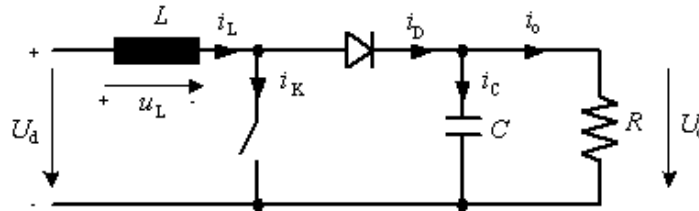


Figure 1: Boost converter.

Exercise 2

The voltages and current in the boost converter of figure 1 are $U_d = 12V$, $U_o = 24V$, $I_o = 1A$ with a capacitor of $C = 470\mu F$ and a switching frequency of $f_s = 20kHz$. Calculate the choke peak current $i_{L,peak}$, which is also the peak value of the switch current $i_{K,peak}$,

- a) when the choke value is $L = 150\mu H$. What happens is the value of the choke is higher?
- b) when the choke value is $L = 50\mu H$.

Calculate the ratio of the peak current of the choke with its average values, i.e. $i_{L,peak}/I_L$, as a function of L_{oB}/L . L_{oB} the minimal value of the choke L to keep the circuit working in the continuous conduction mode (CCM).

Exercise 3

Using figure 1, calculate the rms-value of the current i_D (figure 2) which is also the current in capacitor C , i_C , rms-value. The characteristic of the circuit are: $8 \leq U_d \leq 16V$, $U_o = 24V$, $I_o = 1A$, the output power $P_o \geq 5W$, $C = 470\mu F$, $L = 427\mu H$, $f_s = 20kHz$ and the duty ratio $D = 0,5$.

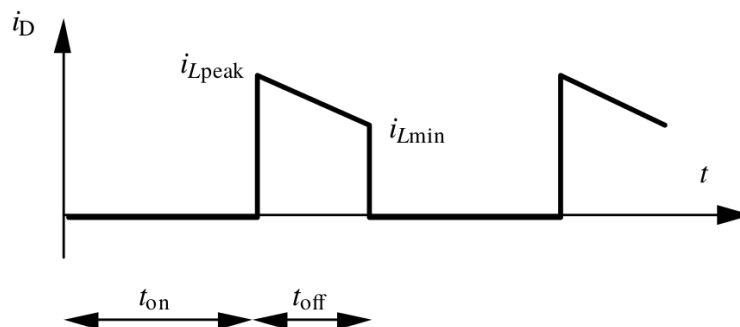


Figure 2: Diode current $i_D(t)$.