

**Exercise 1**

The Series load resonant (SLR) DC-DC converter of figure 1 works in discontinuous conduction mode (DCM) at a switching frequency  $\omega_s$  smaller than the resonant frequency  $\omega_0 = 1/\sqrt{L_r C_r}$  of the LC-circuit. The switching frequency is set to be  $\omega_s < \omega_0/2$ .

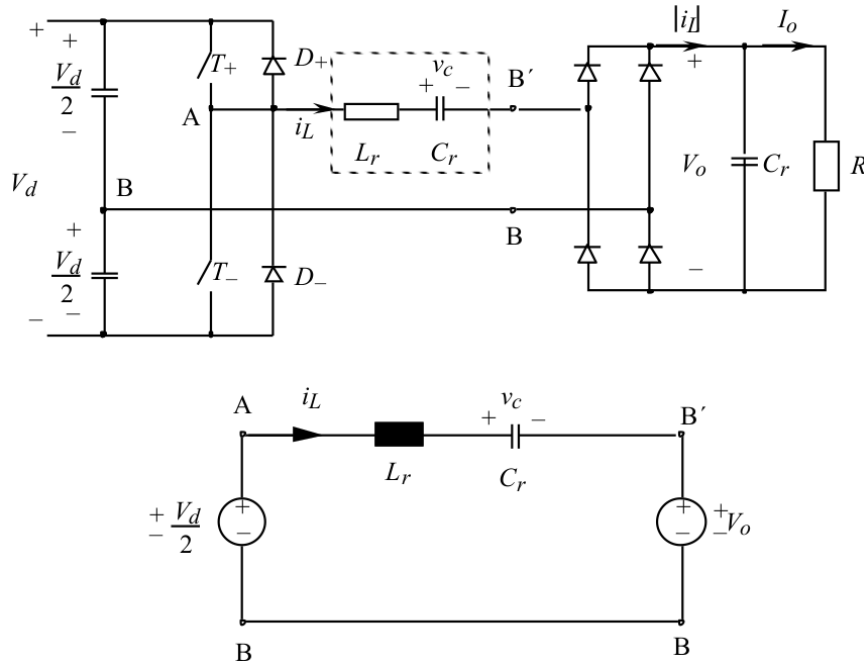


Figure 1: SLR DC-DC converter.

a) Show that the choke maximal current ratio is

$$\frac{I_{L_r,peak}}{I_b} = 1 + 2\frac{V_o}{V_d}, \quad \text{with } I_b = \frac{V_d}{2Z_0} \text{ and } Z_0 = \sqrt{\frac{L_r}{C_r}} \quad (1)$$

b) Show that the voltage ratio of the peak value over the capacitor  $C_r$  is

$$\frac{V_{C_r,peak}}{V_b} = 2 \quad \text{with } V_b = \frac{V_d}{2} \quad (2)$$

c) Show that the SLR-converter can only work as a voltage step-down.

The instantaneous voltage over  $C_r$  and current in the resonant circuit can be expressed as

$$v_{C_r}(t) = V_{in} - (V_{in} - V_{C_0})\cos(\omega_0 t) + Z_0 I_{L_0} \sin(\omega_0 t) \quad (3)$$

and

$$i_{L_r}(t) = I_{L_0} \cos(\omega_0 t) + \frac{V_{in} - V_{C_0}}{Z_0} \sin(\omega_0 t) \quad (4)$$

where  $V_{AB'}$  is the input voltage of the resonant circuit (figure 2),  $V_{C_0}$  is the initial voltage over  $C_r$ , and  $I_{L_0}$  the initial current of  $L_r$ .

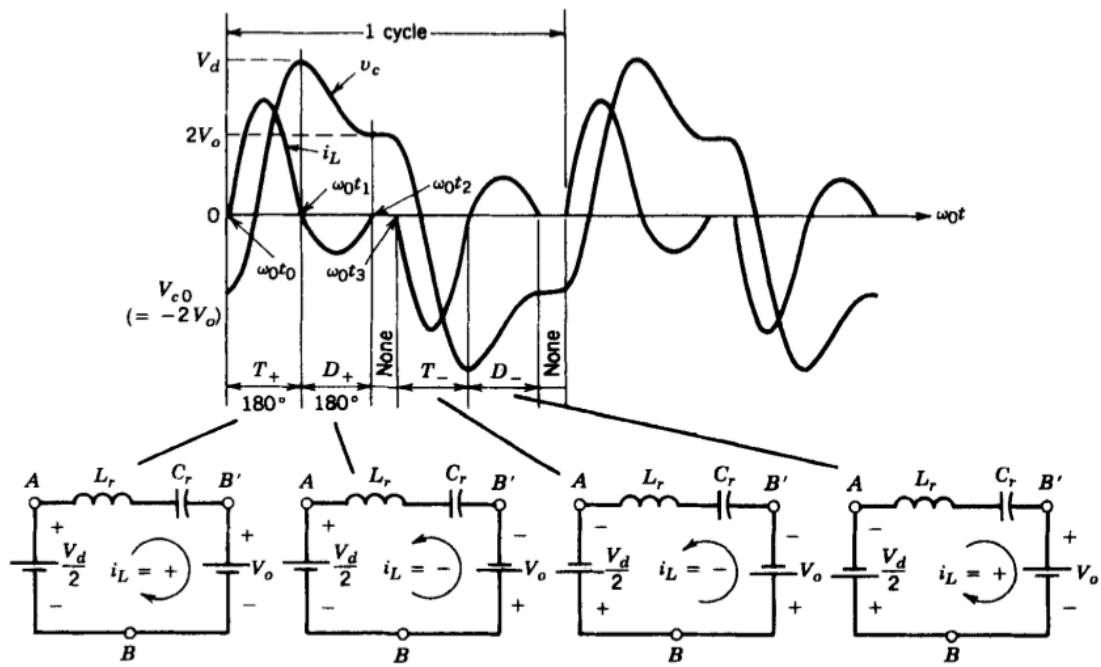


Figure 2: SLR DC-DC converter; discontinuous-conduction mode with  $\omega_s < \frac{1}{2}\omega_0$ .

### Exercise 2

In the figure, a ZCS (Zero current switch) DC-DC converter is represented.

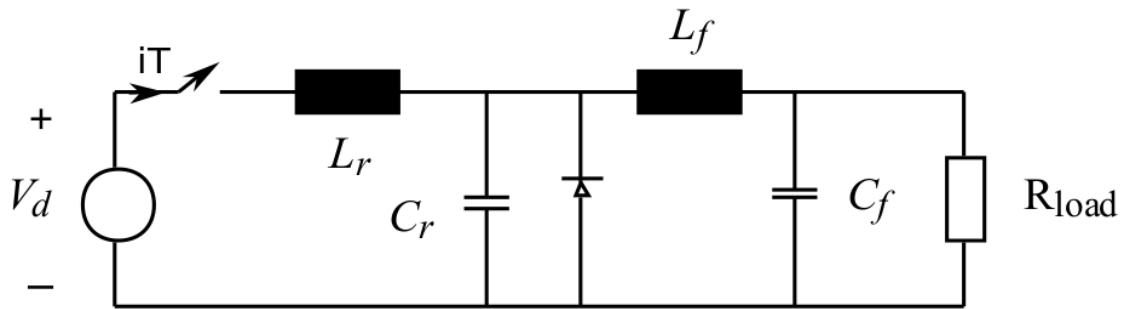


Figure 3: ZCS resonant switch DC-DC converter.

The characteristics of the circuit are as follow:

- the resonance frequency  $f_0 = 1\text{MHz}$
- The characteristic impedance  $Z_0 = 10\Omega$
- the input voltage is  $V_d = 15\text{V}$
- the output voltage is  $V_o = 10\text{V}$
- the output power  $P_o = 10\text{W}$

Obtain the instantaneous current  $i_T(t)$  and voltage  $u_{C_r}(t)$  over the capacitor  $C_r$ , and the time intervals  $t_1 - t_0, t'_1 - t_1, t''_1 - t_1, t_2 - t_1, t_3 - t_2, t_3 - t_4$ . Calculate the maximal and minimal value of  $i_T(t)$  and  $u_{C_r}(t)$ . What is the switching frequency  $f_s$ ?

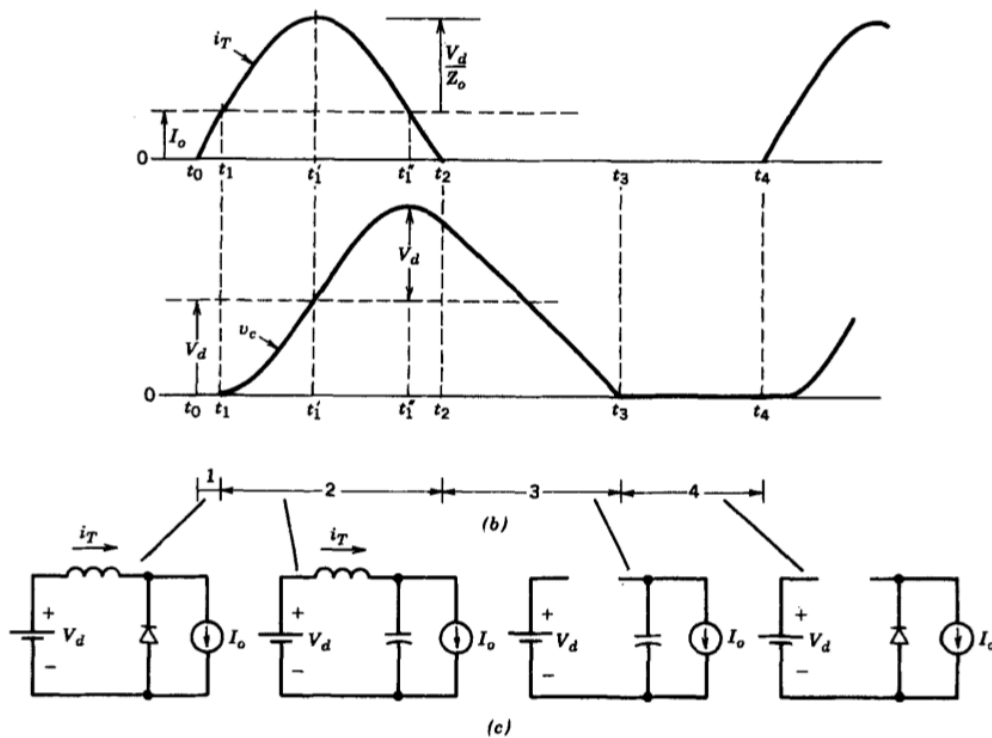


Figure 4: ZCS resonant-switch DC-DC converter waveforms.

The resonant circuit with a parallel load has the following equations: the current in the choke  $L_r$  is

$$i_{L_r}(t) = I_o + (I_{L0} - I_o)\cos(\omega_0 t) + \frac{V_d - V_{C0}}{Z_0}\sin(\omega_0 t) \quad (5)$$

and the voltage over the capacitor  $C_r$

$$v_{C_r}(t) = V_d - (V_d - V_{C0})\cos(\omega_0 t) + Z_0(I_{L0} - I_o)\sin(\omega_0 t) \quad (6)$$

The initial values are  $V_{C0}$  for the capacitor  $C_r$  and  $I_{L0}$  for the inductance  $L_r$ .