

### Exercise 1

A flyback converter is working in the incomplete demagnetization area with the control ratio  $D = 0,4$ . To realize this setting, two flyback converters can also be connected in parallel like in the figure 1 to reduce the power in each converter.

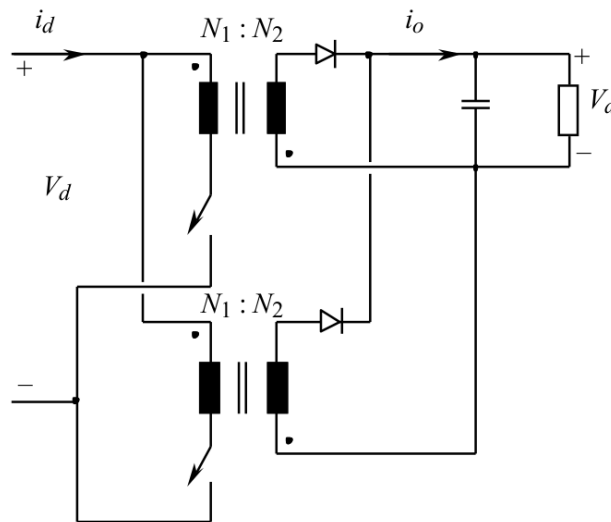


Figure 1: Two Flyback-converters connected in parallel.

Compare the input current  $i_d$  and output current  $i_o$  in the two possibilities when the output voltage is considered as constant. What are the current peak values in both cases when the transformer ratio  $N_1 : N_2 = 1$ ? The parallel flyback converters are controlled with a  $\pi$  delay with the other one.

### Exercise 2

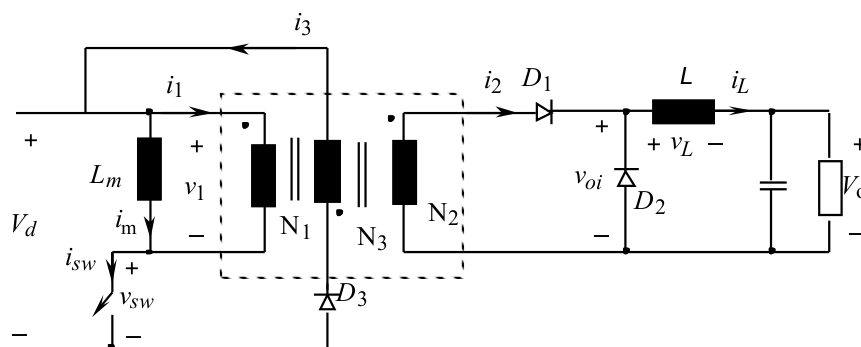


Figure 2: Forward-converter.

The characteristics of the Forward-converter of figure 2 are as followed:

$V_d = 48V \pm 10\%$ ,  $V_o = 5V$ ,  $f_s = 100kHz$ , the power in the load  $P_o$  varies between 15W and 50W. The demagnetization winding number of turn is  $N_3 = N_1$ .

- a) Calculate the minimal value of the ratio  $N_2/N_1$  allowed.

- b) Calculate the inductance of the choke  $L$  that keeps the converter working in continuous conduction mode (CCM).

## **Exercise 3**

Using the results of the previous exercise, calculate the RMS-value of the current in the inductance  $I_L$  when  $V_d = 48\text{V}$ ,  $N_2/N_1 = 1/4$ , the output power  $P_o = 50\text{W}$  and the inductance is  $L = 20,68\mu\text{H}$ .