

**Exercise 1**

Obtain the small signal transfer function  $\frac{\tilde{v}_o(s)}{\tilde{d}(s)}$  of a Flyback-converter working in continuous conduction mode (CCM).  $\tilde{v}_o$  is the small perturbation in the output signal  $v_o(t)$  and  $\tilde{d}$  is the small perturbation in the switch duty ration  $d(t)$ . For the sake of simplicity, the ratio of the transformer  $N1/N2 = 1$  and the components are assumed to be ideal. Draw the Bode-diagram when  $V_d = 24\text{V}$ ,  $V_o = 12\text{V}$  and the resistance of the load is  $R = 5\Omega$ . The switching frequency is  $f_s = 200\text{kHz}$  and the values of the components are  $L = 10\mu\text{H}$  and  $C = 100\mu\text{F}$ .

**Exercise 2**

Obtain the transfer function  $\frac{\tilde{v}_o(s)}{\tilde{d}_1(s)}$  of a flyback converter working in discontinuous conduction mode (DCM). It is assumed that in the converter is with a feedback loop. The rest of the values are in the previous exercise. What is the value of  $R$  that set the converter working at the limit of CCM and DCM? Draw the Bode diagram when the resistive load  $R = 15\Omega$ .