


Lecture 3

Lecturer: G. S. Paraoanu


*Department of Applied Physics, School of Science,
Aalto University, P.O. Box 15100, FI-00076 AALTO, Finland*

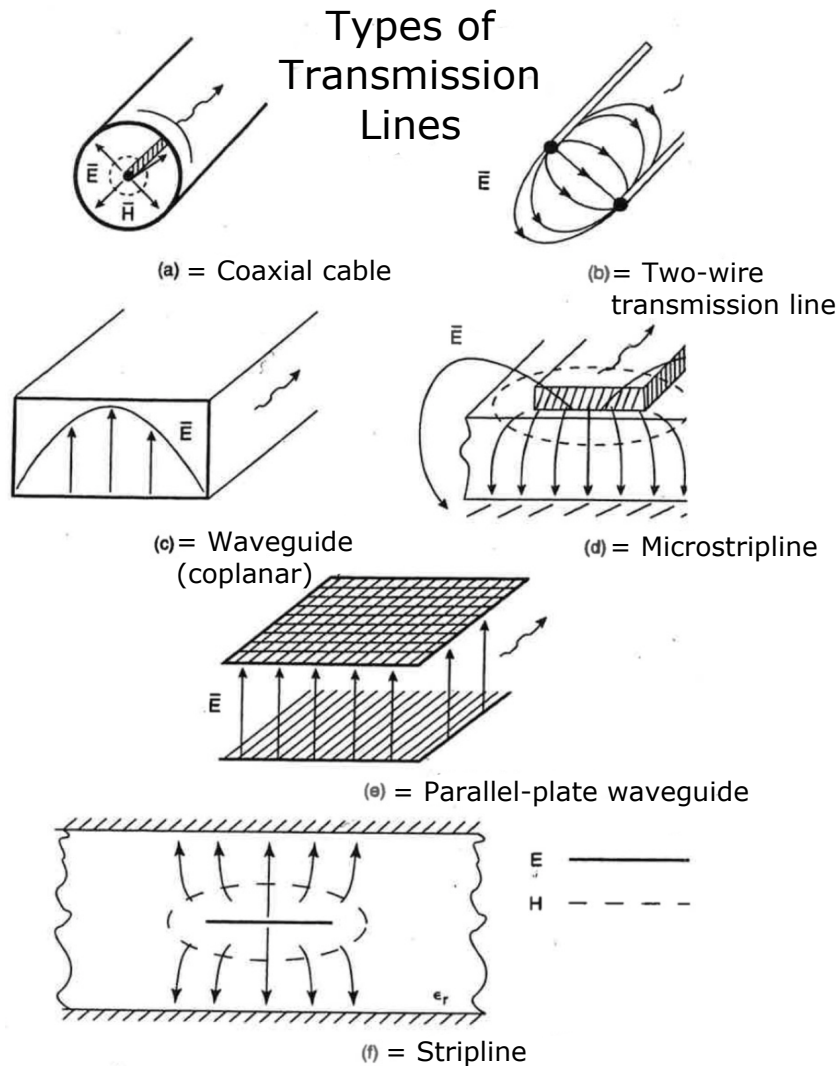I. TRANSMISSION LINES

- Electromagnetic waves can propagate in free space (Review this! Based on Maxwell's equations!). But also they can be guided by conducting or dielectric boundaries.
- Transmission line behavior: occurs when $\lambda \ll$ length of transmission line.
- Transmission lines = guiding devices for the electromagnetic field.
- The electromagnetic fields are TEM (transverse electromagnetic mode) if the conductors are ideal (zero-resistance); otherwise there will be a small axial component of the electromagnetic field.



EXAMPLE: The coaxial line

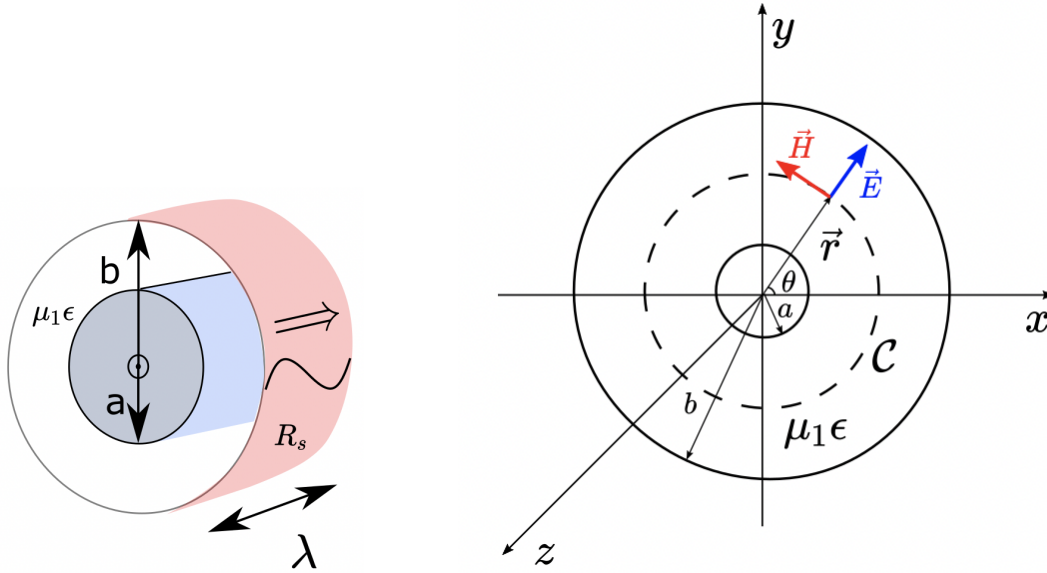


* How to calculate the \vec{E} , \vec{H} fields inside?

Electric Field:
$$\vec{E} = \frac{V_0}{\ln \frac{b}{a}} \hat{r} \quad (1)$$

Proof:

$$\vec{\nabla} \cdot \vec{D} = \rho \implies \int d\vec{S} \cdot \vec{E} = \int \frac{\rho}{2} dV \implies 2\pi r \cdot (\Delta z) \cdot E = \frac{1}{\epsilon} (\Delta z) \cdot \rho \cdot \pi a^2 \quad \therefore E = \frac{1}{r} \cdot \frac{\rho a^2}{2\epsilon}$$

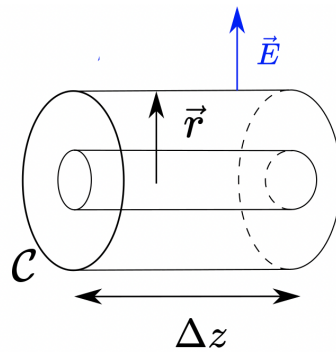Also $V_0 = \int_a^b dr \cdot E = \int_a^b \frac{dr}{r} \cdot \rho \frac{a^2}{2\epsilon} \ln \frac{b}{a} \rightarrow \rho \frac{a^2}{2\epsilon} = \frac{V_0}{\ln \frac{b}{a}}$, so $\vec{E} = \frac{V_0}{\ln \frac{b}{a}} \hat{r}$.




Magnetic Field:
$$\vec{H} = \frac{I_0}{2\pi r} \cdot \hat{e}_\theta \quad (2)$$

Proof:

$$\vec{\nabla} \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t} \implies \int_C \vec{H} \cdot d\vec{\ell} = \int \vec{J} \cdot d\vec{S} = I_0, \text{ or } 2\pi r \cdot H = I_0 \implies \vec{H} = \frac{I_0}{2\pi r} \cdot \hat{e}_\theta.$$

II. TOWARDS A DISTRIBUTED MODEL OF INDUCTORS, CAPACITANCES, RESISTANCES, CONDUCTANCES

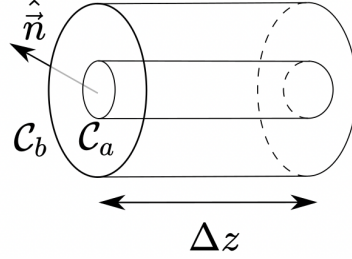Problem: How to connect the electric and magnetic fields to circuit elements.



Answer: Via stored or dissipated energy.

1. Inductance per unit length

$$\text{Magnetic energy} = \frac{\mu}{4} \int ds \cdot (\Delta z) \vec{H}^2 = \frac{(L' \Delta z) I_0^2}{4} \implies L' = \frac{\mu}{I_0^2} \int ds \vec{H}^2$$

$$L' = \frac{\mu}{I_0^2} \int ds H^2 = \frac{\mu}{I_0^2} \cdot I_0^2 \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{1}{(2\pi r)^2} = \frac{\mu}{2\pi} \ln \frac{b}{a}.$$

Therefore,

$$L' = \frac{\mu}{2\pi} \ln \frac{b}{a} \quad (\text{measured in units of H/m}). \quad (3)$$

2. Capacitance per unit length

$$\text{Electrostatic energy} = \frac{\epsilon}{4} \int ds \cdot (\Delta z) \cdot E^2 = \frac{(C' \Delta z) V_0^2}{4} \implies C' = \frac{\epsilon}{V_0^2} \cdot \int ds \cdot E^2$$

$$C' = \frac{\epsilon}{V_0^2} \int ds E^2 = \frac{\epsilon}{V_0^2} \cdot V_0^2 \cdot \frac{1}{\ln^2 \frac{b}{a}} \int_0^{2\pi} d\theta \int_0^b dr \cdot r \cdot \frac{1}{r^2}$$

$$\implies C' = \frac{2\pi\epsilon}{\ln \frac{b}{a}} \quad (\text{measured in units of F/m}). \quad (4)$$

3. Resistance per unit length

$$\text{Power dissipated in the lossy conductors} = \frac{R_s}{2} \int_{C_a+C_b} dl \cdot \Delta z \cdot \vec{J}_s^2 = \frac{R_s}{2} \Delta z \cdot \int_{C_a+C_b} dl \cdot H^2 = \frac{R' \Delta z}{2} I_0^2. \text{ Here } R_s = \text{surface resistance, } \vec{J}_s = \hat{n} \times \vec{H} = \text{surface current, } \hat{n} = \text{vector unit}$$

pointing outwards (normal to the conducting surface), and $R' = \frac{R_s}{I_0^2} \int_{C_a+C_b} d\ell \cdot \vec{H}^2$.

$$R' = \frac{R_s}{I_0^2} \int_{C_a+C_b} d\ell \cdot H^2 = \frac{R_s}{(2\pi)^2} \left[\int_0^{2\pi} d\theta \cdot a \cdot \frac{1}{a^2} + \int_0^{2\pi} d\theta \cdot b \cdot \frac{1}{b^2} \right] = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$$

$$R' = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right) \quad (\text{measured in units of } \Omega/\text{m}). \quad (5)$$

4. Conductance (radial) per unit length

$$\epsilon = \epsilon' - i\epsilon'' = \epsilon_0\epsilon_r(1 - i \tan \delta)$$

$$\epsilon' = \epsilon_0\epsilon_r$$

$\epsilon'' = \epsilon \tan \delta \rightarrow$ dissipation in the dielectric between the core metal and the outside shield.


$$\text{Power dissipated} = \frac{\omega\epsilon''}{2} \int ds \cdot \Delta z \cdot E^2 = \frac{G'V_0^2}{2} \rightarrow G'' = \frac{\omega\epsilon''}{V_0^2} \int ds \cdot E^2$$

$$\Rightarrow G' = \frac{\omega\epsilon''}{V_0^2} \int ds \cdot E^2 = \frac{\omega\epsilon''}{V_0^2} \cdot \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{V_0^2}{r^2 \ln \frac{b}{a}}$$

$$\Rightarrow G' = \frac{2\pi\omega\epsilon''}{\ln \frac{b}{a}} \quad (\text{measured in units of S/m}). \quad (6)$$

NOTE: In the calculation 3. resistance per unit length we used the surface resistance R_s and the surface current \vec{J}_s . Note that these concepts are different from "just" resistance and from the current density \mathcal{J} which appears in Maxwell's equation (see Lecture 1) or when we write Ohm's law in the form $\vec{J} = \sigma\vec{E}$ (see Lecture 2).

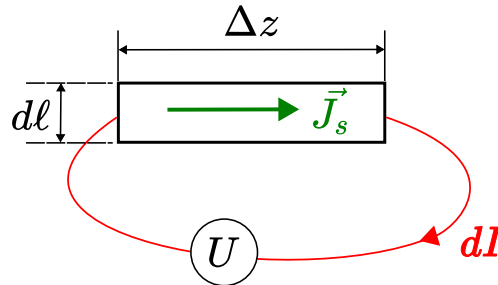Consider a slab of metal, like in the next figure. The current density is defined as $\mathcal{J} = \frac{dI}{ds}$,



so it represents the current per unit area that flows through the wires. It has dimension of

(charge/unit time)/(unit area), so it is measured in A/m². But for a thin sheet of metal a sensible quantity to define is

$$\mathcal{J}_s = \frac{dI}{dl} \quad (7)$$

which means (charge/unit time)/(unit length across the sheet). It is called surface current density and it is measured in A/m.

We can then consider the quantity $U/(\Delta z)$, which is the drop of voltage per unit length in the direction of the current, and define


$$R_s = \frac{U/(\Delta z)}{\mathcal{J}_s} \quad (8)$$

This quantity has units of Ohms, so we can call it resistance. As a result, the power dissipated is

$$\frac{1}{2} \int dI \cdot U = \frac{1}{2} \Delta z \int_{\mathcal{C}} dl (R_s \mathcal{J}_s) \mathcal{J}_s = \frac{1}{2} \Delta z \int_{\mathcal{C}} dl R_s \mathcal{J}_s^2 \quad (9)$$

where \mathcal{C} is a contour containing the element dl .

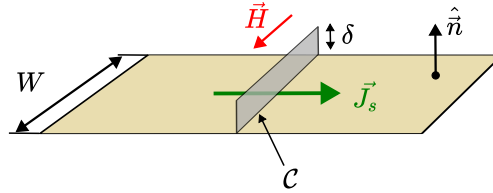To obtain the connection between the surface current density and the magnetic field, consider the contour \mathcal{C} in the figure below. We also take for simplicity the vector \vec{H} as shown in the figure, which reflect the way it is in a small length W around the coaxial cable.



So we have from the Maxwell-Ampère law $\nabla \times \vec{H} = \vec{\mathcal{J}} + \frac{\partial \vec{D}}{\partial t}$ and therefore applying Stokes' theorem we get

$$\int_{\mathcal{C}} d\vec{l} \vec{H} = HW \quad (10)$$

$$= \int_S d\vec{s} \left(\vec{\mathcal{J}} + \frac{\partial \vec{D}}{\partial t} \right) = \mathcal{J} \delta W = \mathcal{J}_s W \quad (11)$$


where you can see using the definitions above that $\mathcal{J}_s = \mathcal{J} \delta$. So in the end $\mathcal{J}_s = H$. It is easy to generalize this relation to $\vec{\mathcal{J}}_s = \hat{n} \times \vec{H}$.

- Examples of materials used in coaxes:

Conductor	Copper Cu	Aluminum Al	Silver Ag	Gold Au
Resistivity ρ [n $\Omega \cdot$ m]	16.9	26.7	16.3	22.0

Dielectric	Dry Air	Polyethylene	PTFE	PVC
ϵ_r	1.0006	2.2	2.1	3.2
$\tan \delta$	low	0.0002	0.0002	0.001
Resistivity ($\Omega \cdot$ m)	high	10^{15}	10^{15}	10^{15}
Breakdown voltage (mV/m)	3	47	59	34

Other transmission lines:

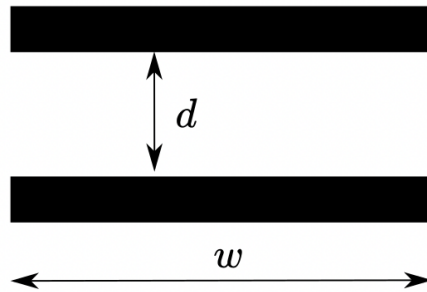


$$L' = \frac{\mu d}{w} \quad (12)$$

$$C' = \frac{\epsilon' w}{d} \quad (13)$$

$$R' = \frac{2R_s}{w} \quad (14)$$
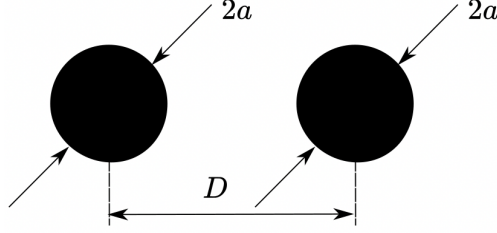
$$G' = \frac{\omega \epsilon'' w}{d} \quad (15)$$



$$L' = \frac{\mu}{\pi} \cosh^{-1} \frac{D}{2a} \quad (16)$$

$$C' = \frac{\pi \epsilon'}{\cosh^{-1} \frac{D}{2a}} \quad (17)$$

$$R' = \frac{R_s}{\pi a} \quad (18)$$

$$G' = \frac{\pi \omega \epsilon''}{\cosh^{-1} \frac{D}{2a}} \quad (19)$$

III. TRANSMISSION LINES: GENERAL MODELS

- If the length of a circuit is $\gtrsim \lambda$ we have to use either a simulator of Maxwell's equations or a distributed model of lumped elements.
- Transmission lines: Two parallel conductors that guide the electromagnetic field. Examples: two-wire lines, striplines, microstrip lines.

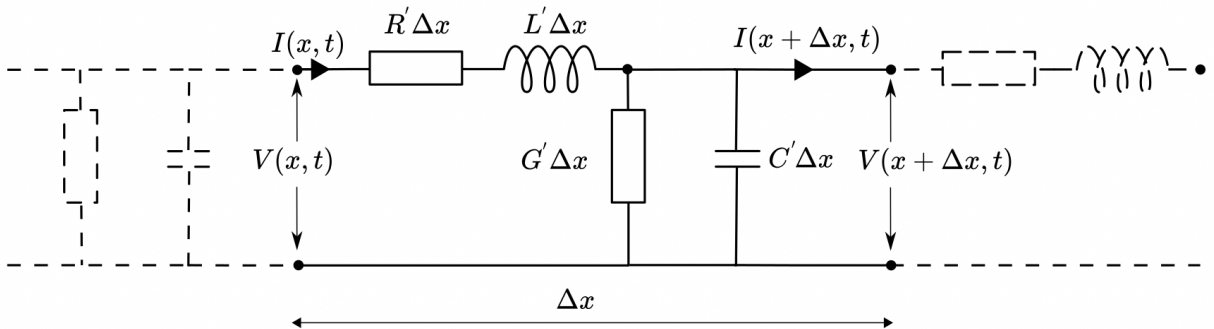


FIG. 1. Schematic of the distributed model of a transmission line, with lumped circuit elements defined per unit length L', C', R', G' . Here we denote the coordinate along the line by x (instead of z as in the previous section), in order to avoid any notational confusion with the Z of impedances.

R', L', G', C' = resistance, inductance, conductance, capacitance per unit length.

Kirchoff says:

$$\begin{cases} V(x, t) = I(x, t)R'\Delta x + L'\Delta x \cdot \frac{\partial I(x, t)}{\partial t} + V(x + \Delta x, t) \\ I(x, t) = V(x + \Delta x, t)G'\Delta x + C'\Delta x \frac{\partial V(x + \Delta x, t)}{\partial t} + I(x + \Delta x, t) \end{cases} \quad (20)$$

$$\Delta x \rightarrow 0 \begin{cases} -\frac{\partial V(x, t)}{\partial x} = R'I(x, t) + L'\frac{dI(x, t)}{dt} \\ -\frac{\partial I(x, t)}{\partial x} = G'V(x, t) + C'\frac{\partial V(x, t)}{\partial t} \end{cases} \quad (21)$$

Therefore,

$$\begin{cases} -\frac{\partial^2 V(x, t)}{\partial x^2} = -R'(G'V(x, t) + C'\frac{\partial V(x, t)}{\partial t}) - L'(G'\frac{\partial V(x, t)}{\partial t} + C'\frac{\partial^2 V(x, t)}{\partial t^2}) \\ -\frac{\partial^2 I(x, t)}{\partial x^2} = -G'(R'I(x, t) + L'\frac{\partial I(x, t)}{\partial t}) - C'(R'\frac{\partial I(x, t)}{\partial t} + L'\frac{\partial^2 I(x, t)}{\partial t^2}) \end{cases} \quad (22)$$

or

$$\begin{cases} \frac{\partial^2 V(x, t)}{\partial x^2} = L'C'\frac{\partial^2 V(x, t)}{\partial t^2} + (R'C' + L'G')\frac{\partial V(x, t)}{\partial t} + R'G'V(x, t) \\ \frac{\partial^2 I(x, t)}{\partial x^2} = L'C'\frac{\partial^2 I(x, t)}{\partial t^2} + (R'C' + L'G')\frac{\partial I(x, t)}{\partial t} + R'G'I(x, t) . \end{cases} \quad (23)$$

Harmonic signals:

$$V(x, t) = V(x)e^{i\omega t}, \quad V(x), I(x) = \text{phasors}, \quad I(x, t) = I(x)e^{i\omega t}$$

$$\Rightarrow \begin{cases} \frac{d^2 V(x)}{dx^2} - \gamma^2 V(x) = 0, \quad \text{where } \gamma = \alpha + i\beta = \sqrt{(R' + i\omega L')(G' + i\omega C')} \\ \frac{d^2 I(x)}{dx^2} - \gamma^2 I(x) = 0, \quad \gamma = \text{propagation constant}, \alpha = \text{attenuation constant}, \beta = \text{phase constant} \end{cases}$$

$$\text{General Solution: } V(x) = V^\dagger e^{-\gamma x} + V^- e^{\gamma x}. \quad (24)$$

From $-\frac{\partial V(x, t)}{\partial x} = R'I(x, t) + L'\frac{\partial I(x, t)}{\partial t}$, we get $I(x) = -\frac{1}{R' + i\omega L'} \frac{dV(x)}{dx}$ or $I(x) = \frac{1}{Z_0} V^\dagger e^{\gamma x} - \frac{1}{Z_0} V^- e^{-\gamma x} = I^+ e^{-\gamma x} + I^- e^{\gamma x}$, where $Z_0 = \sqrt{\frac{R' + i\omega L'}{G' + i\omega C'}}$ = characteristic impedance of the transmission line, and where $I^\pm = \pm \frac{V^\pm}{Z_0}$.

Lossless transmission case: $R' = G' = 0$

$$\gamma = i\beta = i\omega\sqrt{L'C'}$$

$$Z_0 = \frac{1}{Y_0} = \sqrt{\frac{L'}{C'}} \rightarrow \text{now independent of frequency!}$$

Note: Free-space impedance = 377 Ω

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}} = \text{phase velocity.}$$

Exercise: Show that for the loss-less case $R' \ll \omega L'$, $G' \ll \omega C'$, we have $\beta \simeq \omega\sqrt{L'C'}$ and $\alpha \simeq \frac{1}{2}\sqrt{L'C'}(\frac{R'}{L'} + \frac{G'}{C'})$.

TABLE I. Some standardized values of Z_0 .

Z_0	Application
50 Ω	Instrumentation, communication
75 Ω	TV, VHF radio
300 Ω	RF
600 Ω	Audio

NOTE:

Let's contemplate a bit what is the meaning of the quantities $V^+e^{-\gamma x}$ and $V^-e^{\gamma x}$. These are the phasors of the waves propagating in the positive and negative direction of the x -axis, respectively.


How do you see this?

Let's take first the "+" wave. We have

$V^+e^{-\gamma x}e^{i\omega t} = V^+e^{-\alpha x}e^{i\omega(t-\frac{x}{v_p})}$, where $\gamma = \alpha + i\beta$ and the phase velocity $v_p = \frac{\omega}{\beta}$. Now let's look at what happens if we follow a constant phase $t - \frac{x}{v_p} = \varphi$. We get $x = v_p t - \varphi$. So this means propagation in the positive x -direction.

In contrast, the "-" wave

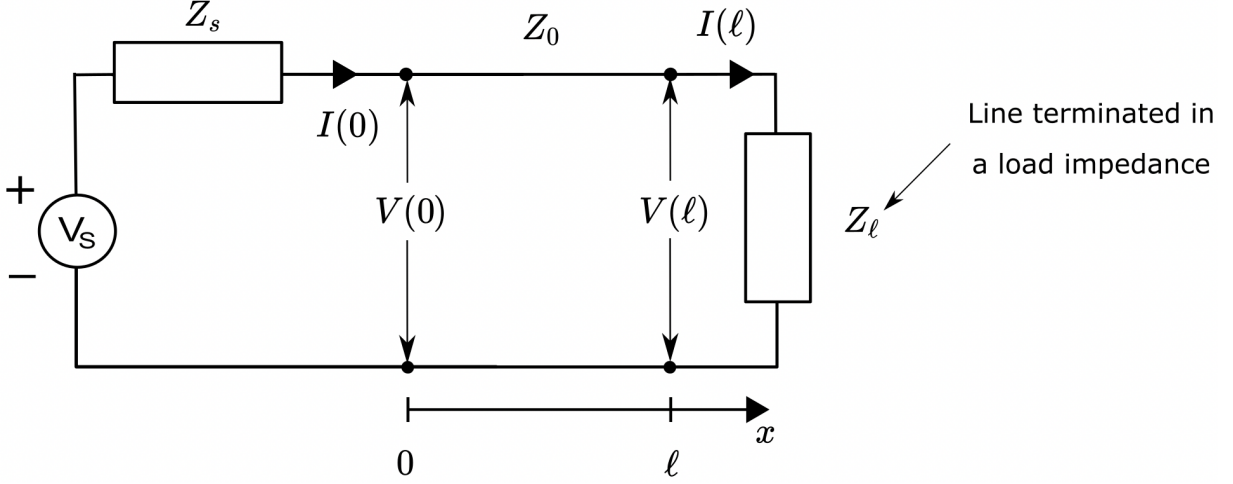$V^-e^{\gamma x}e^{i\omega t} = V^-e^{-\alpha x}e^{i\omega(t+\frac{x}{v_p})}$, where also here $\gamma = \alpha + i\beta$ and the phase velocity $v_p = \frac{\omega}{\beta}$. Again we follow a constant phase but now that phase is $t + \frac{x}{v_p} = \varphi$. We get $x = -v_p t - \varphi$. So this means propagation in the negative x -direction.



IV. INCIDENT AND REFLECTED WAVES ALONG A LOADED TRANSMISSION LINE

$$V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x}$$

$$I(x) = I^+ e^{-\gamma x} + I^- e^{\gamma x}, \quad I^\pm = \pm \frac{V^\pm}{Z_0}$$

$$\begin{cases} V(0) = V_s - Z_s I_0 & \text{--- Kirchoff's law} \\ V(l) = Z_\ell I(l), \end{cases} \quad (25)$$

or

$$\begin{cases} V^+ + V^- = V_s - \frac{Z_s}{Z_0} (V^+ + V^-) \\ V^+ e^{-\gamma \ell} + V^- e^{\gamma \ell} = \frac{Z_\ell}{Z_0} (V^+ e^{-\gamma \ell} - V^- e^{\gamma \ell}) \end{cases} \quad (26)$$

- Reflection and transmission coefficients

Define a reflection coefficient of the load at $x = \ell$: $\Gamma_V = \frac{V^- e^{\gamma \ell}}{V^+ e^{-\gamma \ell}}$.

$$\rightarrow 1 + \Gamma_V = \frac{Z_\ell}{Z_0} (1 - \Gamma_V).$$

$$\implies \Gamma_V = \frac{Z_\ell - Z_0}{Z_\ell + Z_0} \quad (27)$$

We can also define a current reflection coefficient at the load

$$\Gamma_I = \frac{I^- e^{\gamma \ell}}{I^+ e^{-\gamma \ell}} = -\Gamma_V \quad (28)$$

Define a transmission coefficient at the load $x = \ell$: $T_V = \frac{V^+e^{+\ell} + V^-e^{\gamma\ell}}{V^+e^{-\gamma\ell}}$.

$$\therefore T_V = 1 + \Gamma_V, \quad (29)$$

and for the current

$$T_I = \frac{I^+e^{-\gamma\ell} + I^-e^{\gamma\ell}}{I^+e^{-\gamma\ell}} = 1 + \Gamma_I. \quad (30)$$

- Average power delivered to the load

$\overline{P}_\ell = \frac{1}{2}\text{Re}[V(\ell)I^*(\ell)]$, where the $1/2$ comes from the fact that the field is harmonic.

Now,

$$\begin{cases} 1 - \Gamma_V = \frac{I^-e^{\gamma\ell} + I^+e^{-\gamma\ell}}{I^+e^{-\gamma\ell}} = \frac{I(\ell)}{I^+e^{-\gamma\ell}} \\ 1 + \Gamma_V = \frac{V^+e^{-\gamma\ell} + V^-e^{\gamma\ell}}{V^+e^{\gamma\ell}} = \frac{V(\ell)}{V^+e^{-\gamma\ell}}. \end{cases} \quad (31)$$

$$\therefore (1 + \Gamma_V^*)(1 + \Gamma_V) = \frac{V(\ell)I^*(\ell)}{I^+*V^+e^{-\gamma\ell}(e^{-\gamma\ell})^*}, \text{ but } I^+ = \frac{V^+}{Z_0}$$

$V(\ell)I^*(\ell) = \frac{1}{Z_0}|V^+e^{-\gamma\ell}|^2 \cdot (1 - \Gamma_V^*)(1 + \Gamma_V) \equiv 1 - \Gamma_V^* + \Gamma_V - |\Gamma_V|^2$, where $\Gamma_V^* + \Gamma_V = \text{Imaginary!}$.

$$\overline{P}_\ell = \frac{1}{2Z_0} \cdot |V^+e^{-\gamma\ell}|^2(1 - |\Gamma_V|^2). \quad (32)$$

- VSWR (Voltage standing-wave ratio)

$$V(x) = V^+e^{-\gamma x} + V^-e^{\gamma x} = V^+e^{-\gamma x}[1 + \Gamma_V e^{-2\gamma(\ell-x)}] \quad (\text{Remember that } \Gamma_V \equiv \frac{V^-e^{\gamma\ell}}{V^+e^{-\gamma\ell}}.)$$


Let's consider a lossless line $\alpha = 0$, $\gamma = i\beta = \frac{2\pi i}{\lambda}$

$|V(x)| = |V^+| \cdot |1 + \Gamma_V e^{-2i\beta(\ell-x)}|$ — oscillates, min. and max. separated by $\frac{\pi}{\beta} = \frac{\lambda}{2}$.

$VSWR = \frac{1+|\Gamma_V|}{1-|\Gamma_V|}$ = ratio between the max. line voltage and min. line voltage.

- Impedance along the line
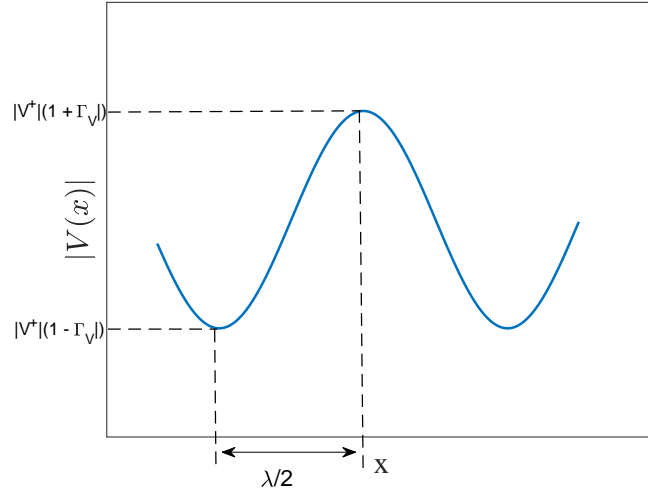
$$Z(x) = \frac{V(x)}{I(x)} = Z_0 \frac{V^+e^{-\gamma x} + V^-e^{\gamma x}}{V^+e^{-\gamma x} - V^-e^{\gamma x}} = \frac{1 + \Gamma_V e^{-2\gamma(\ell-x)}}{1 - \Gamma_V e^{-2\gamma(\ell-x)}}.$$



Take $x = 0 \rightarrow$ we get $Z(0) \equiv Z_{in} =$ input impedance of the line, i.e., the impedance seen when looking toward the load.

$$Z_{in} = Z_0 \cdot \frac{Z_\ell + Z_0 \tanh \gamma \ell}{Z_0 + Z_\ell \tanh \gamma \ell} \quad (33)$$

Note that this can be verified immediately by recalling that $\Gamma_V = \frac{Z_\ell - Z_0}{Z_\ell + Z_0}$, and that in general, $Z_{in} \neq Z_0$, so the termination matters! Also, Z_{in} is frequency-dependent.

V. FURTHER READING

- David M. Pozar — Microwave Engineering.
- R.E. Collin — Foundations for Microwave Engineering.