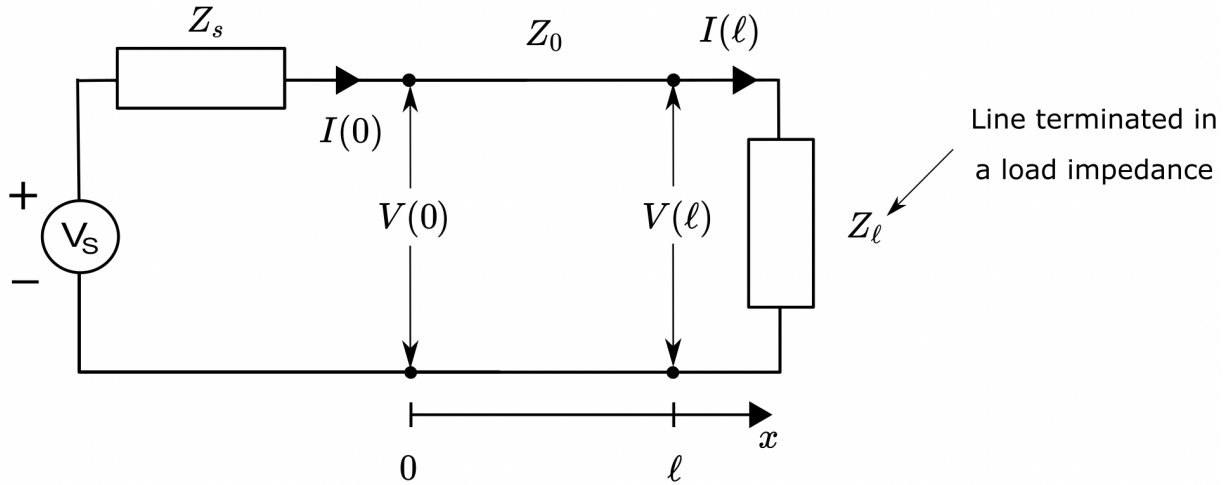


## Lecture 4

Lecturer: G. S. Paraoanu

*Department of Applied Physics, School of Science,  
Aalto University, P.O. Box 15100, FI-00076 AALTO, Finland*

## I. RECAP FROM PREVIOUS LECTURE



- Reflection and transmission coefficients

$$\Gamma_V = \frac{Z_l - Z_0}{Z_l + Z_0} = -\Gamma_I \quad (1)$$

- Average power delivered to the load

$\overline{P}_\ell = \frac{1}{2} \text{Re}[V(\ell)I^*(\ell)]$ , where the  $1/2$  comes from the fact that the field is harmonic.

$$\overline{P}_\ell = \frac{1}{2Z_0} \cdot |V^+ e^{-\gamma\ell}|^2 (1 - |\Gamma_V|^2) . \quad (2)$$

- VSWR


$$VSWR = \frac{1 + |\Gamma_V|}{1 - |\Gamma_V|} . \quad (3)$$

- Input impedance

$$Z_{in} = Z_0 \cdot \frac{Z_l + Z_0 \tanh \gamma\ell}{Z_0 + Z_l \tanh \gamma\ell} . \quad (4)$$

## II. EXAMPLES OF LOADS (TERMINATIONS)


### 1. Matched Load

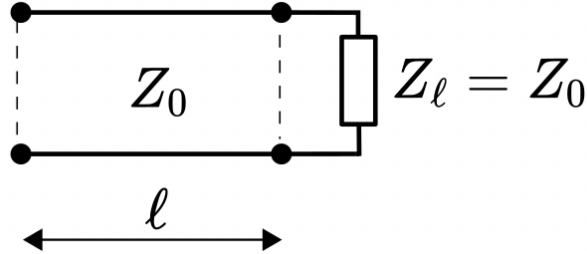

$$Z_\ell = Z_0 \implies \Gamma_V \equiv \frac{Z_\ell - Z_0}{Z_\ell + Z_0} = 0 \quad \text{No reflection!}$$

VSWR = 1,  $Z_{in} = Z_0$ ,  $P_\ell = \frac{1}{2Z_0}|V^+|^2 e^{-2\alpha\ell}$  — power delivered is maximum.  
This is only obtained if  $\alpha \neq 0$ .


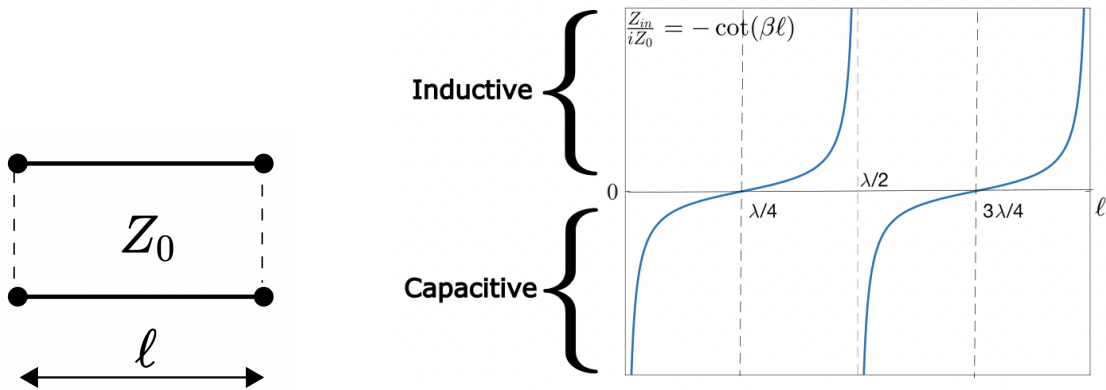
### 2. Open-Circuit $Z_\ell = \infty \implies \Gamma_V = \frac{Z_\ell - Z_0}{Z_\ell + Z_0} = 1$



VSWR =  $\infty$ ,  $Z_{in} = Z_0 \coth \gamma\ell$ ,  $P_\ell = 0$  — Compare this with the DC-case where all the input power is delivered!

For  $\alpha = 0$  (lossless),  $Z_{in} = -iZ_0 \cot \frac{2\pi\ell}{\lambda}$  if  $\ell = \frac{\lambda}{4}$ ,  $Z_{in} = 0$ , so the open line will look as a shortcut!
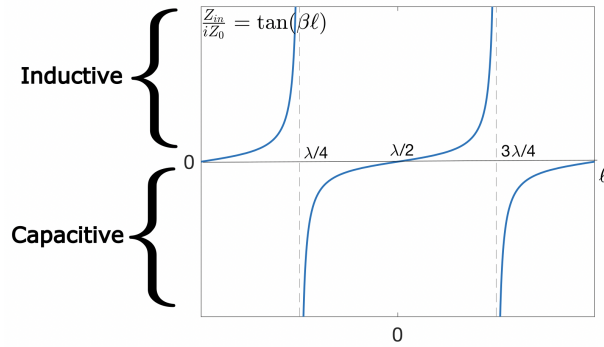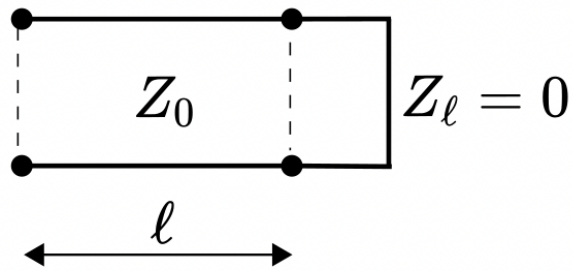
### 3. Short-circuit $Z_\ell = 0 \implies \Gamma_V = \frac{Z_\ell - Z_0}{Z_\ell + Z_0} = -1$ ,




$$\text{VSWR} = \infty, \quad Z_{in} = Z_0 \tanh \gamma\ell, \quad P_\ell = 0.$$

For  $\alpha = 0$  (lossless),  $\beta = \frac{2\pi}{\lambda}$  and  $Z_{in} = iZ_0 \tan \frac{2\pi\ell}{\lambda}$  — If  $\ell = \frac{\lambda}{4}$ ,  $Z_{in} = \infty$ , so the shorted line looks like an infinite impedance to a source! (even if the resistance of the wire is zero!)
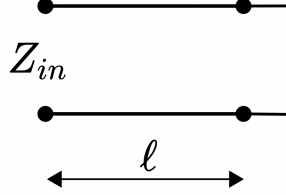
### III. RESONATORS FROM TRANSMISSION LINES

It is possible to make resonators from transmission lines, 3D cavities, etc. – The most usual case is the short-circuited transmission-line resonator.



$$Z_\ell = 0, \quad Z_{in} = Z_0 \tanh(\alpha\ell + i\beta\ell) = Z_0 \frac{\tanh \alpha\ell + i \tan \beta\ell}{1 + i \tan \beta\ell \tanh \alpha\ell}.$$

If losses are not too large,  $\alpha\ell \ll 1$ , we have  $\tanh \alpha\ell \approx \alpha\ell$ , so

$$Z_{in} = Z_0 \frac{\alpha\ell + i \tan \beta\ell}{1 + i\alpha\ell \tan \beta\ell}. \quad (5)$$

Now, recall from the previous lecture that  $\beta = \omega/v_p = \omega\sqrt{L'C'}$ ,  $v_p = 1/\sqrt{L'C'}$ ,  $Z_0 = \sqrt{L'/C'}$ ,

$\alpha = \frac{R'}{2}\sqrt{C'/L'}$ . We also take  $G' = 0$ .

We will consider  $\beta_0\ell = \pi$ , or  $\ell = \lambda_0/2$  as the resonance condition, leading to a resonance frequency  $\omega_0$ .

We can find this frequency from  $\frac{\omega_0}{v_p}\ell = \omega_0\sqrt{L'C'}\ell = \pi$ , so  $\omega_0 = \frac{\pi}{\ell\sqrt{L'C'}}$ . Let's check that everything is O.K.: so we get  $\omega_0 = 2\pi \times \nu_0$ , where  $\nu_0 = v_p/\lambda_0 = v_p/(2\ell) = \text{frequency of oscillation} = \text{inverse of period of oscillation}$ .

We can expand this around this point:  $\tan \beta\ell \simeq \tan\left(\pi + \pi\frac{\omega-\omega_0}{\omega_0}\right) = \tan \pi\frac{\omega-\omega_0}{\omega_0} \simeq \pi\frac{\omega-\omega_0}{\omega_0}$ , if  $|\omega - \omega_0| \ll \omega_0$ .


$$\begin{aligned} \text{So, } Z_{in} &= Z_0 \frac{\alpha\ell + i\pi\frac{\omega-\omega_0}{\omega_0}}{1 + \alpha\ell\pi\frac{\omega-\omega_0}{\omega_0}} \simeq Z_0(\alpha\ell + i\pi\frac{\omega-\omega_0}{\omega_0}) \\ &= \sqrt{L'/C'}(\frac{\ell}{2}R'\sqrt{C'/L'} + i\ell\sqrt{L'C'}(\omega - \omega_0)) = \frac{1}{2}R'\ell + iL'\ell(\omega - \omega_0). \end{aligned}$$

Suppose now that we look back at the series RLC circuit

$$Z = R + i\frac{L}{\omega}(\omega^2 - \omega_0^2) \simeq R + 2iL(\omega - \omega_0) \text{ near resonance, } \omega \simeq \omega_0.$$

Therefore, we can identify  $\underline{R = \frac{1}{2}R'\ell}$  and  $\underline{L = \frac{1}{2}L'\ell}$ .
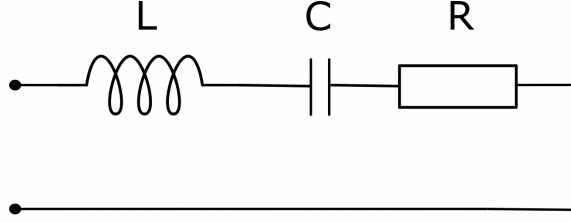
$$\text{Quality Factor } Q = \frac{\omega_0 L}{R} = \frac{\omega_0 L'}{R'} = \frac{\beta_0}{2\alpha}. \quad (6)$$



**Interesting question to think about:** Why do we get the factor 1/2 in the RLC equivalent above?

–Answer: Because the current in the short-circuited line is half a sinusoid, therefore we obtain only half of the total resistance and inductance of the full length  $\ell$ .

To see this explicitly, let us write the solution

$$\begin{cases} V(x) \simeq V^+ e^{-i\beta x} + V^- e^{i\beta x} \text{ — here we neglect } \alpha. \\ I(x) \simeq -\frac{\beta}{\omega L} (-V^+ e^{-i\beta x} + V^- e^{i\beta x}) \end{cases} \quad (7)$$

Since  $I(0) = 0 \implies V^+ \equiv V^-$  at this point (also you can see that  $\Gamma_V \equiv \frac{V^-}{V^+} e^{2i\beta_0 \ell} = -1$  and  $\beta_0 \ell = \pi$ ).

So

$$\begin{cases} V(x) = 2V^+ \cos \beta_0 x \\ I(x) = -\frac{2i\beta}{\omega L} V^+ \sin \beta_0 x = I^+ \sin \beta_0 x . \end{cases} \quad (8)$$

Therefore the magnetic-field energy:

$$\overline{W}_{L'} = \int_0^{\lambda_0/2} dx \cdot \frac{1}{4} L' |I(x)|^2 = \frac{1}{4} |I^+|^2 L' \int_0^{\lambda_0/2} \sin^2 \beta_0 x dx = \frac{\lambda_0}{16} \cdot |I^+|^2 L'. \quad (9)$$

At resonance:  $\overline{W}_{C'} = \overline{W}_{L'}$ , so

$$\overline{W} = \overline{W}_{C'} + \overline{W}_{L'} = \frac{\lambda_0}{8} L' |I^+|^2 . \quad (10)$$

$$\bar{P} = \frac{1}{2} \int_0^{\lambda_0} dx \cdot R' |I(x)|^2 = \frac{R'}{2} |I^+|^2 \int_0^{\lambda_0} \sin^2 \beta_0 x dx,$$

so

$$\bar{P} = \frac{\lambda_0}{8} R' |I^+|^2. \quad (11)$$

Therefore,

$$Q = \frac{\omega_0 \bar{W}}{\bar{P}} = \frac{\omega L'}{R'}, \quad (12)$$

or:  $Q = \frac{\pi}{\ell R'} \sqrt{\frac{L'}{C'}} = \frac{\pi Z_0}{\ell R'} = \frac{\pi}{2\ell\alpha}$ , where we used  $\alpha \simeq \frac{R}{2Z_0}$ ,  $\omega_0 = \frac{\pi}{\ell\sqrt{L'C'}}$ .

### References

- David M. Pozar — Microwave Engineering.
- R.E. Collin — Foundations for Microwave Engineering.