

EX 1 wye and delta connections

The phase voltage of a wye connected 3-phases source is $\bar{V}_{an} = 230\angle -40^\circ$. The source is feeding a delta connected 3-phases load, the impedance of which is $\bar{Z} = 10\angle -30^\circ$.

- a. Draw the circuit sketch of this situation
- b. calculate the line-to-line voltages of the source ($\bar{V}_{ab}, \bar{V}_{bc}, \bar{V}_{ca}$) and the phase currents of the load ($\bar{I}_{ab}, \bar{I}_{bc}, \bar{I}_{ca}$)

EX 2 impedances


The phase voltage of a wye connected 3-phases source is $\bar{V}_{an} = 230\angle 0^\circ$. The source is feeding a delta connected 3-phases load, the impedance of which is unknown. The measurement of the c-phase current gives $\bar{I}_c = 10\angle 75^\circ$. Calculate the load impedance, i.e., the impedance of one branch of the delta connected load.

EX 1 wye and delta connections

The phase voltage of a wye connected 3-phases source is $\bar{V}_{an} = 230\angle -40^\circ$. The source is feeding a delta connected 3-phases load, the impedance of which is $\bar{Z} = 10\angle -30^\circ$.

- c. Draw the circuit sketch of this situation.
- d. calculate the line-to-line voltages of the source ($\bar{V}_{ab}, \bar{V}_{bc}, \bar{V}_{ca}$) and the phase currents of the load ($\bar{I}_{ab}, \bar{I}_{bc}, \bar{I}_{ca}$)

Solution

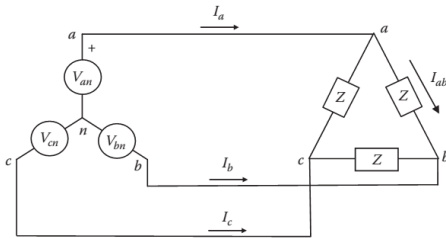

From the lecture slides, one can find an equation for the line-to-line voltage:

$$\begin{aligned} \bar{V}_{ab} &= \bar{V}_{an} - \bar{V}_{bn} \\ &= 230\angle -40^\circ - 230\angle (-40 - 120)^\circ \\ &= 398.4\angle -10^\circ \end{aligned}$$

$$\begin{aligned} \bar{V}_{bc} &= \bar{V}_{bn} - \bar{V}_{cn} \\ &= 230\angle (-40 - 120)^\circ - 230\angle (-40 - 240)^\circ \\ &= 398.4\angle -130^\circ \end{aligned}$$

$$\begin{aligned} \bar{V}_{ca} &= \bar{V}_{cn} - \bar{V}_{an} \\ &= 230\angle (-40 - 240)^\circ - 230\angle -40^\circ \\ &= 398.4\angle 110^\circ \end{aligned}$$

the angle of the line-to-line voltage ca could also be -250° ($-250+360=110$)

The currents are calculated from the voltage over the impedance, i.e.,

$$\begin{aligned} \bar{I}_{ab} &= \frac{\bar{V}_{ab}}{\bar{Z}} & \bar{I}_{bc} &= \frac{\bar{V}_{bc}}{\bar{Z}} & \bar{I}_{ca} &= \frac{\bar{V}_{ca}}{\bar{Z}} \\ &= \frac{398.4\angle -10^\circ}{10\angle -30^\circ} & &= \frac{398.4\angle -130^\circ}{10\angle -30^\circ} & &= \frac{398.4\angle 110^\circ}{10\angle -30^\circ} \\ &= 39.84\angle 20^\circ & &= 39.84\angle -100^\circ & &= 39.84\angle 140^\circ \end{aligned}$$

Note that the currents are also 120 degrees phase-shifted from each other.

EX 2: impedances

The phase voltage of a wye connected 3-phases source is $\bar{V}_{an} = 230\angle 0^\circ$. The source is feeding a delta connected 3-phases load, the impedance of which is unknown. The measurement of the c-phase current gives $\bar{I}_c = 10\angle 75^\circ$. Calculate the load impedance, i.e., the impedance of one branch of the delta connected load.

Solution

Let us first calculate the voltage over one of the branches of the delta-connected load, i.e., the line-to-line voltage, e.g.

$$\begin{aligned}\bar{V}_{ab} &= \sqrt{3}\bar{V}_{an}\angle 30^\circ \\ &= \sqrt{3}(230\angle 0^\circ)\angle 30^\circ \\ &= 398.4\angle 30^\circ\end{aligned}$$

The load current can be calculated from the source current as, e.g.,

$$\bar{I}_{ab} = \frac{\bar{I}_a\angle 30^\circ}{\sqrt{3}}, \text{ where}$$

$$\begin{aligned}\bar{I}_a &= \bar{I}_c\angle -120^\circ \\ &= (10\angle 75^\circ)\angle -120^\circ \\ &= 10\angle -45^\circ\end{aligned}$$

so that

$$\begin{aligned}\bar{I}_{ab} &= \frac{\bar{I}_a\angle 30^\circ}{\sqrt{3}} \\ &= \frac{(10\angle -45^\circ)\angle 30^\circ}{\sqrt{3}} \\ &= 5.77\angle -15^\circ\end{aligned}$$

The impedance can then be calculated as:

$$\begin{aligned}\bar{Z} &= \frac{\bar{V}_{ab}}{\bar{I}_{ab}} \\ &= \frac{398.4\angle 30^\circ}{5.77\angle -15^\circ} \\ &= 69.05\angle 45^\circ \Omega\end{aligned}$$