

**Problem 1:**

For the half-wave rectifier, the source is a sinusoid of 300 V rms at a frequency of 50 Hz. The load resistor is 25.

Determine

- a) the average load current
- b) the power absorbed by the load
- c) the apparent power supplied by the source
- d) the power factor of the circuit

**Problem 2:**

For the half-wave rectifier with R-L load,  $R=100\Omega$ ,  $L=0.1$  H,  $\omega=377$  rad/s, and  $V_m=100$ V.  $\beta=3.5$  rad

Determine

- a) expression for the current in this circuit,
- b) the average current,
- c) the rms current
- d) the power absorbed by the resistor, and
- e) the power factor.

**Problem 3:**

For a half wave rectifier, the source voltage is 120 V-RMS at 60 Hz. The load resistance is 5  $\Omega$ .

Determine

- a) Average load current.
- b) Average power absorbed by load
- c) Power factor.