

**ELEC-E8412**

Exercise No 04

Solution

**Problem 1:****Power Electronics**

02.11.2023

A single-phase full wave rectifier with resistive load of  $12 \Omega$  and AC source of  $120 V_{rms}$ , 60 Hz. Determine,


- a) The average, peak, and rms currents in the load and in each diode.

$$i_{o(avg)} = 2 * \frac{V_m}{\pi * R}$$

$$i_{o(avg)} = \frac{2 * 120 * \sqrt{2}}{3.14 * 12} = 9A$$

$$i_{D(avg)} = \frac{i_{o(avg)}}{2}$$

$$i_{D(avg)} = \frac{9}{2} = 4.5A$$

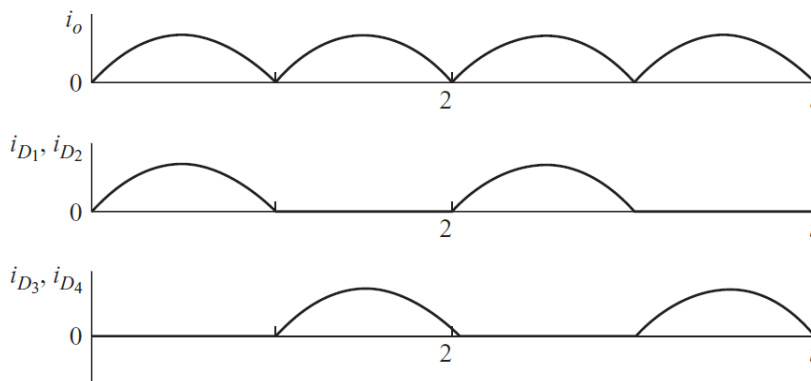

Peak load and diode current

$$i_{o(peak)} = i_{D(peak)} = \frac{V_m}{R} = \frac{120 * \sqrt{2}}{12} = 14.14 A$$

RMS load current

$$i_{o(rms)} = \frac{V_{rms}}{R} = \frac{120}{12} = 10 A$$

RMS diode current

$$i_{D(rms)} = \frac{i_{o(rms)}}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07A$$

- b) Determine the peak reverse voltage across each of the diodes.

When the diode is reverse biased the voltage across it is equal to the supply voltage, i.e.

$$V_D = V_m = V_{rms} * \sqrt{2} = 169.7V$$

**Problem 2:**

A single-phase full-wave rectifier with an ac source of  $200 \sin(\omega t)$  V has a resistive load of  $20 \Omega$ .  $\omega=377$ .

Determine

- a) Average current in the load and in each diode.

$$i_{o(avg)} = 2 * \frac{V_m}{\pi * R} = \frac{2 * 200}{3.14 * 20} = 6.366 \text{ A}$$

$$i_{D(avg)} = \frac{i_{o(avg)}}{2} = \frac{6.366}{2} = 3.18 \text{ A}$$

- b) Peak reverse voltage across each of the diodes.

When the diode is reverse biased the voltage across it is equal to the supply voltage

- c) Power factor

$$pf = \frac{P}{S} = \frac{i_{o(rms)}^2 * R}{V_{in(rms)} * i_{in(rms)}}$$

$$i_{o(rms)} = \frac{V_{rms}}{R} = \frac{200}{\sqrt{2} * 20} = 7.07 \text{ A}$$

$$pf = \frac{i_{o(rms)}^2 * R}{V_{in(rms)} * i_{in(rms)}} = \frac{(7.07)^2 * 20}{\frac{200}{\sqrt{2}} * 7.07} = 0.999 \cong 1$$

**Problem 3:**

For the controlled single-phase bridge rectifier has an  $18 \Omega$  resistive load and has a  $120 \text{ V}_{\text{rms}}$  at  $60 \text{ Hz}$  source. The delay angle  $\alpha$  is  $45^\circ$ .

Determine

a) average load current

$$i_{o(avg)} = \frac{V_{o(avg)}}{R} = \frac{V_m * (1 + \cos\alpha)}{\pi * R} = \frac{120 * \sqrt{2} * (1 + \cos 45^\circ)}{3.14 * 18} = 5.12 \text{ A}$$

b) rms load current

$$i_{o(rms)} = \frac{V_m}{R} * \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}} = \frac{120 * \sqrt{2}}{18} * \sqrt{\frac{1}{2} - \frac{0.785}{2\pi} + \frac{\sin 90^\circ}{4\pi}} = 6.35 \text{ A}$$

c) rms source current

The input and output RMS currents are same.

d) power factor

$$pf = \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}} = \sqrt{\frac{1}{2} - \frac{0.785}{2\pi} + \frac{\sin 90^\circ}{4\pi}} = 0.953$$

Or

$$pf = \frac{i_{o(rms)}^2 * R}{V_{in(rms)} * i_{in(rms)}} = \frac{(6.35)^2 * 18}{120 * 6.35} = 0.953$$

**Problem 4:**

A load of  $50 \Omega$  is connected to an AC source of 60 Hz,  $230 V_{\text{rms}}$ . Full wave-controlled rectifiers has a delay angle of 45 degrees.

Determine

a) Average load current

$$i_{o(avg)} = \frac{V_{o(avg)}}{R} = \frac{V_m * (1 + \cos\alpha)}{\pi * R} = \frac{230 * \sqrt{2} * (1 + \cos 45)}{3.14 * 50} = 3.53 A$$

b) Power absorbed by the load

$$P = i_{o(rms)}^2 * R$$

$$i_{o(rms)} = \frac{V_m}{R} * \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}} = \frac{230 * \sqrt{2}}{50} * \sqrt{\frac{1}{2} - \frac{0.785}{2\pi} + \frac{\sin 90}{4\pi}} = 3.99 A$$

c) Source VA.

$$S = V_{in(rms)} * i_{in(rms)} = 230 * 3.99 = 917.7 VA$$

**Problem 5:**

For an ideal full-wave rectifier with a 60-Hz ac source and maximum voltage of 100 V.

It is to supply a load that requires a dc voltage of 100 V and will draw 0.4 A.

Determine the filter capacitance required to limit the peak-to-peak output voltage ripple to 1 percent of the dc output.

$$\Delta V = \frac{V_m}{2 * f * R * C}$$

$$V = I * R, \quad R = \frac{100}{0.4} = 250 \Omega$$

$$C = \frac{V_m}{2 * f * R * \Delta V} = \frac{100}{2 * 60 * 250 * 0.01 * 100} = 3333 \mu F$$