

Problem 1:

A buck converter has an input of 12 V and an output of 3 V.
The load resistor is 6 Ω , the f_{sw} is 400 kHz, $L = 5 \mu\text{H}$, and $C = 10 \mu\text{F}$.

Determine

- duty ratio
- average and peak inductor currents
- average source current
- peak and average diode current

Problem 2:

A buck converter has an input of 50 V and an output of 25 V.
The f_{sw} is 100 kHz, and the output power to a load resistor is 125 W.

Determine

- duty ratio
- value of inductance to limit the peak inductor current to 6.25 A.
- minimum inductor current

Problem 3:

A boost converter circuit has the following parameters:

$$V_{in} = 5 \text{ V}, V_{out} = 20 \text{ V}, \text{ and } P_{out} = 40 \text{ W}, f_{sw} = 85 \text{ kHz}.$$

Minimum value of the inductor current must be at least 80% of the average inductor current.

Determine the duty ratio and the minimum inductor value.

Problem 4:

A boost converter circuit has the following parameters:

$$V_{in} = 20 \text{ V}, D = 0.6, R = 12.5 \Omega, L = 10 \mu\text{H}, C = 40 \mu\text{F}, f_{sw} = 200 \text{ kHz}.$$

Determine

- V_{out}
- Average, maximum, and minimum inductor currents.
- Average current in the diode