

Problem 1:

A buck converter has an input of 12 V and an output of 3 V.
The load resistor is 6 Ω, the f_{sw} is 400 kHz, $L = 5 \mu\text{H}$, and $C = 10 \mu\text{F}$.

Determine

a) duty ratio

$$D = \frac{V_o}{V_{in}} = \frac{3}{12} = 0.25$$

b) average and peak inductor currents

$$I_{avg} = \frac{(I_{max} + I_{min})}{2} = \frac{V_o}{R} = \frac{3}{6} = 0.5 \text{ A}$$

$$I_{max} = V_o \left(\frac{1}{R} + \frac{1-D}{2 * L * f} \right) = 3 \left(\frac{1}{6} + \frac{1-0.25}{2 * 5 * 10^{-6} * 4 * 10^5} \right) = 1.0625 \text{ A}$$

c) average source current

for an Ideal converter, $P_{in} = P_{out}$

$$P_{in} = \frac{V_o^2}{R} \quad V_{in} * I_{in} = \frac{V_o^2}{R}$$

$$I_{in} = \frac{V_o^2}{R * V_{in}} = \frac{3^2}{6 * 12} = 0.125 \text{ A}$$

d) peak and average diode current

$$I_{D(avg)} = I_{L(avg)} * (1 - D) = \frac{V_o}{R} * (1 - D) = \frac{3}{6} * (1 - 0.25) = 0.375 \text{ A}$$

$$I_{D(peak)} = I_{L(peak)} = I_{max} = 1.0625 \text{ A}$$

Problem 2:

A buck converter has an input of 50 V and an output of 25 V.
The f_{sw} is 100 kHz, and the output power to a load resistor is 125 W.
Determine

a) duty ratio

$$R = \frac{V_o^2}{P_{out}} = \frac{25^2}{125} = 5\Omega$$

a) duty ratio

$$D = \frac{V_o}{V_{in}} = \frac{25}{50} = 0.5$$

b) value of inductance to limit the peak inductor current to 6.25 A.

$$I_{max} = V_o \left(\frac{1}{R} + \frac{1-D}{2 * L * f} \right) = 25 \left(\frac{1}{5} + \frac{1-0.5}{2 * L * 10^5} \right)$$

$$I_{max} = 6.25 A \rightarrow L = 50 \mu H$$

c) minimum inductor current

$$I_{min} = V_o \left(\frac{1}{R} - \frac{1-D}{2 * L * f} \right) = 25 \left(\frac{1}{5} + \frac{1-0.5}{2 * 50 * 10^{-6} * 10^5} \right) = 3.75A$$

Problem 3:

A boost converter circuit has the following parameters:

$$V_{in} = 5 \text{ V}, V_{out} = 20 \text{ V}, \text{ and } P_{out} = 40 \text{ W}, f_{sw} = 85 \text{ kHz}.$$

Minimum value of the inductor current must be at least 80% of the average inductor current.

Determine the duty ratio and the minimum inductor value.

$$I_{min} > 0.8 I_{avg}$$

$$I_{min} = \left(\frac{V_{in}}{(1-D)^2 * R} \right) - \left(\frac{V_{in}}{2 * L} DT \right)$$

$$I_{max} = \left(\frac{V_{in}}{(1-D)^2 * R} \right) + \left(\frac{V_{in}}{2 * L} DT \right)$$

$$I_{avg} = \left(\frac{V_{in}}{(1-D)^2 * R} \right)$$

$$\left(\frac{V_{in}}{(1-D)^2 * R} \right) - \left(\frac{V_{in}}{2 * L} DT \right) > 0.8 * \left(\frac{V_{in}}{(1-D)^2 * R} \right)$$

$$\left(\frac{V_{in}}{(1-D)^2 * R} \right) - 0.8 * \left(\frac{V_{in}}{(1-D)^2 * R} \right) > \left(\frac{V_{in}}{2 * L} DT \right)$$

$$0.2 * \left(\frac{V_{in}}{(1-D)^2 * R} \right) > \left(\frac{V_{in}}{2 * L} DT \right)$$

After rearranging, we get

$$L > \frac{D * (1-D)^2 * R}{0.4 * f}$$

For D and R,

$$\frac{1}{1-D} = \frac{V_o}{V_{in}} = \frac{20}{5}, \quad D = 0.75$$

$$R = \frac{V_o^2}{P_{out}} = \frac{20^2}{40} = 10 \Omega$$

$$L > 13.79 \mu H$$

Problem 4:

A boost converter circuit has the following parameters:

$$V_{in}=20 \text{ V}, D=0.6, R=12.5 \ \Omega, L=10 \ \mu\text{H}, C=40 \ \mu\text{F}, f_{sw}=200 \ \text{kHz}.$$

Determine

a) V_{out}

$$V_o = \frac{V_{in}}{1-D} = \frac{20}{1-0.6} = 50V$$

b) **Average, maximum, and minimum inductor currents.**

$$I_{avg} = \frac{(I_{max} + I_{min})}{2} = \left(\frac{V_{in}}{(1-D)^2 * R} \right) = \left(\frac{20}{(1-0.6)^2 * 12.5} \right) = 10A$$

$$I_{min} = \left(\frac{V_{in}}{(1-D)^2 * R} \right) - \left(\frac{V_{in}}{2 * L} DT \right) = \left(\frac{20}{(1-0.6)^2 * 12.5} \right) - \frac{20 * 0.6}{2 * 10 * 10^{-6} * 2 * 10^5} = 7A$$

$$I_{max} = \left(\frac{V_{in}}{(1-D)^2 * R} \right) + \left(\frac{V_{in}}{2 * L} DT \right) = \left(\frac{20}{(1-0.6)^2 * 12.5} \right) + \frac{20 * 0.6}{2 * 10 * 10^{-6} * 2 * 10^5} = 13A$$

c) **Average current in the diode**

$$I_{D(avg)} = I_{L(avg)} * (1-D) = 10 * (1-0.6) = 4A$$

Or

$$I_{D(avg)} = \frac{V_o}{R} = \frac{50}{12.5} = 4A$$