

Problem 1:

A buck-boost converter circuit has the following parameters:

$$V_{in} = 24 \text{ V}, D = 0.65, R = 7.5 \text{ } \Omega, L = 50 \text{ } \mu\text{H}, C = 200 \text{ } \mu\text{F}, f_{sw} = 100 \text{ kHz.}$$

Determine

a) $V_{out} \quad V_o = \frac{V_{in} * D}{1 - D}$

b) **Average, maximum, and minimum inductor currents.**

$$I_{avg} = \left(\frac{V_{in} * D}{(1 - D)^2 * R} \right), \quad \Delta I_L = \left(\frac{V_{in} * D T}{L} \right), \quad I_{min} = I_{avg} - \frac{\Delta I_L}{2}, \quad I_{max} = I_{avg} + \frac{\Delta I_L}{2}$$

Problem 2:

A buck-boost converter circuit has the following parameters:

$$V_{in} = 12 \text{ V}, D = 0.6, R = 10 \text{ } \Omega, L = 10 \text{ } \mu\text{H}, C = 20 \text{ } \mu\text{F}, f_{sw} = 200 \text{ kHz.}$$

Determine

a) V_{out}

b) **Average, maximum, and minimum inductor currents.**

c) **Average value of input current**

$$V_{in} * I_{in(avg)} = \frac{V_o^2}{R} = \left(\frac{(V_{in} * D)^2}{(1 - D)^2 * R} \right)$$

Problem 3:

A square-wave inverter has a dc source of 125 V, an output frequency of 50 Hz, and an RL series load with $R = 12 \text{ } \Omega$ and $L = 35 \text{ mH}$. Determine

- a) expression for load current
- b) rms load current
- c) average source current

$$i_o(t) = \begin{cases} \frac{V_{in}}{R} + (I_{min} - \frac{V_{in}}{R})e^{-t/\tau} & 0 < t < \frac{T}{2} \\ -\frac{V_{in}}{R} + (I_{max} + \frac{V_{in}}{R})e^{-(t-T/2)/\tau} & \frac{T}{2} < t < T \end{cases}$$

$$I_{max} = -I_{min} = \frac{V_{in}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right)$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) d(t)} = \sqrt{\frac{2}{T} \int_0^{T/2} \left[\frac{V_{dc}}{R} + \left(I_{min} - \frac{V_{dc}}{R} \right) e^{-t/\tau} \right]^2 dt}$$