

Problem 1:

A buck-boost converter circuit has the following parameters:

$$V_{in} = 24 \text{ V}, D = 0.65, R = 7.5 \text{ } \Omega, L = 50 \text{ } \mu\text{H}, C = 200 \text{ } \mu\text{F}, f_{sw} = 100 \text{ kHz.}$$

Determine

a) V_{out}

$$V_o = \frac{V_{in} * D}{1 - D} = \frac{24}{1 - 0.65} = 44.571 \text{ V}$$

b) **Average, maximum, and minimum inductor currents.**

$$I_{avg} = \left(\frac{V_{in} * D}{(1 - D)^2 * R} \right) = \left(\frac{24 * 0.65}{(1 - 0.65)^2 * 7.5} \right) = 16.98 \text{ A}$$

$$\Delta I_L = \left(\frac{V_{in} * DT}{L} \right) = \frac{24 * 0.65}{50 * 10^{-6} * 10^5} = 3.12 \text{ A}$$

$$I_{min} = I_{avg} - \frac{\Delta I_L}{2} = 16.98 - \frac{3.12}{2} = 15.42 \text{ A}$$

$$I_{max} = I_{avg} + \frac{\Delta I_L}{2} = 16.98 + \frac{3.12}{2} = 18.54 \text{ A}$$

Problem 2:

A buck-boost converter circuit has the following parameters:

$$V_{in} = 12 \text{ V}, D = 0.6, R = 10 \text{ } \Omega, L = 10 \text{ } \mu\text{H}, C = 20 \text{ } \mu\text{F}, f_{sw} = 200 \text{ kHz.}$$

Determine

a) V_{out}

$$V_o = \frac{V_{in} * D}{1 - D} = \frac{12 * 0,6}{1 - 0.6} = 18V$$

b) **Average, maximum, and minimum inductor currents.**

$$I_{avg} = \left(\frac{V_{in} * D}{(1 - D)^2 * R} \right) = \left(\frac{12 * 0.6}{(1 - 0.6)^2 * 10} \right) = 4.5A$$

$$\Delta I_L = \left(\frac{V_{in} * DT}{L} \right) = \frac{12 * 0.6}{10 * 10^{-6} * 2 * 10^5} = 3.6A$$

$$I_{min} = I_{avg} - \frac{\Delta I_L}{2} = 4.5 - \frac{3.6}{2} = 2.7A$$

$$I_{max} = I_{avg} + \frac{\Delta I_L}{2} = 4.5 + \frac{3.6}{2} = 6.3A$$

c) **Average value of input current**

$$I_{in(avg)} = ?$$

$$V_{in} * I_{in(avg)} = \frac{V_o^2}{R} = \left(\frac{(V_{in} * D)^2}{(1 - D)^2 * R} \right)$$

$$I_{in(avg)} = \frac{V_o^2}{R} = \left(\frac{(V_{in} * D)^2}{(1 - D)^2 * R * V_{in}} \right) = \frac{0.6^2 * 12}{(1 - 0.6)^2 * 10 * 12} = 2.7A$$

Problem 3:

A square-wave inverter has a dc source of 125 V, an output frequency of 50 Hz, and an RL series load with $R=12\ \Omega$ and $L=35\ \text{mH}$. Determine

- expression for load current
- rms load current
- average source current

$$i_o(t) = \begin{cases} \frac{V_{in}}{R} + (I_{min} - \frac{V_{in}}{R})e^{-t/\tau} & 0 < t < \frac{T}{2} \\ -\frac{V_{in}}{R} + (I_{max} + \frac{V_{in}}{R})e^{-(t-\frac{T}{2})/\tau} & \frac{T}{2} < t < T \end{cases}$$

$$T = \frac{1}{f} = \frac{1}{50} = 0.02\ \text{s}$$

$$I_{max} = -I_{min} = \frac{V_{in}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right)$$

$$\tau = \frac{L}{R} = \frac{0.035}{12} = 0.00292$$

$$\frac{T}{2\tau} = \frac{0.02}{2 * 0.00292} = 3.425$$

- expression for load current

$$I_{max} = -I_{min} = \frac{V_{in}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right) = \frac{125}{12} \left(\frac{1 - e^{-3.425}}{1 + e^{-3.425}} \right) = 9.76\ \text{A}$$

$$\begin{aligned} i_o(t) &= \frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-t/\tau} = \frac{125}{12} + \left(-9.76 - \frac{125}{12} \right) e^{-t/0.00292} \\ &= 10.417 - 20.177 e^{-t/0.00292} \quad 0 \leq t \leq \frac{1}{100} \end{aligned}$$

$$\begin{aligned} i_o(t) &= \frac{-V_{in}}{R} + \left(I_{max} + \frac{V_{in}}{R} \right) e^{-(t-\frac{T}{2})/\tau} = \frac{-125}{12} + \left(9.76 + \frac{125}{12} \right) e^{-(t-0.01)/0.00292} \\ &= -10.417 + 20.177 e^{-(t-0.01)/0.00292} \quad \frac{1}{100} \leq t \leq \frac{1}{50} \end{aligned}$$

b) rms load current

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{2}{T} \int_0^{T/2} \left[\frac{V_{\text{dc}}}{R} + \left(I_{\text{min}} - \frac{V_{\text{dc}}}{R} \right) e^{-t/\tau} \right]^2 dt}$$

$$I_{\text{rms}} = \sqrt{\frac{2}{T} \int_0^{T/2} \left(\frac{V_{\text{in}}}{R} + \left(I_{\text{min}} - \frac{V_{\text{in}}}{R} \right) e^{-t/\tau} \right)^2 dt} = \sqrt{100 \int_0^{0.01} (10.417 - 20.177e^{-t/0.00292})^2 dt}$$
$$= 7.0143 \text{ A}$$

c) average source current

$$I_{\text{in}} = \frac{p_{\text{in}}}{V_{\text{in}}}$$

$$p_{\text{in}} = p_{\text{out}} = RI_{\text{rms}}^2 = 12 * (7.0143)^2 = 590.4 \text{ W}$$

$$I_{\text{in}} = \frac{p_{\text{in}}}{V_{\text{in}}} = \frac{590.4}{125} = 4.72 \text{ A}$$