

d. The phase angle θ between p_r and u_r may be found from Eq. (2.64).

$$\theta = 90^\circ - \tan^{-1} kr = 90^\circ - 79.6^\circ = 10.4^\circ$$

e. The energy density is given by Eq. (2.84).

$$D_{\text{avg}} = \frac{|p_r|^2}{\rho_0 c^2} \left(1 + \frac{1}{2k^2 r^2} \right) = \frac{360}{1.4 \times 10^5} \left(1 + \frac{1}{2 \times 29.8} \right) \\ = 2.62 \times 10^{-3} \text{ watt-sec/m}^3$$

f. The sound pressure level is found from Eq. (1.18).

$$\text{SPL} = 20 \log_{10} \frac{18.97}{2 \times 10^{-5}} \\ = 119.5 \text{ db } re 2 \times 10^{-5} \text{ newton/m}^2 \text{ (} re 2 \times 10^{-4} \text{ microbar)}$$

This sound pressure level is about 15 db higher than the highest level that is measured at 25 ft above a full symphony orchestra. In other words, 1 watt of acoustic power creates a very high sound pressure level at 1 ft from the source.

CHAPTER 3

ELECTRO-MECHANO-ACOUSTICAL CIRCUITS

PART VI Mechanical Circuits

3.1. Introduction. The subject of electro-mechano-acoustics (sometimes called dynamical analogies) is the application of electrical-circuit theory to the solution of mechanical and acoustical problems. In classical mechanics, vibrational phenomena are represented entirely by differential equations. This situation existed also early in the history of telephony and radio. As telephone and radio communication developed, it became obvious that a schematic representation of the elements and their interconnections was valuable. These schematic diagrams made it possible for engineers to visualize the performance of a circuit without laboriously solving its equations. The performance of radio and television systems can be studied from a single sheet of paper when such schematic diagrams are used. Such a study would have been hopelessly difficult if only the equations of the system were available.

There is another important advantage of a schematic diagram besides its usefulness in visualizing the system. Often one has a piece of equipment for which he desires the differential equations. The schematic diagram may then be drawn from visual inspection of the equipment. Following this, the differential equations may be formed directly from the schematic diagrams. Most engineers are trained to follow this procedure rather than to attempt to formulate the differential equations directly.

Schematic diagrams have their simplest applications in circuits that contain lumped elements, *i.e.*, where the only independent variable is time. In distributed systems, which are common in acoustics, there may be as many as three space variables and a time variable. Here, a schematic diagram becomes more complicated to visualize than the differential equations, and the classical theory comes into its own again. There are many problems in acoustics, however, in which the elements are lumped and the schematic diagram may be used to good advantage.

Four principal requirements are fulfilled by the methods used in this text to establish schematic representations for acoustic and mechanical devices. They are:

1. The methods must permit the formation of schematic diagrams from visual inspection of devices.
2. They must be capable of such manipulation as will make possible the combination of electrical, mechanical, and acoustical elements into one schematic diagram.
3. They must preserve the identity of each element in combined circuits so that one can recognize immediately a force, voltage, mass, inductance, and so on.
4. They must use the familiar symbols and the rules of manipulation for electrical circuits.

Several methods that have been devised fulfill one or two of the above four requirements, but not all four. A purpose of this chapter is to present a new method for handling combined electrical, mechanical, and acoustic systems. It incorporates the good features of previous theories and also fulfills the above four requirements. The symbols used conform with those of earlier texts wherever possible.¹⁻⁵

3.2. Physical and Mathematical Meanings of Circuit Elements. The circuit elements we shall use in forming a schematic diagram are those of electrical-circuit theory. These elements and their mathematical meaning are tabulated in Table 3.1 and should be learned at this time. There are generators of two types. There are four types of circuit elements: resistance, capacitance, inductance, and transformation. There are three generic quantities: (a) the drop across the circuit element; (b) the flow through the circuit element; and (c) the magnitude of the circuit element.†

Attention should be paid to the fact that the quantity a is not restricted to voltage e , nor b to electrical current i . In some problems a will represent force f , or velocity u , or pressure p , or volume velocity U . In those cases b will represent, respectively, velocity u , or force f , or volume

¹ B. Geblishoj, "Electromechanical and Electroacoustical Analogies," Academy of Technical Sciences, Copenhagen, 1947.

² F. A. Firestone, A New Analogy between Mechanical and Electrical Systems, *J. Acoust. Soc. Amer.*, **4**: 249-267 (1933); The Mobility Method of Computing the Vibrations of Linear Mechanical and Acoustical Systems: Mechanical-electrical Analogies, *J. Appl. Phys.*, **9**: 373-387 (1938).

³ H. F. Olson, "Dynamical Analogies," D. Van Nostrand Company, Inc., New York, 1943.







⁴ W. P. Mason, Electrical and Mechanical Analogies, *Bell System Tech. J.*, **20**: 405-414 (1941).

⁵ A. Bloch, Electro-mechanical Analogies and Their Use for the Analysis of Mechanical and Electro-mechanical Systems, *J. Inst. Elec. Eng.*, **92**: 157-169 (1945).

† Among the four circuit elements, the first three are two-poles. This list is exhaustive. The transformation element is a four-pole. There are other lossless four-poles which one might have chosen in addition, $e.g.$, the ideal gyrator.

velocity U , or pressure p . Similarly, the quantity c might be any appropriate quantity such as mass, compliance, inductance, resistance, etc. The physical meaning of the circuit elements c depends on the way in which the quantities a and b are chosen, with the restriction that ab has the dimension of power in all cases. The complete array of alternatives is shown in Table 3.2.

TABLE 3.1. Mathematical and Physical Significance of Symbols

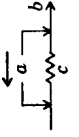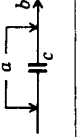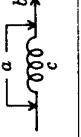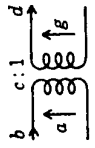Symbol	Name	Meaning	
		Transient	Steady-state
	Constant-drop generator	The quantity a is independent of what is connected to the generator. The arrow points to the positive terminal of the generator	
	Constant-flow generator	The quantity b is independent of what is connected to the generator. The arrow points in the direction of positive flow	
	Resistance-type element	$a = bc$	$a = bc$
	Capacitance-type element	$a = \frac{1}{c} \int b dt$	$a = \frac{b}{j\omega c}$
	Inductance-type element	$a = \frac{db}{dt}$	$a = j\omega cb$
	Transformation-type element	$a = cg$ $cb = d$ $\frac{a}{b} = c^2 \frac{g}{d}$	$a = cg$ $cb = d$ $\frac{a}{b} = c^2 \frac{g}{d}$

An important idea to fix in your mind is that the *mathematical operations associated with a given symbol are invariant*. If the element is of the inductance type, for example, the drop a across it is equal to the time derivative of the flow b through it multiplied by its size c . Note that this rule is not always followed in electrical-circuit theory because there conductance and resistance are often indiscriminately written beside the symbol for a resistance-type element. The invariant operations to be associated with each symbol are shown in columns 3 and 4 of Table 3.1.

Element	Electrical				Mechanical		Acoustical	
	a	b	e	i	f	p	U	d
Element		$c = R_E$	$c = \frac{1}{R_M} = r_M$	$c = R_Z$	$c = R_M$	$c = R_A$	$c = \frac{1}{R_V} = r_V$	$c = \frac{1}{Z_V} = \frac{d}{U} = v_Z = \frac{1}{Z_V}$
		$c = C_E$	$c = M_M$	$c = C_M$	$c = C_A$	$c = M_V$	$c = C_V$	$c = C_A$
		$c = L$	$c = C_M$	$c = M_M$	$c = M_A$	$c = M_V$	$c = M_V$	$c = C_A$
		$c = Z_E = \frac{1}{e}$	$c = Z_M = \frac{1}{f} = \frac{Z_M}{n}$	$c = Z_Z = \frac{1}{i} = \frac{Z_Z}{e}$	$c = Z_M = \frac{1}{f} = \frac{Z_M}{n}$	$c = Z_A = \frac{1}{d} = \frac{Z_A}{p}$	$c = Z_V = \frac{1}{d} = \frac{Z_V}{p}$	$c = Z_V = \frac{1}{d} = \frac{Z_V}{p}$

TABLE 3.2. Values for a, b, and c in Electrical, Mechanical, and Acoustical Circuits

† Preferred analogies.

3.3. Mechanical Circuits. Mechanical-circuit elements need not always be represented by electrical symbols. Since one frequently draws a mechanical circuit directly from inspection of the mechanical device, more obvious forms of mechanical elements are sometimes useful, at least until the student is thoroughly familiar with the analogous circuit. We shall accordingly devise a set of "mechanical" elements to be used as an introduction to the elements of Table 3.1.

TABLE 3.3. Conversion from Mobility-type Analogy to Impedance-type Analogy, or Vice Versa

Element	MECHANICAL ANALOGIES		ACOUSTICAL ANALOGIES	
	Mobility type	Impedance type	Mobility type	Impedance type
Infinite mechanical or acoustic impedance generator (zero mobility)				
Zero mechanical or acoustic impedance generator (infinite mobility)				
Dissipative element (resistance and responsiveness)				
Mass element				
Compliant element				
Impedance element				
Transformation element	 Mech. to acous. (mobility type)		 Mech. to acous. (impedance type)	

In electrical circuits, a voltage measurement is made by attaching the leads from a voltmeter across the two terminals of the element. Voltage is a quantity that we can measure without breaking into the circuit. To measure electric current, however, we must break into the circuit because this quantity acts *through* the element. In mechanical devices, on the other hand, we can measure the velocity (or the displacement) without disturbing the machine by using a capacitive or inertially operated vibration pickup to determine the quantity at any point on the machine. It is not velocity but force that is analogous to electric current. Force cannot be measured unless one breaks into the device.

It becomes apparent then that if a mechanical element is strictly analogous to an electrical element it must have a velocity difference appearing between (or across) its two terminals and a force acting through it. Analogously, also, the product of the rms force f in newtons and the in-phase component of the rms velocity u in meters per second is the power in watts. We shall call this type of analogy, in which a velocity corresponds to a voltage and a force to a current, the *mobility-type analogy*. It is also known as the "inverse" analogy.

Many texts teach in addition a "direct" analogy. It is the opposite of the mobility analogy in that force is made to correspond to voltage and velocity to current. In this text we shall call this kind of analogy an *impedance-type analogy*. To familiarize the student with both concepts, all examples will be given here both in mobility-type and impedance-type analogies.

Mechanical Impedance Z_M , and Mechanical Mobility z_M . The mechanical impedance is the complex ratio of force to velocity at a given point in a mechanical device. We commonly use the symbol Z_M for mechanical impedance, where the subscript M stands for "mechanical." The units are newton-seconds per meter, or mks mechanical ohms.

The mechanical mobility is the inverse of the mechanical impedance. It is the complex ratio of velocity to force at a given point in a mechanical device. We commonly use the symbol z_M for mechanical mobility. The units are meters per second per newton, or mks mechanical mohms.†

Mass M_M . Mass is that physical quantity which when acted on by a force is accelerated in direct proportion to that force. The unit is the kilogram. At first sight, mass appears to be a one-terminal quantity because only one connection is needed to set it in motion. However, the force acting on a mass and the resultant acceleration are reckoned with respect to the earth (inertial frame) so that in reality the second terminal of mass is the earth.

The mechanical symbol used to represent mass is shown in Fig. 3.1. The upper end of the mass moves with a velocity u with respect to the ground. The J-shaped configuration represents the "second" terminal of the mass and has zero velocity. The force can be measured by a suitable device inserted between the point 1 and the next element or generator connecting to it.

Mass M_M obeys Newton's second law that

$$f(t) = M_M \frac{du(t)}{dt} \tag{3.1}$$

† The word "mohm" stands for mobility ohm. The units are meters per second per newton.

where $f(t)$ is the instantaneous force in newtons, M_M is the mass in kilograms, and $u(t)$ is the instantaneous velocity in meters per second.

In the steady state [see Eqs. (2.33) to (2.35)], with an angular frequency ω equal to 2π times the frequency of vibration, we have the special case of Newton's second law,

$$f = j\omega M_M u \tag{3.2}$$

where $j = \sqrt{-1}$ as usual and f and u are rms complex quantities.

The mobility-type analogous symbol that we use as a replacement for the mechanical symbol in our circuits is a capacitance type. It is shown in Fig. 3.2a. The mathematical operation invariant for this symbol is found from Table 3.1. In the steady state we have

$$a = \frac{b}{j\omega c} \quad \text{or} \quad u = \frac{f}{j\omega M_M} \tag{3.3}$$

This equation is seen to satisfy the physical law given in Eq. (3.2). Note the similarity in appearance of the mechanical and analogous symbols in Figs. 3.1 and 3.2a. In electrical circuits the time integral of the current through a capacitor is charge. The analogous quantity here is the time integral of force, which is momentum.

The impedance-type analogous symbol for a mass is an inductance. It is shown in Fig. 3.2b. The invariant operation for steady state is $a = j\omega c b$ or $f = j\omega M_M u$. It also satisfies Eq. (3.2). Note, however, that in this analogy one side of the mass element is not necessarily grounded; this often leads to confusion. In electrical circuits the time integral of the voltage across an inductance is flux-turns. The analogous quantity here is momentum.

Mechanical Compliance C_M . A physical structure is said to be a mechanical compliance C_M if, when it is acted on by a force, it is displaced in direct proportion to the force. The unit is the meter per newton. Compliant elements usually have two apparent terminals.

The mechanical symbol used to represent a mechanical compliance is a spring. It is shown in Fig. 3.3. The upper end of the element moves with a velocity u_1 and the lower end with a velocity u_2 . The force required to produce the difference between the velocities u_1 and u_2 may be measured by breaking into the machine at either point 1 or point 2. Just as the same current would be measured at either end of an element in an electrical circuit, so the same force will be found here at either end of the compliant element.

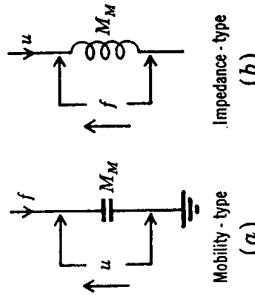


FIG. 3.2. (a) Mobility-type and (b) impedance-type symbols for a mass.

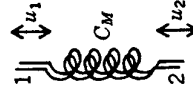


FIG. 3.3. Mechanical symbol for a mechanical compliance.

Mechanical compliance C_M obeys the following physical law,

$$a = \frac{1}{c} \int b dt \quad \text{or} \quad f(t) = \frac{1}{C_M} \int u(t) dt \quad (3.4)$$

where C_M is the mechanical compliance in meters per newton and $u(t)$ is the instantaneous velocity in meters per second equal to $u_1 - u_2$, the difference in velocity of the two ends.

In the steady state, with an angular frequency ω equal to 2π times the frequency of vibration, we have,

$$f = \frac{u}{j\omega C_M} \quad (3.5)$$

where f and u are taken to be rms complex quantities.

The mobility-type analogous symbol used as a replacement for the mechanical symbol in our circuits is an inductance. It is shown in Fig. 3.4a. The invariant mathematical operation that this symbol represents is given in Table 3.1. In the steady state we have

$$u = j\omega C_M f \quad (3.6)$$

In electrical circuits the time integral of the voltage across an inductance is flux-turns. The analogous quantity here is the time integral of velocity, which is displacement.

This equation satisfies the physical law given in Eq. (3.5). Note the similarity in appearance of the mechanical and analogous symbols in Figs. 3.3 and 3.4a.

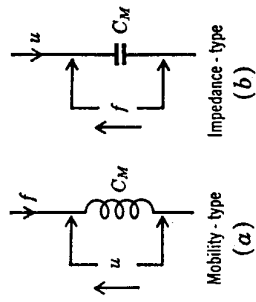


Fig. 3.4. (a) Mobility-type and (b) impedance-type symbols for a mechanical compliance.

The impedance-type analogous symbol for a mechanical compliance is a capacitance. It is shown in Fig. 3.4b. The invariant operation for steady state is $a = b/j\omega c$, or $f = u/j\omega C_M$. It also satisfies Eq. (3.5). In electrical circuits the time integral of the current through a capacitor is the charge. The analogous quantity here is the displacement.

Mechanical Resistance R_M , and *Mechanical Responsiveness r_M* . A physical structure is said to be a mechanical resistance R_M if, when it is acted on by a force, it moves with a velocity directly proportional to the force. The unit is the mks mechanical ohm.

We also define here a quantity r_M , the mechanical responsiveness, that is the reciprocal of R_M . The unit of responsiveness is the mks mechanical mohm.

The above representation for mechanical resistance is usually limited to viscous resistance. Frictional resistance is excluded because, for it, the ratio of force to velocity is not a constant. Both terminals of resistive elements can usually be located by visual inspection.

The mechanical element used to represent viscous resistance is the fluid dashpot shown schematically in Fig. 3.5. The upper end of the element moves with a velocity u_1 and the lower with a velocity u_2 . The force required to produce the difference between the two velocities u_1 and u_2 may be measured by breaking into the machine at either point 1 or point 2.

Mechanical resistance R_M obeys the following physical law,

$$f = R_M u = \frac{1}{r_M} u \quad (3.7)$$

where f is the force in newtons, u is the difference between the velocities u_1 and u_2 of the two ends, R_M is the mechanical resistance in mechanical ohms, *i.e.*, newtons/(meter per second), and r_M is the mechanical responsiveness in mks mechanical mohms, *i.e.*, meters per second per newton.

The mobility-type analogous symbol used to replace the mechanical symbol in our circuits is a resistance. It is shown in Fig. 3.6a. The

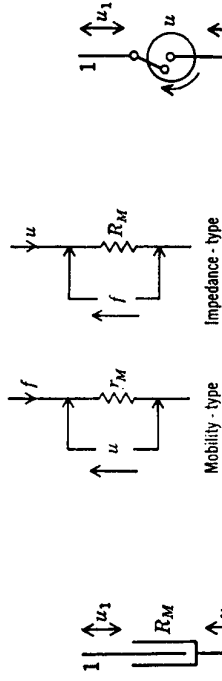


Fig. 3.5. Mechanical symbol for mechanical (viscous) resistance. (a) Mobility-type and (b) impedance-type symbols for a constant-velocity generator.

invariant mathematical operation that this symbol represents is given in Table 3.1. In either the steady or transient state we have

$$u = r_M f = \frac{1}{R_M} f \quad (3.8)$$

In the steady state u and f are taken to be rms complex quantities. This equation satisfies the physical law given in Eq. (3.7).

The impedance-type analogous symbol for a mechanical resistance is shown in Fig. 3.6b. It also satisfies Eq. (3.7).

Mechanical Generators. The mechanical generators considered will be one of two types, constant-velocity or constant-force. A *constant-velocity generator* is represented as a very strong motor attached to a shuttle mechanism in the manner shown in Fig. 3.7. The opposite ends of the generator have velocities u_1 and u_2 . One of these velocities, either u_1 or u_2 , is determined by factors external to the generator. The differ-

ence between the velocities u_1 and u_2 , however, is a velocity u that is independent of the external load connected to the generator.

The symbols that we used in the two analogies to replace the mechanical symbol for a constant-velocity generator are shown in Fig. 3.8. The invariant mathematical operations that these symbols represent are also given in Table 3.1. The tips of the arrows point to the "positive" terminals of the generators. The double circles in Fig. 3.8a indicate that the internal mobility of the generator is zero. The dashed line in Fig. 3.8b indicates that the internal impedance of the generator is infinite.

A *constant-force generator* is represented here by an electromagnetic transducer (e.g., a moving-coil loudspeaker) in the primary of which an electric current of constant amplitude is maintained. Such a generator produces a force equal to the product of the current i , the flux density B , and the effective length of the wire l cutting the flux ($f = Bli$). This device is shown schematically in Fig. 3.9. The opposite ends of the

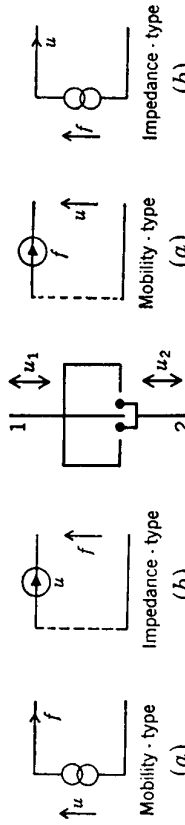


FIG. 3.8. (a) Mobility-type and (b) impedance-type symbols for a constant-velocity generator.

generator have velocities u_1 and u_2 that are determined by factors external to the generator. The force that the generator produces and that may be measured by breaking into the device at either point 1 or point 2 is a constant force, independent of what is connected to the generator.

The symbols used in the two analogies to replace the mechanical symbol for a constant-force generator are given in Fig. 3.10. The invariant mathematical operations that these symbols represent are also given in Table 3.1. The arrows point in the direction of positive flow. Here, the dashed line indicates infinite mobility, and the double circles indicate zero impedance.

Levers. SIMPLE LEVER. It is apparent that the lever is a device closely analogous to a transformer. The lever in its simplest form consists of a weightless bar resting on an immovable fulcrum, so arranged that a downward force on one end causes an upward force on the other end (see Fig. 3.11). From elementary physics we may write the equation of balance of moments around the fulcrum,

$$f_1 l_1 = f_2 l_2$$

or, if not balanced, assuming small displacements,

$$u_1 l_2 = u_2 l_1 \tag{3.9}$$

Also,

$$z_{M1} = \left(\frac{l_1}{l_2}\right)^2 z_{M2}$$

$$Z_{M1} = \left(\frac{l_2}{l_1}\right)^2 Z_{M2} \tag{3.10}$$

The above equations may be represented by the ideal transformers of Fig. 3.12, having a transformation ratio of $\left(\frac{l_1}{l_2}\right):1$ for the mobility type and $\left(\frac{l_2}{l_1}\right):1$ for the impedance type.

FLOATING LEVER. As an example of a simple floating lever, consider a weightless bar resting on a fulcrum that yields under force. The bar is

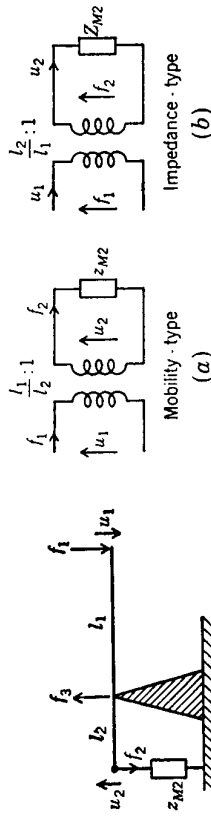


FIG. 3.11. Simple lever.

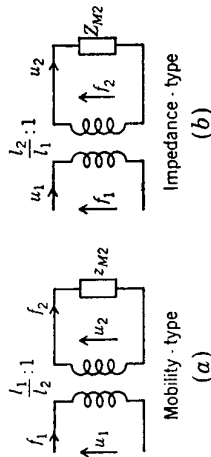


FIG. 3.12. (a) Mobility-type and (b) impedance-type symbols for a simple lever.

so arranged that a downward force on one end tends to produce an upward force on the other end. An example is shown in Fig. 3.13.

To solve this type of problem, we first write the equations of moments. Summing the moments about the center support gives

$$l_1 f_1 = l_2 f_2$$

and summing the moments about the end support gives

$$(l_1 + l_2) f_1 = l_2 f_3 \tag{3.11}$$

When the forces are not balanced, and if we assume infinitesimal displacements, the velocities are related to the forces through the mobilities, so that

$$u_3 = z_{M3} f_3 = z_{M3} \frac{l_1 + l_2}{l_2} f_1$$

$$u_2 = z_{M2} f_2 = z_{M2} \frac{l_1}{l_2} f_1 \tag{3.12}$$

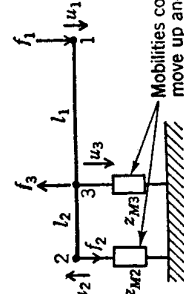


FIG. 3.13. Floating lever.

Also, by superposition, it is seen from simple geometry that

$$u'_1 = u_3 \frac{l_1 + l_2}{l_2} \quad \text{for } u_2 = 0$$

$$u''_1 = u_2 \frac{l_1}{l_2} \quad \text{for } u_3 = 0$$

so that

$$u_1 = u'_1 + u''_1 = \frac{l_1 + l_2}{l_2} u_3 + \frac{l_1}{l_2} u_2 \quad (3.13)$$

and, finally,

$$\frac{u_1}{f_1} = z_{M1} = z_{M3} \left(\frac{l_1 + l_2}{l_2} \right)^2 + z_{M2} \left(\frac{l_1}{l_2} \right)^2 \quad (3.14)$$

This equation may be represented by the analogous circuit of Fig. 3.14. The lever loads the generator with two mobilities connected in series, each of which behaves as a simple lever when the other is equal to zero. It will be seen that this is a way of obtaining the equivalent of two series masses without a common zero-velocity (ground) point. This will be illustrated in Example 3.3.

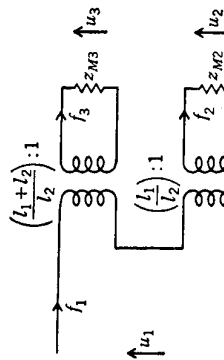


Fig. 3.14. Mobility-type symbol for a floating lever.

Example 3.1. The mechanical device of Fig. 3.15 consists of a piston of mass M_{M1} sliding on an oil surface inside a cylinder of mass M_{M2} . This cylinder in turn slides in an oiled groove cut in a rigid body. The sliding (viscous) resistances are R_{M1} and R_{M2} , respectively. The cylinder is held by a spring of compliance C_M . The mechanical generator maintains a constant sinusoidal velocity of angular frequency ω , whose rms magnitude is u m/sec. Solve for the force f produced by the generator.

Solution. Although the force will be determined ultimately from an analysis of the mobility-type analogous circuit for this mechanical device, it is frequently useful to draw a mechanical-circuit diagram. This interim step to the desired circuit will be especially helpful to the student who is inexperienced in the use of analogies. Its use virtually eliminates errors from the final circuit.

To draw the mechanical circuit, note first the junction points of two or more elements. This locates all element terminals which move with the same velocity. There are in this example two velocities, u and u_2 , in addition to "ground," or zero velocity. These two velocities are represented in the mechanical-circuit diagram by the velocities of two imaginary rigid bars, 1 and 2 of Fig. 3.16, which oscillate in a vertical direction. The circuit drawing is made by attaching all element terminals with velocity u to the first bar and all terminals with velocity u_2 to the second bar. All terminals with zero

velocity are drawn to a ground bar. Note that a mass always has one terminal on ground.† Three elements of Fig. 3.15 have one terminal with the velocity u : the generator, the mass M_{M1} , and the viscous resistance R_{M1} . These are attached to bar 1. Four elements have one terminal with the velocity u_2 : the viscous resistances R_{M2} and R_{M2} , the mass M_{M2} , and the compliance C_M . These are attached to bar 2. Five elements have one terminal with zero velocity: the generator, both masses, the viscous resistance R_{M2} , and the compliance C_M .

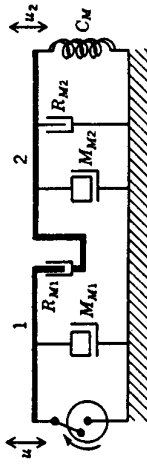


Fig. 3.16. Mechanical circuit for the device of Fig. 3.15.

We are now in a position to transform the mechanical circuit into a mobility-type analogous circuit. This is accomplished simply by replacing the mechanical elements with the analogous mobility-type elements. The circuit becomes that shown in Fig. 3.17. Remember that, in the mobility-type analogy, force "flows" through the elements and velocity is the drop across them. The resistors must have lower case r 's written alongside them. As defined above, $r_M = 1/R_M$, and the unit is the mks mechanical mohm.

The equations for this circuit are found in the usual manner, using the rules of Table 3.1. Let us determine $z_M = u/f$, the mechanical mobility presented to the

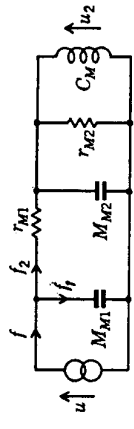


Fig. 3.17. Mobility-type analogous circuit for the device of Fig. 3.15.

generator. The mechanical mobility of the three elements in parallel on the right-hand side of the schematic diagram is

$$\begin{aligned} \frac{u_2}{f_2} &= \frac{1}{\frac{1}{j\omega M_{M2}} + \frac{1}{r_{M2}} + \frac{1}{j\omega C_M}} \\ &= \frac{1}{j\omega M_{M2} + R_{M2} + \frac{1}{j\omega C_M}} \end{aligned}$$

Including the element r_{M1} , the mechanical mobility for that part of the circuit through which f_2 flows is, then,

$$\frac{u}{f_2} = r_{M1} + \frac{1}{j\omega M_{M2} + R_{M2} + \frac{1}{j\omega C_M}}$$

Note that the input mechanical mobility z_M is given by

$$z_M = \frac{u}{f} = \frac{u}{f_1 + f_2}$$

† An exception to this rule may occur when the mechanical device embodies one or more floating levers, as we just learned.

and

$$f_1 = \frac{u}{1/j\omega M_{M1}} = j\omega M_{M1}u$$

Substituting f_1 and f_2 into the second equation preceding gives us the input mobility.

$$z_M = \frac{u}{f} = \frac{1}{j\omega M_{M1} + \frac{1}{\tau_{M1} + \frac{1}{j\omega M_{M2} + R_{M2} + \frac{1}{j\omega C_M}}}} \quad (3.15a)$$

The mechanical impedance is the reciprocal of Eq. (3.15a).

$$Z_M = \frac{f}{u} = j\omega M_{M1} + \frac{1}{\tau_{M1} + \frac{1}{j\omega M_{M2} + R_{M2} + \frac{1}{j\omega C_M}}} \quad (3.15b)$$

The result is

$$f = Z_M u \quad \text{newtons} \quad (3.16)$$

Example 3.2. As a further example of a mechanical circuit, let us consider the two masses of 2 and 4 kg shown in Fig. 3.18. They are assumed to rest on a frictionless

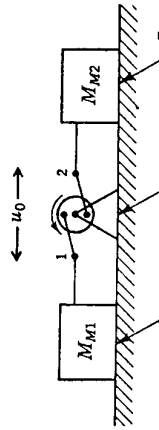


Fig. 3.18. Three-element mechanical device.

plane surface and to be connected together through a generator of constant velocity that is also free to slide on the frictionless plane surface. Let its velocity be

$$u_0 = 2 \cos 1000t \quad \text{cm/sec}$$

Draw the mobility-type analogous circuit, and determine the force f produced by the generator. Also, determine the mobility presented to the generator.

Solution. The masses do not have the same velocity with respect to ground. The difference between the velocities of the two masses is u_0 . The element representing a mass is that shown in Fig. 3.2a with one end grounded and the other moving at the velocity of the mass.

The mobility-type circuit for this example is shown in Fig. 3.19. The velocity u_0 equals $u_1 + u_3$, where u_1 is the velocity with respect to ground of M_{M1} , and u_2 is that for M_{M2} . The force f is

$$\begin{aligned} f_{rms} &= \frac{(u_0)_{rms}}{\frac{1}{j\omega M_{M1}} + \frac{1}{(1/j\omega M_{M2})}} \\ &= \frac{j\omega M_{M1} M_{M2} u_0}{M_{M1} + M_{M2}} \\ &= \frac{j1000 \times 2 \times 4 \times 0.02}{(2 + 4) \sqrt{2}} = j18.9 \text{ newtons} \end{aligned} \quad (3.17)$$

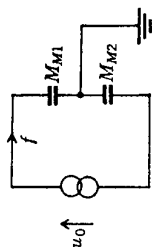


Fig. 3.19. Mobility-type analogous circuit for the device of Fig. 3.18.

The j indicates that the time phase of the force is 90° leading with respect to that of the velocity of the generator.

Obviously, when one mass is large compared with the other, the force is that necessary to move the smaller one alone. This example reveals the only type of case in which masses can be in series without the introduction of floating levers. At most, only two masses can be in series because a common ground is necessary. The mobility presented to the generator is

$$\begin{aligned} z_M &= \left(\frac{u_0}{f}\right)_{rms} = \frac{M_{M1} + M_{M2}}{j\omega M_{M1} M_{M2}} \\ &= \frac{1}{j1000 \times 8} = -j7.5 \times 10^{-4} \text{ mohms} \end{aligned} \quad (3.18)$$

Example 3.3. An example of a mechanical device embodying a floating lever is shown in Fig. 3.20. The masses attached at points 2 and 3 may be assumed to be

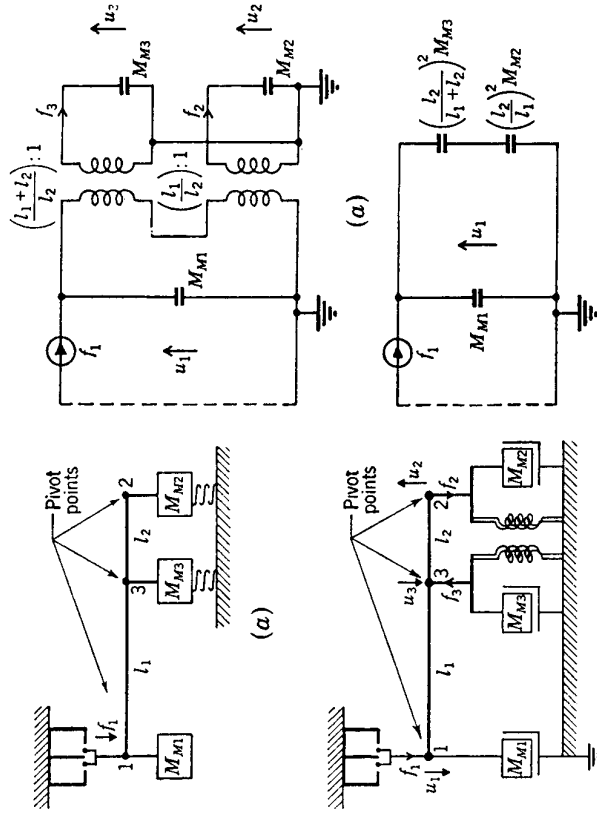


Fig. 3.20. (a) Mechanical device embodying a floating lever. (b) Mechanical diagram of (a). The compliances of the springs are very large so that all of f_2 and f_3 go to move M_{M2} and M_{M3} .

Fig. 3.21. (a) Mobility-type analogous circuit for the device of Fig. 3.20. (b) Same as (a) but with transformers removed.

resting on very compliant springs. The driving force f_1 will be assumed to have a frequency well above the resonance frequencies of the masses and their spring supports so that

$$\begin{aligned} z_{M2} &\doteq \frac{1}{j\omega M_{M2}} \\ z_{M3} &\doteq \frac{1}{j\omega M_{M3}} \end{aligned}$$

Also, assume that a mass is attached to the weightless lever bar at point 1, with a

mobility

$$z_{M1} = \frac{1}{j\omega M_{M1}}$$

Solve for the total mobility presented to the constant-force generator f_1 .

Solution. By inspection, the mobility-type analogous circuit is drawn as shown in Fig. 3.21*a* and *b*. Solving for $z_M = u_1/f_1$, we get

$$z_M = \frac{1}{j\omega \left[\frac{M_{M2}M_{M3}z^2}{M_{M3}l^2 + M_{M2}(l_1 + l_2)^2} + M_{M1} \right]} \quad (3.19)$$

Note that if $l_2 \rightarrow 0$, the mobility is simply that of the mass M_{M1} . Also, if $l_1 \rightarrow 0$, the mobility is that of M_{M1} and M_{M3} , that is,

$$z_M = \frac{1}{j\omega(M_{M3} + M_{M1})} \quad (3.20)$$

It is possible with one or more floating levers to have one or more masses with no ground terminal.

PART VII Acoustical Circuits


3.4. Acoustical Elements. Acoustical circuits are frequently more difficult to draw than mechanical ones because the elements are less easy to identify. As was the case for mechanical circuits, the more obvious forms of the elements will be useful as an intermediate step toward drawing the analogous circuit diagram. When the student is more familiar with acoustical circuits, he will be able to pass directly from the acoustic device to the final form of the equivalent circuit.

In acoustic devices, the quantity we are able to measure most easily without modification of the device is sound pressure. Such a measurement is made by inserting a small hollow probe tube into the sound field at the desired point. This probe tube leads to one side of a microphone diaphragm. The other side of the diaphragm is exposed to atmospheric pressure. A movement of the diaphragm takes place when there is a difference in pressure across it. This difference between atmospheric pressure and the pressure with the sound field is the sound pressure p .

Because we can measure sound pressure by such a probe-tube arrangement without disturbing the device, it seems that sound pressure is analogous to voltage in electrical circuits. Such a choice requires us to consider current as being analogous to some quantity which is proportional to velocity. As we shall show shortly, a good choice is to make current analogous to volume velocity, the volume of gas displaced per second.

A strong argument can be made for this choice of analogy when one considers the relations governing the flow of air inside such acoustic devices as loudspeakers, microphones, and noise filters. Inside a certain type of microphone, for example, there is an air cavity that connects to the outside air through a small tube (see Fig. 3.22). Assume, now, that the outer end of this tube is placed in a sound wave. The wave will cause a movement of the air particles in the tube. Obviously, there is a junction between the tube and the cavity at the inner end of the tube at point *A*. Let us ask ourselves the question, What physical quantities are continuous at this junction point?

First, the sound pressure just inside the tube at *A* is the same as that in the cavity just outside *A*. That is to say, we have continuity of sound pressure. Second, the quantity of air leaving the inner end of the small tube in a given interval of time is the quantity that enters the cavity in the same interval of time. That is, the mass per second of gas leaving the small tube equals the mass per second of gas entering the volume. Because the pressure is the same at both places, the density of the gas must also be the same, and it follows that there is continuity of volume velocity (cubic meters per second) at this junction. Analogously, in the case of electricity, there is continuity of electric current at a junction. Continuity of volume velocity must exist even if there are several tubes or cavities joining near one point. A violation of the law of conservation of mass otherwise would occur.

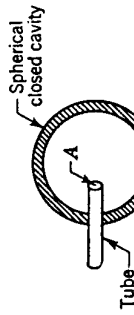


We conclude that the quantity that flows *through* our acoustical element must be the volume velocity U in cubic meters per second and the drop across our acoustical elements must be the pressure p in newtons per square meter. This conclusion indicates that the impedance type of analogy is the preferred analogy for acoustical circuits. The product of the effective sound pressure p times the in-phase component of the effective volume velocity U gives the acoustic power in watts.

In this part, we shall discuss the more general aspects of acoustical circuits. In Chap. 5 of this book, we explain fully the approximations involved and the rules for using the concepts enunciated here in practical problems.

Acoustic Mass M_A . Acoustic mass is a quantity proportional to mass but having the dimensions of kilograms per meter⁴. It is associated with a mass of air accelerated by a net force which acts to displace the gas without appreciably compressing it. The concept of acceleration without compression is an important one to remember. It will assist you in distinguishing acoustic masses from other elements.

The acoustical element that is used to represent an acoustic mass is a tube filled with the gas as shown in Fig. 3.23.

The physical law governing the motion of a mass that is acted on by a force is Newton's second law, $f(t) = M_M du(t)/dt$. This law may be expressed in acoustical terms as follows,



$$\frac{f(t)}{S} = \frac{M_M}{S} \frac{d[u(t)S]}{dt} = p(t) = \frac{M_M}{S^2} \frac{dU(t)}{dt} \tag{3.21}$$

or

$$p(t) = M_A \frac{dU(t)}{dt} \tag{3.21}$$

where $p(t)$ = instantaneous difference between pressures in newtons per square meter existing at each end of a mass of gas of M_M kg undergoing acceleration.

$M_A = M_M/S^2$ = acoustic mass in kilograms per meter⁴ of the gas undergoing acceleration. This quantity is nearly equal to the mass of the gas inside the containing tube divided by the square of the cross-sectional area. To be more exact we must note that the gas in the immediate vicinity of the ends of the tube also adds to the mass. Hence, there are "end corrections" which must be considered. These corrections are discussed in Chap. 5 (pages 132 to 139).

$U(t)$ = instantaneous volume velocity, of the gas in cubic meters per second across any cross-sectional plane in the tube. The volume velocity $U(t)$ is equal to the linear velocity $u(t)$ multiplied by the cross-sectional area S .

In the steady state, with an angular frequency ω , we have

$$p = j\omega M_A U \tag{3.22}$$

where p and U are taken to be rms complex quantities.

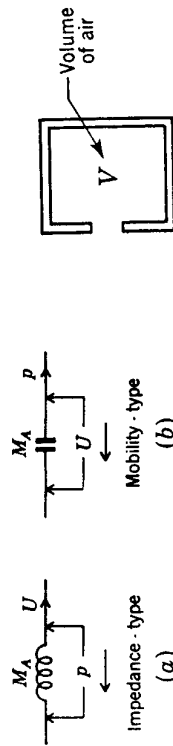


Fig. 3.24. (a) Impedance-type and (b) mobility-type symbols for an acoustic mass.

The impedance-type analogous symbol for acoustic mass is shown in Fig. 3.24a, and the mobility-type is given in Fig. 3.24b. In the steady state, for either, we get Eq. (3.22). The arrows point in the direction of positive flow or positive drop.

Acoustic Compliance C_A . Acoustic compliance is a constant quantity having the dimensions of meter⁵ per newton. It is associated with a volume of air that is compressed by a net force without an appreciable average displacement of the center of gravity of air in the volume. In other words, compression without acceleration identifies an acoustic compliance.

The acoustical element that is used to represent an acoustic compliance is a volume of air drawn as shown in Fig. 3.25.

The physical law governing the compression of a volume of air being acted on by a net force was given as $f(t) = (1/C_M)[u(t)dt]$. Converting from mechanical to acoustical terms,

$$\frac{f(t)}{S} = \frac{1}{C_M S} \int u(t) \frac{S}{S} dt \quad \text{or} \quad p(t) = \frac{1}{C_M S^2} \int U(t) dt \tag{3.23}$$

or

$$p(t) = \frac{1}{C_A} \int U(t) dt$$

where $p(t)$ = instantaneous pressure in newtons per square meter acting to compress the volume V of the air.

$C_A = C_M S^2$ = acoustic compliance in meters⁵ per newton of the volume of the air undergoing compression. The acoustic compliance is nearly equal to the volume of air divided by γP_0 , as we shall see in Chap. 5 (pages 128 to 131).

$U(t)$ = instantaneous volume velocity in cubic meters per second of the air flowing into the volume that is undergoing compression. The volume velocity $U(t)$ is equal to the linear velocity $u(t)$ multiplied by the cross-sectional area S .

In the steady state with an angular frequency ω , we have

$$p = \frac{U}{j\omega C_A} \tag{3.24}$$

where p and U are taken to be rms complex quantities.

The impedance-type analogous element for acoustic compliance is shown in Fig. 3.26a and the mobility-type in Fig. 3.26b. In the steady state for either, Eq. (3.24) applies.

Acoustic Resistance R_A , and *Acoustic Reactance* τ_A . Acoustic resistance R_A is associated with the dissipative losses occurring when there is a viscous movement of a quantity of gas through a fine-mesh screen or through a capillary tube. It is a constant quantity having the dimensions newton-seconds per meter⁵. The unit is the mks acoustic ohm.

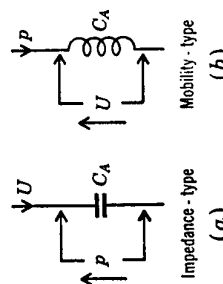


Fig. 3.26. (a) Impedance-type and (b) mobility-type symbols for an acoustic compliance.

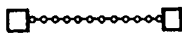


Fig. 3.27. Fine-mesh screen which serves as an acoustical symbol for acoustic resistance.

The acoustic element used to represent an acoustic resistance is a fine-mesh screen drawn as shown in Fig. 3.27.

The reciprocal of acoustic resistance is the acoustic responsiveness τ_A . The unit is the mks acoustic mohm with dimensions meter⁵ per second per newton.

The physical law governing dissipative effects in a mechanical system was given by $f(t) = R_M u(t)$, or, in terms of acoustical quantities,

$$p(t) = R_A U(t) = \frac{1}{\tau_A} U(t) \quad (3.25)$$

where $p(t)$ = difference between instantaneous pressures in newtons per square meter across the dissipative element. In the steady state p is an rms complex quantity.

$R_A = R_M/S^2$ = acoustic resistance in acoustic ohms, *i.e.*, newton-seconds per meter⁵.

$\tau_A = \tau_M S^2$ = acoustic responsiveness in acoustic mohms, *i.e.*, meter⁵ per newton-seconds.

$U(t)$ = instantaneous volume velocity in cubic meters per second of the gas through the cross-sectional area of resistance. In the steady state U is an rms quantity.

The impedance-type analogous symbol for acoustic resistance is shown in Fig. 3.28a and the mobility-type in Fig. 3.28b.

Acoustic Generators. Acoustic generators can be of either the constant-volume velocity or the constant-pressure type. The prime movers in our

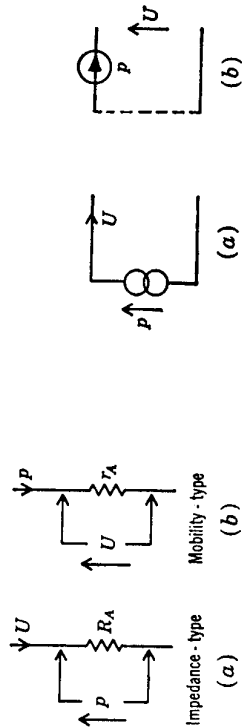


Fig. 3.28. (a) Impedance-type symbol for acoustic resistance and (b) mobility-type symbol for acoustic responsiveness. pressure generator.

acoustical circuits will be exactly like those shown in Figs. 3.7 and 3.9 except that u_2 often will be zero and u_1 will be the velocity of a small piston of area S . Remembering that $u = u_1 - u_2$, we see that the generator of Fig. 3.7 has a constant-volume velocity $U = uS$ and that of Fig. 3.9 a constant pressure of $p = f/S$.

The two types of analogous symbols for acoustic generators are given in Figs. 3.29 and 3.30. The arrows point in the direction of the positive

terminal or the positive flow. As before, the double circles indicate zero impedance or mobility and a dashed line infinite impedance or mobility.

Mechanical Rotational Systems. Mechanical rotational systems are handled in the same manner as mechanical rectilinear systems. The following quantities are analogous in the two systems.

<p><i>Rectilinear systems</i></p> <p>f = force, newtons</p> <p>v = velocity, m/sec</p> <p>ξ = displacement, m</p> <p>$Z_M = f/v$ = mechanical impedance, mks mechanical ohms</p> <p>$z_M = v/f$ = mechanical mobility, mks mechanical mohms</p> <p>R_M = mechanical resistance, mks mechanical ohms</p> <p>$r_M =$ mechanical responsiveness, mks mechanical mohms</p> <p>$M_M =$ mass, kg</p> <p>$C_M =$ mechanical compliance, m/newton</p> <p>$W_M =$ mechanical power, watts</p>	<p><i>Rotational systems</i></p> <p>T = torque, newton-m</p> <p>θ = angular velocity, radians/sec</p> <p>ϕ = angular displacement, radians</p> <p>$Z_R = T/\theta$ = rotational impedance, mks rotational ohms</p> <p>$z_R = \theta/T$ = rotational mobility, mks rotational mohms</p> <p>$R_R =$ rotational resistance, mks rotational ohms</p> <p>$r_R =$ rotational responsiveness, mks rotational mohms</p> <p>$I_R =$ moment of inertia, kg-m²</p> <p>$C_R =$ rotational compliance, radians/newton-m</p> <p>$W_R =$ rotational power, watts</p>
--	--

Example 3.4. The acoustic device of Fig. 3.31 consists of three cavities V_1, V_2 , and V_3 , two fine-mesh screens R_{A1} and R_{A2} , four short lengths of tube T_1, T_2, T_3 , and T_4 , and a constant-pressure generator. Because the air in the tubes is not confined, it

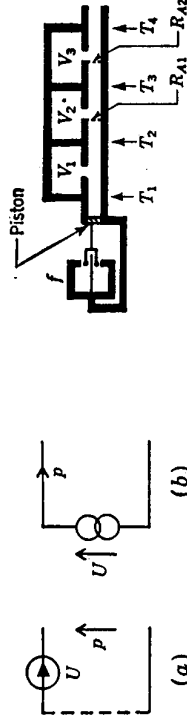


Fig. 3.30. (a) Impedance-type and (b) mobility-type symbols for a constant-volume velocity generator.

experiences negligible compression. Because the air in each of the cavities is confined, it experiences little average movement. Let the force of the generator be

$$f = 10^{-5} \cos 1000t \quad \text{newtons}$$

the radius of the tube $a = 0.5$ cm; the length of each of the four tubes $l = 5$ cm; the volume of each of the three cavities $V = 10$ cm³; and the magnitude of the two acoustic resistances $R_A = 10$ mks acoustic ohms. Neglecting end corrections, solve for the volume velocity U_0 at the end of the tube T_4 .

Solution. Remembering that there is continuity of volume velocity and pressure at the junctions, we can draw the impedance-type analogous circuit from inspection. It is shown in Fig. 3.32. The bottom line of the schematic diagram represents atmospheric pressure, which means that here the variational pressure p is equal to zero. At each of the junctions of the elements 1 to 4, a different variational pressure can be observed. The end of the fourth tube (T_4) opens to the atmosphere, which requires that M_{A4} be connected directly to the bottom line of Fig. 3.32.

Note that the volume velocity of the gas leaving the tube T_1 is equal to the sum

of the volume velocities of the gas entering V_1 and V_2 . The volume velocity of the gas leaving V_2 is the same as that flowing through the screen R_{A1} and is equal to the sum of the volume velocities of the gas entering V_2 and V_3 .

One test of the validity of an analogous circuit is its behavior for direct current. If one removes the piston and blows into the end of the tube T_1 (Fig. 3.31), a steady flow of air from T_4 is observed. Some resistance to this flow will be offered by the two screens R_{A1} and R_{A2} . Similarly in the schematic diagram of Fig. 3.32, a steady pressure p will produce a steady flow U through M_{A1} , resisted only by R_{A1} and R_{A2} .

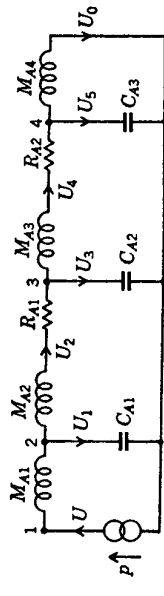


Fig. 3.32. Impedance-type analogous circuit for the acoustic device of Fig. 3.31.

As an aside, let us note that an acoustic compliance can occur in a circuit without one of the terminals being at ground potential only if it is produced by an elastic diaphragm. For example, if the resistance R_{A1} in Fig. 3.31 were replaced by an impervious but elastic diaphragm, the element R_{A1} in Fig. 3.32 would be replaced by a compliance-type element with both terminals above ground potential. In this case a steady flow of air could not be maintained through the device of Fig. 3.31, as can also be seen from the circuit of Fig. 3.32, with R_{A1} replaced by a compliance. Determine the element sizes of Fig. 3.32.

$$p = \frac{f}{S} = \frac{10^{-5} \cos 1000t}{\pi(5 \times 10^{-3})^2} = 0.1273 \cos 1000t \quad \text{newton/m}^2$$

$$M_{A1} = M_{A2} = M_{A3} = M_{A4} = M_{A4} = \frac{\rho d}{S} = \frac{1.18 \times 0.05}{7.85 \times 10^{-4}} = 750 \text{ kg/m}^4$$

$$C_{A1} = C_{A2} = C_{A3} = \frac{V}{\gamma P_0} = \frac{10^{-6}}{1.4 \times 10^5} = 7.15 \times 10^{-11} \text{ m}^5/\text{newton}$$

$$R_{A1} = R_{A2} = 10 \text{ mks acoustic ohms}$$

As is customary in electric-circuit theory, we solve for U_0 indirectly. First, arbitrarily let $U_0 = 1 \text{ m}^3/\text{sec}$, and determine the ratio p/U_0 .

$$p_4 = j\omega M_{A4} U_0 = j7.5 \times 10^5 \text{ newtons/m}^2$$

$$U_5 = j\omega C_{A3} p_4 = -5.36 \times 10^{-3} \text{ m}^3/\text{sec}$$

$$U_4 = U_5 + U_0 = 0.946$$

$$p_3 = (R_{A2} + j\omega M_{A3}) U_4 + p_4 = 9.46 + j14.6 \times 10^5$$

$$U_3 = j\omega C_{A2} p_3 = -0.1043 + j6.77 \times 10^{-7}$$

$$U_2 = U_3 + U_4 = 0.842 + j6.77 \times 10^{-7}$$

$$p_2 = (R_{A1} + j\omega M_{A2}) U_2 + p_3 = 17.37 + j2.091 \times 10^6$$

$$U_1 = j\omega C_{A1} p_2 = -0.1496 + j1.242 \times 10^{-6}$$

$$U = U_2 + U_1 = 0.692 + j1.919 \times 10^{-6}$$

$$p = j\omega M_{A1} U + p_2 = 15.93 + j2.61 \times 10^6 \quad \text{for } U_0 = 1$$

The desired value of U_0 is

$$U_0 = p \frac{U_0}{p} = \frac{0.1273 \cos 1000t}{15.93 + j2.61 \times 10^6}$$

$$\approx 4.88 \times 10^{-8} \cos(1000t - 90^\circ)$$

$$\approx 4.88 \times 10^{-8} \sin 1000t$$

In other words, the impedance is principally that of the four acoustic masses in series so that U_0 lags p by nearly 90° .

Example 3.5. A Helmholtz resonator is frequently used as a means for eliminating an undesired frequency component from an acoustic system. An example is given in Fig. 3.33a. A constant-force generator G produces a series of tones, among which is one that is not wanted. These tones actuate a microphone M whose acoustic impedance is 500 mks acoustic ohms. If the tube T has a cross-sectional area of 5 cm^2 , $l_1 = l_2 = 5 \text{ cm}$, $l_3 = 1 \text{ cm}$, $V = 1000 \text{ cm}^3$, and the cross-sectional area of l_4 is 2 cm^2 , what frequency is eliminated from the system?

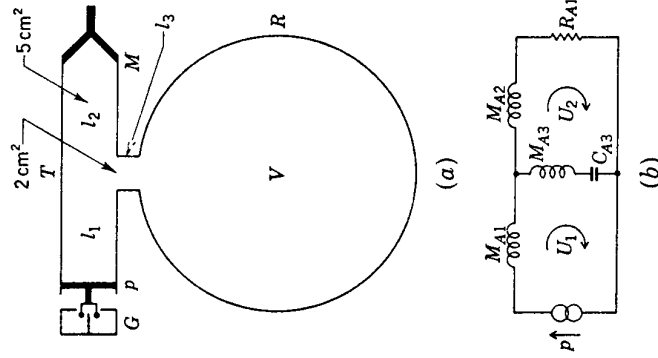


Fig. 3.33. (a) Acoustic device consisting of a constant-force generator G , piston P , tube T with length $l_1 + l_2$, microphone M , and Helmholtz resonator R with volume V and connecting tube as shown. (b) Impedance-type analogous circuit for the device of (a).

Solution. By inspection we may draw the impedance-type analogous circuit of Fig. 3.33b. The element sizes are

$$M_{A1} = M_{A2} = \frac{\rho d}{S^2} = \frac{1.18 \times 0.05}{5 \times 10^{-4}} = 118 \text{ kg/m}^4$$

$$M_{A3} = \frac{\rho l_3}{S_R} = \frac{1.18 \times 0.01}{2 \times 10^{-4}} = 59 \text{ kg/m}^4$$

$$C_{A3} = \frac{V}{\gamma P_0} = \frac{10^{-3}}{1.4 \times 10^5} = 7.15 \times 10^{-9} \text{ m}^5/\text{newton}$$

$$R_{A1} = 500 \text{ mks acoustic ohms}$$

It is obvious that the volume velocity U_2 of the transducer M will be zero when the shunt branch is at resonance. Hence,

$$\omega = \frac{1}{\sqrt{M_{A3} C_{A3}}} = \frac{10^4}{\sqrt{42.2}} = 1540 \text{ radians/sec}$$

$$f = 245 \text{ cps}$$

PART VIII Transducers

A transducer is defined as a device for converting energy from one form to another. Of importance in this text is the electromechanical transducer for converting electrical energy into mechanical energy, and vice versa. There are many types of such transducers. In acoustics we are concerned with microphones, earphones, loudspeakers, and vibration pickups and vibration producers which are generally linear passive reversible networks.

The type of electromechanical transducer chosen for each of these instruments depends upon such factors as the desired electrical and mechanical impedances, durability, and cost. It will not be possible here to discuss all means for electromechanical transduction. Instead we shall limit the discussion to electromagnetic and electrostatic types. Also, we shall deal with mechano-acoustic transducers for converting mechanical energy into acoustic energy.

3.5. Electromechanical Transducers. Two types of electromechanical transducers, electromagnetic and electrostatic, are commonly employed in loudspeakers and microphones. Both may be represented by transformers with properties that permit the joining of mechanical and electrical circuits into one schematic diagram.

Electromagnetic-mechanical Transducer. This type of transducer can be characterized by four terminals. Two have voltage and current associated with them. The other two have velocity and force as the measurable properties. Familiar examples are the moving-coil loudspeaker or microphone and the variable-reluctance earphone or microphone.

The simplest type of moving-coil transducer is a single length of wire in a uniform magnetic field as shown in Fig. 3.34. When a wire is moved upward with a velocity u as shown in Fig. 3.34a, a potential difference e will be produced in the wire such that terminal 2 is positive. If, on the other hand, the wire is fixed in the magnetic field (Fig. 3.34b) and a current i is caused to flow into terminal 2 (therefore, 2 is positive), a force will be produced that acts on the wire upward in the same direction as that indicated previously for the velocity.

The basic equations applicable to the moving-coil type of transducer are

$$f = Bli \quad (3.26a)$$

$$e = Blu \quad (3.26b)$$

where i = electrical current in amperes

f = "open-circuit" force in newtons produced on the mechanical circuit by the current i

B = magnetic-flux density in webers per square meter

l = effective length in meters of the electrical conductor that moves at right angles across the magnetic lines of force of flux density B

u = velocity in meters per second

e = "open-circuit" electrical voltage in volts produced by a velocity u

The right-hand sides of Eqs. (3.26) have the same sign because when u and f are in the same direction the electrical terminals have the same sign.

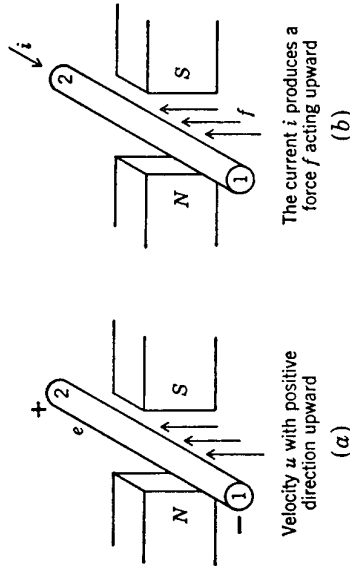


FIG. 3.34. Simplified form of moving-coil transducer consisting of a single length of wire cutting a magnetic field of flux density B . (a) The conductor is moving vertically at constant velocity so as to generate an open-circuit voltage across terminals 1 and 2. (b) A constant current is entering terminal 2 to produce a force on the conductor in a vertical direction.

The analogous symbol for this type of transducer is the "ideal" transformer given in Fig. 3.35. The "windings" on this ideal transformer have infinite impedance, and the transformer obeys Eqs. (3.26) at all frequencies, including steady flow.

The mechanical side of this symbol necessarily is of the mobility type if current flows in the primary. The invariant mathematical operations which this symbol represents are given in Table 3.1. They lead directly to Eqs. (3.26). The arrows point in the directions of positive flow or positive potential.

Electrostatic-mechanical Transducer. This type of transducer may also be characterized by four terminals. At two of them, voltages and currents can be measured. At the other two, forces and velocities can be measured. This transducer is satisfactorily described by the following mathematical relations,

$$e = -\tau \dot{x} \quad (3.27a)$$

$$f = \tau q \quad (3.27b)$$

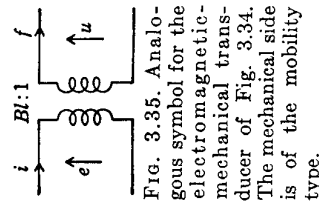


FIG. 3.35. Analogous symbol for the electromagnetic-mechanical transducer of Fig. 3.34. The mechanical side is of the mobility type.

where $e =$ "open-circuit" electrical voltage in volts produced by a displacement ξ .

$\xi =$ displacement in meters of a dimension of the piezoelectric device.

$q =$ electrical charge in coulombs stored in the dielectric of the piezoelectric device.

$f =$ "open-circuit" force in newtons produced by an electrical charge q .

$\tau =$ coupling coefficient† with dimensions of newtons per coulomb or volts per meter. It is a real number when the network is linear, passive, and reversible.

An example is a piezoelectric crystal microphone such as is shown in Fig. 3.36. A force applied uniformly over the face of the crystal causes an inward displacement of magnitude ξ . As a result of this displacement, a voltage e appears across the electrical terminals 1 and 2. Let us assume that a positive displacement (inward) of the crystal causes terminal 1 to become positive. For small displacements, the induced voltage is proportional to displacement. The inverse of this effect occurs when no external force acts on the crystal face but an electrical generator is connected to the terminals 1 and 2. If the external generator is connected so that terminal 1 is positive, an internal force f is produced which acts to expand the crystal. For small displacements, the developed force f is proportional to the electric charge q stored in the dielectric of the crystal.

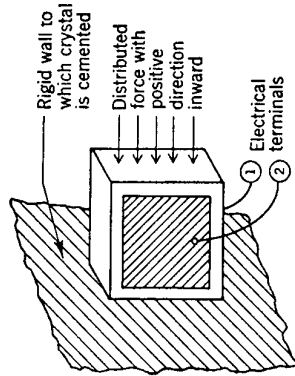


Fig. 3.36. Piezoelectric crystal transducer mounted on a rigid wall.

ments, the developed force f is proportional to the electric charge q stored in the dielectric of the crystal.

Equations (3.27) are often inconvenient to use because they contain charge and displacement. One prefers to deal with current and velocity, which appear directly in the equation for power. Conversion to current and velocity may be made by the relations

$$u = \frac{dq}{dt} = j\omega\xi \quad (3.28a)$$

$$i = \frac{dq}{dt} = j\omega q \quad (3.28b)$$

† The coupling coefficient is frequently defined differently in advanced texts on electrostatic-mechanical transducers. For example, in some texts it is defined as the square root of $C'_M C'_E \tau^2 \pi^2 / 8$, where C'_M and C'_E are defined after Eq. (3.37). The author does not intend that the definition for coupling coefficient in this text should be adopted as standard; rather, the term is used simply for convenience in the discussion.

so that Eqs. (3.27) become

$$e = -\frac{\tau}{j\omega} u \quad (3.29a)$$

$$f = \frac{\tau}{j\omega} i \quad (3.29b)$$

Unfortunately, the usual analogous symbol for this type of transformer is not as simple as that for the electromagnetic-mechanical type. Two possible forms are shown in Fig. 3.37. The mechanical sides are of the impedance-type analogy. Let us discuss Fig. 3.37a first.

The element C'_M is the mechanical compliance of the transducer. In order to measure C'_M , a sinusoidal driving force f is applied to the transducer terminals 3 and 4, and the resulting sinusoidal displacement is measured. During this measurement the electrical terminals are short-circuited ($e = 0$). A very low driving frequency is used so that the mass reactance and mechanical resistance can be neglected.

The element C'_E is the electrical capacitance of the crystal measured at low frequencies with the mechanical terminals open-circuited ($u = 0$). Application of a current i to the primary will produce a voltage across the condenser C'_E of $i/j\omega C'_E$. This in turn produces an open-circuit force

$$f = \frac{i}{j\omega C'_E} \tau C'_E = \frac{\tau i}{j\omega} \quad (3.30)$$

A velocity u applied at the secondary of the transducer by an external generator produces a current through the condenser C'_E equal to $-uC'_E$. This in turn generates an open-circuit voltage

$$e = -uC'_E \frac{1}{j\omega C'_E} = -\frac{\tau u}{j\omega} \quad (3.31)$$

Equations (3.30) and (3.31) are seen to equal Eqs. (3.29).

In Fig. 3.37b, C_M is also the mechanical compliance of the transducer, but measured in a different way. A sinusoidal driving force is applied to terminals 3 and 4 of the transducer at a very low frequency so that mass reactance and mechanical resistance can be neglected, and the resulting sinusoidal displacement is measured. During this measurement the electrical terminals 1 and 2 are open-circuited ($i = 0$). The element C_E is

the electrical capacitance measured at low frequencies with the mechanical terminals *short-circuited* ($f = 0$).

Application of a current i to the primary will produce a velocity across the compliance C_M equal to $C_M r i$. This velocity will produce an open-circuit force

$$f = \frac{\tau i}{j\omega} \quad (3.32)$$

A velocity u applied at the secondary of the transformer by an external generator produces a force across the compliance C_M equal to $-u/j\omega C_M$. This force will in turn generate a voltage across C_M equal to

$$e = -\frac{\tau u}{j\omega} \quad (3.33)$$

Equations (3.32) and (3.33) are seen to equal Eqs. (3.29). The transducers of Fig. 3.37 are identical. The elements in Fig. 3.37 are related by the equations

$$C'_B = \frac{C_B}{1 + C'_M C_B \tau^2} \quad (3.34)$$

$$C_M = \frac{C'_M}{1 + C'_M C_B \tau^2} \quad (3.35)$$

$$C_B = C'_B (1 + C'_M C_B \tau^2) \quad (3.36)$$

$$C'_M = C_M (1 + C_B C_M \tau^2) \quad (3.37)$$

where C'_B = electrical capacitance measured with the mechanical "terminals" blocked so that no motion occurs ($u = 0$)

C_B = electrical capacitance measured with the mechanical "terminals" operating into zero mechanical impedance so that no force is built up ($f = 0$)

C_M = mechanical compliance measured with the electrical terminals open-circuited ($i = 0$)

C'_M = mechanical compliance measured with the electrical terminals short-circuited ($e = 0$)

The choice between the alternative analogous symbols of Fig. 3.37 is usually made on the basis of the use to which the transducer will be put. If the electrostatic transducer is a microphone, it usually is operated into the grid of a vacuum tube so that the electrical terminals are essentially open-circuited. In this case the circuit of Fig. 3.37b is the better one to use, because C_B can be neglected in the analysis when $i = 0$. On the other hand, if the transducer is a loudspeaker, it usually is operated from a low-impedance amplifier so that the electrical terminals are essentially short-circuited. In this case the circuit of Fig. 3.37a is the one to use, because $C'_B \omega$ is small in comparison with the output admittance of the amplifier.

The circuit of Fig. 3.37a corresponds more closely to the physical facts

than does that of Fig. 3.37b. If the crystal could be held motionless ($u = 0$) when a voltage was impressed across terminals 1 and 2, there would be no stored mechanical energy. All the stored energy would be electrical. This is the case for circuit (a), but not for (b). In other respects the two circuits are identical.

At higher frequencies, the mass M_M and the resistance R_M of the crystal must be considered in the circuit. These elements can be added in series with terminal 3 of Fig. 3.37.

These analogous symbols indicate an important difference between electromagnetic and electrostatic types of coupling. For the electromagnetic case, we ordinarily use a mobility-type analogy, but for the electrostatic case we usually employ the impedance-type analogy.

In the next part we shall introduce a different method for handling electrostatic transducers. It involves the use of the mobility-type analog in place of the impedance-type analog. The simplification in analysis that results will be immediately apparent. By this new method it will also be possible to use the impedance-type analog for the electromagnetic case.

3.6. Mechano-acoustic Transducer. This type of transducer occurs at a junction point between the mechanical and acoustical parts of an analogous circuit. An example is the plane at which a loudspeaker diaphragm acts against the air. This transducer may also be characterized by four terminals. At two of the terminals, forces and velocities can be measured. At the other two, pressures and volume velocities can be measured. The basic equations applicable to the mechano-acoustic transducer are

$$f = Sp \quad (3.38a)$$

$$U = Su \quad (3.38b)$$

where f = force in newtons

p = pressure in newtons per square meter

U = volume velocity in cubic meters per second

u = velocity in meters per second

S = area in square meters

The analogous symbols for this type of transducer are given at the bottom of Table 3.3 (page 51). They are seen to lead directly to Eqs. (3.38).

3.7. Examples of Transducer Calculations

Example 3.6. An ideal moving-coil loudspeaker produces 2 watts of acoustic power into an acoustic load of 4×10^4 mks acoustic ohms when driven from an amplifier with a constant-voltage output of 1.0 volts. The area of the diaphragm is 100 cm². What open-circuit voltage will it produce when operated as a microphone with an rms diaphragm velocity of 10 cm/sec?

Solution. From Fig. 3.35 we see that, always,

$$e = \beta hu$$

The power dissipated W gives us the rms volume velocity of the diaphragm U .

$$U = \sqrt{\frac{W}{R_s}} = \sqrt{\frac{2}{4 \times 10^4}} = 7.07 \times 10^{-3} \text{ m}^3/\text{sec}$$

$$\mu = 0.707 \text{ m/sec}$$

$$Bf = \frac{e}{u} = \frac{1}{0.707} = 1.4 \text{ volts/m-sec}$$

Hence, the open-circuit voltage for an rms velocity of 0.1 m/sec is

$$e = 1.316 \times 0.1 = 0.1316 \text{ volt}$$

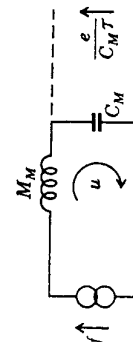


FIG. 3.38. Analogous circuit of the impedance type for a crystal microphone.

Example 3.7. An ammonium dihydrogen phosphate (ADP) crystal of the Z-cut expander bar type (discussed in Chap. 6) has the following mechanical and electrical properties:

- $\tau = 2 \times 10^8$ newtons/coulomb, or volts/m
- $C_M = 9.5 \times 10^{-8}$ m/newton
- $M_M = 1.47 \times 10^{-4}$ kg
- $C_E = 26 \times 10^{-12}$ farad
- $R_M =$ negligibly small

This crystal is to be used in a microphone with a circular (weightless) diaphragm. Determine the diameter of the diaphragm if the microphone is to yield an open-circuit voltage of -70 db re 1 volt for a sound pressure level of 74 db re 0.0002 microbar at 10,000 cps.

Solution. The circuit for this transducer with the transformer removed is shown in Fig. 3.38. Because only the open-circuit voltage is desired, C_E may be neglected in the calculations. f is the total force applied to the crystal by the diaphragm. Solving for e yields

$$e = \frac{fC_M \tau}{1 - \omega^2 C_M M_M}$$

The force f equals the area of the diaphragm S times the sound pressure p . Solving for p ,

$$p = 0.0002 \text{ antilog } 74/20$$

$$= 1 \text{ dyne/cm}^2 = 0.1 \text{ newton/m}^2$$

Solving for e ,

$$\frac{1}{e} = \text{antilog } \frac{70}{20} = 3.16 \times 10^3$$

or

$$e = 3.16 \times 10^{-4} \text{ volts}$$

Hence,

$$S = \frac{f}{p} = \frac{3.16 \times 10^{-4}(1 - 9.5 \times 10^{-4} \times 10^{-12} \times 6.28^2 \times 10^8)}{0.1 \times 19}$$

$$= 1.57 \times 10^{-4} \text{ m}^2$$

$$S = 1.57 \text{ cm}^2$$

This corresponds to a diaphragm with a diameter of about 1.41 cm.

Example 3.8. A loudspeaker diaphragm couples to the throat of an exponential horn that has an acoustic impedance of $300 + j300$ mks acoustic ohms. If the area of the loudspeaker diaphragm S_D is 0.08 m^2 , determine the mechanical-impedance load on the diaphragm due to the horn.

Solution. The analogous circuit is shown in Fig. 3.39. The mechanical impedance at terminals 1 and 2 represent the load on the diaphragm.

$$Z_M = \frac{f}{u} = S_D^2 (300 + j300)$$

$$= 6.4 \times 10^{-3}(300 + j300)$$

$$= 1.92 + j1.92 \text{ mks mechanical ohms}$$

PART IX Circuit Theorems, Energy, and Power

In this part we discuss conversions from one type of analogy to the other, Thévenin's theorem, energy and power relations, transducer impedances, and combinations of transducers.

3.8. Conversion from Mobility-type Analogies to Impedance-type Analogies. In the preceding parts we showed that electromagnetic and electrostatic transducers require two different types of analogy if they are to be represented by the networks shown in Table 3.1. A further need for two types of analogy is apparent from the standpoint of ease of drawing an analogous circuit by inspection. The mobility type of analogy is better for mechanical systems and the impedance type for acoustic systems. The circuits we shall use, however, will frequently contain electrical, mechanical, and acoustical elements. Since analogies cannot be mixed in a given circuit, we must have a simple means for converting from one to the other.

We may readily derive one analogy from the other if we recognize that:

1. Elements in series in the circuit of one analogy correspond to elements in parallel on the other.
2. Resistance-type elements become responsiveness-type elements, capacitance-type elements become inductance-type elements, and inductance-type elements become capacitance-type elements.
3. The sum of the drops across the series elements in a mesh of one analogy corresponds to the sum of the currents at a branch point of the other analogy.

This is equivalent to saying that one analogy is the *dual* of the other. In electrical-circuit theory one learns that the quantities that "flow" in one circuit are the same as the "drops" in the dual of that circuit. This is also true here.

To facilitate the conversion from one type of analogy to another, a method that we shall dub the "dot" method is used.⁶ Assume that we

⁶ M. F. Gardner and J. L. Barnes, "Transients in Linear Systems," pp. 46-49, John Wiley & Sons, Inc., New York, 1942.

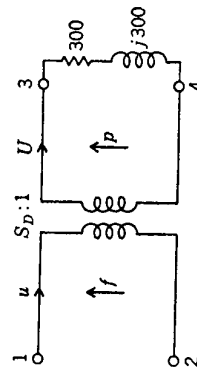


FIG. 3.39. Example of a mechano-acoustic transducer. The acoustic impedance of a horn (at terminals 3 and 4) loads the diaphragm with a mechanical impedance $S_D^2(300 + j300)$ mks mechanical ohms.

have the mobility-type analog of Fig. 3.17 and that we wish to convert it to an impedance-type analog. The procedure is as follows (see Fig. 3.40):

1. Place a dot at the center of each mesh of the circuit and one dot outside all meshes. Number these dots consecutively.
2. Connect the dots together with lines so that there is a line through each element and so that no line passes through more than one element.
3. Draw a new circuit such that each line connecting two dots now contains an element that is the inverse of that in the original circuit. The inverse of any given element may be seen by comparing corresponding

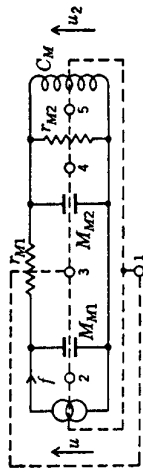


FIG. 3.40. Preparation by the "dot" method for taking the dual of Fig. 3.17.

columns for mobility-type analogies and impedance-type analogies of Table 3.3. The complete inversion (dual) of Fig. 3.40 is shown in Fig. 3.41.

4. Solving for the velocities or the forces in the two circuits using the rules of Table 3.1 will readily reveal that they give the same results.

After completing the formation of an analogous circuit, it is always profitable to ask concerning each element, If this element becomes very small or very large, does the circuit behave in the same way the device itself would behave? If the circuit behaves properly in the extremes, it is probably correct.

3.9. Thévenin's Theorem. It appears possible, from the foregoing discussions, to represent the operation of a transducer as a combination of electrical, mechanical, and acoustical elements. The connection between the electrical and mechanical circuit takes place through an electromechanical transducer. Similarly, the connection between the mechanical and acoustical circuit takes place through a mechano-acoustic transducer. A Thévenin's theorem may be written for the combined circuits, just as is written for electrical circuits only.

The requirements which must be satisfied in the proper statement and use of Thévenin's theorem are that all the elements be linear and there be no hysteresis effects.

In the next few paragraphs we shall demonstrate the application of Thévenin's theorem to a loudspeaker problem. The mechanical-radi-

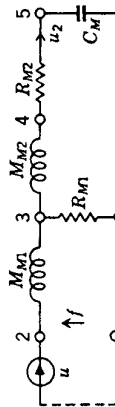


FIG. 3.41. Dual of the circuit of Fig. 3.40. Solving for the forces or velocities in this circuit using the rules of Table 3.1 yields the same values as solving for the forces or velocities in Fig. 3.40.

cal circuit takes place through an electromechanical transducer. Similarly, the connection between the mechanical and acoustical circuit takes place through a mechano-acoustic transducer. A Thévenin's theorem may be written for the combined circuits, just as is written for electrical circuits only.

The requirements which must be satisfied in the proper statement and use of Thévenin's theorem are that all the elements be linear and there be no hysteresis effects.

In the next few paragraphs we shall demonstrate the application of Thévenin's theorem to a loudspeaker problem. The mechanical-radi-

tion impedance presented by the air to the vibrating diaphragm of a loudspeaker or microphone will be represented simply as Z_{MR} in the impedance-type analogy or $z_{MR} = 1/Z_{MR}$ in the mobility-type analogy. The exact physical nature of Z_{MR} will be discussed in Chap. 5.

Assume a simple electromagnetic (moving-coil) loudspeaker with a diaphragm that has only mass and a voice coil that has only electrical resistance (see Fig. 3.42a). Let this loudspeaker be driven by a constant-voltage generator. By making use of Thévenin's theorem, we wish to find the equivalent mechanical generator u_0 and the equivalent mechanical mobility z_{MS} of the loudspeaker, as seen in the interface between the diaphragm and the air. The circuit of Fig. 3.42a with the transformer removed is shown in Fig. 3.42b. The Thévenin equivalent circuit is shown in Fig. 3.42c. We arrive at the values of u_0 and z_{MS} in two steps.

1. Determine the open-circuit velocity u_0 by terminating the loudspeaker in an infinite mobility, $z_{MA} = \infty$ (that is, $Z_{MA} = 0$) and then measuring the velocity of the diaphragm u_0 . As we discussed in Part II, $Z_{MA} = 0$ can be obtained by acoustically connecting the diaphragm to a tube whose length is equal to one-fourth wavelength. This is possible at low frequencies. Inspection of Fig. 3.42b shows

$$u_0 = \frac{eBl}{j\omega M_{MD}R_E + (Bl)^2} \quad (3.39)$$

that

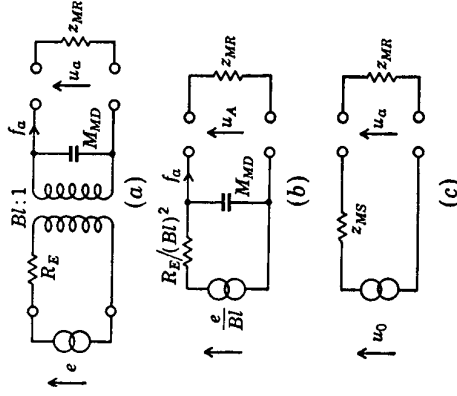


FIG. 3.42. Analogous circuits for a simplified moving-coil loudspeaker radiating sound into air. (a) Analogous circuit. (b) Same, with transformer removed. (c) Same, reduced to its Thévenin's equivalent.

2. Short-circuit the generator e without changing the mesh impedance in that part of the electrical circuit. Then determine the mobility z_{MS} looking back into the output terminals of the loudspeaker. For example, z_{MS} for the circuit of Fig. 3.42b is equal to the parallel combination of $1/j\omega M_{MD}$ and $R_E/(Bl)^2$, that is,

$$z_{MS} = \frac{R_E}{j\omega M_{MD}R_E + (Bl)^2} \quad (3.40)$$

The Thévenin's equivalent circuit for the loudspeaker (looking into the diaphragm) is shown schematically in Fig. 3.42c, where u_0 and the mobility z_{MS} are given by Eqs. (3.39) and (3.40), respectively.

The application of Thévenin's theorem as discussed above is an example of how general theorems originally applying to linear passive electrical

networks can be applied to great advantage to the analogs of mechanical and acoustic systems including transducers.

3.10. Energy and Power Relations. *Electrical Elements.* The expressions for energy stored in the inductance and capacitance elements of electrical circuits are familiar to most students from fundamental studies in physics and circuit theory. They are

$$\text{Instantaneous magnetic stored energy} = T(t) = \frac{1}{2}L|i(t)|^2 \quad (3.41)$$

$$\text{Instantaneous electric stored energy} = V(t) = \frac{1}{2}C|e(t)|^2 \quad (3.42)$$

where $i(t)$ and $e(t)$ are, respectively, the instantaneous current in the inductance and the instantaneous voltage across the capacitance.

In the steady state for an angular frequency ω , these equations become

$$T(t) = \frac{1}{2}L|i|^2(1 + \cos 2\omega t) \quad (3.43)$$

$$V(t) = \frac{1}{2}C|e|^2(1 + \cos 2\omega t) \quad (3.44)$$

where $|i|$ and $|e|$ are the rms magnitude of the complex current through and voltage across the elements L and C , respectively. The quantities T and V have a constant component, and a component which alternates at double frequency. On the average, the alternating component is zero, so that

$$T_{\text{ave}} = \frac{1}{2}L|i|^2 \quad \text{watt-sec} \quad (3.45)$$

$$V_{\text{ave}} = \frac{1}{2}C|e|^2 \quad \text{watt-sec} \quad (3.46)$$

On the average, power is dissipated only in resistive elements. The instantaneous power $W(t)$ dissipated in a resistance R by a sinusoidal current is

$$W(t) = R|i|^2(1 + \cos 2\omega t) \quad (3.47)$$

On the average, the alternating component is zero, so that

$$W_{\text{ave}} = R|i|^2 \quad \text{watts} \quad (3.48)$$

Mechanical and Acoustical Elements. From basic mechanics, the student has also become acquainted with the energy and power relations for the mechanical elements: mass, compliance, and resistance. A summary of the steady-state values of W_{ave} , T_{ave} , and V_{ave} for electrical, mechanical, and acoustical elements is given in Table 3.4. It is interesting to see that T_{ave} for the mobility-type analogy has the same form as V_{ave} for the impedance-type analogy, and vice versa. We are now ready to use these energy and power concepts in the analysis of complete electro-mechano-acoustical circuits.

Energy and Power Functions for Combined Circuits. In a complete electro-mechano-acoustical circuit for a device such as a loudspeaker, the energy and power relations for the individual elements may be used to determine the total active and reactive power supplied by the generator.

TABLE 3.4. Average Values of Power Dissipated and Energy Stored†

Element (see Table 3.2)	Electrical	Type of analogy	Mechanical	Acoustical
W_{ave}	$R i ^2$	Mobility	$\tau_M f ^2$	$r_A p ^2$
		Impedance	$R_M u ^2$	$R_A U ^2$
T_{ave}	$\frac{1}{2}L i ^2$	Mobility	$\frac{1}{2}C_M f ^2$	$\frac{1}{2}C_A p ^2$
		Impedance	$\frac{1}{2}M_M u ^2$	$\frac{1}{2}M_A U ^2$
V_{ave}	$\frac{1}{2}C e ^2$	Mobility	$\frac{1}{2}C_M f ^2$	$\frac{1}{2}C_A p ^2$
		Impedance	$\frac{1}{2}M_M u ^2$	$\frac{1}{2}M_A U ^2$

† Rms values are used for time-varying quantities.

As an example, let us consider in detail the loudspeaker circuit shown in Fig. 3.43. The transducer is of the electromagnetic-mechanical type, which requires the use of the mobility analogy in the mechanical and therefore in the acoustical parts of the circuit.

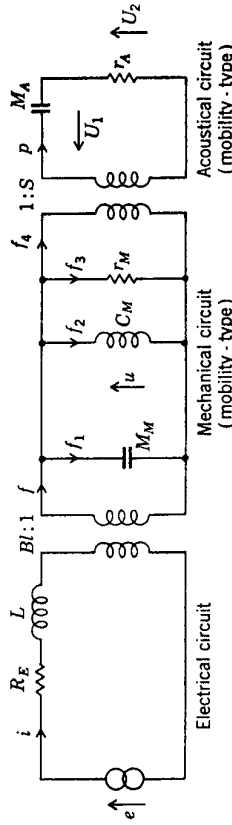


Fig. 3.43. Complete analogous circuit for a direct-radiator loudspeaker of the moving-coil type.

Logically, the total power supplied by the generator e to the circuit must be equal to the sums of the powers dissipated in the resistive elements because the circuit is passive. The power delivered by the loudspeaker to the air is given by the power dissipated in the acoustic responsiveness r_A . From Table 3.4 we find for the mobility case that the total power for the circuit of Fig. 3.43 is equal to

$$W_{\text{ave}} = R_E|i|^2 + \tau_M|f_3|^2 + r_A|p|^2 \quad (3.49)$$

We know that the total amount of inductive energy T_{ave} stored in the circuit must be the sum of the energies stored in the individual inductance-type elements. From Table 3.4 we see for the mobility analogy that the total T_{ave} of Fig. 3.43 is equal to

$$T_{\text{ave}} = \frac{1}{2}L|i|^2 + \frac{1}{2}C_M|f_2|^2 \quad (3.50)$$

$$V_{avz} = \frac{1}{2} M_M |u|^2 + \frac{1}{2} M_A |U_1|^2 \quad (3.51)$$

By way of justification for the choice of mks units made early in this text, it should be noted that direct addition of electrical, mechanical, and acoustic powers and energies is possible in Eqs. (3.49) to (3.51) provided all quantities are given in the mks system. By contrast, if volts and amperes were used in the electrical circuit and egs units in the mechanical and acoustical circuits, energy would be in joules in the electrical circuit and in ergs in the mechanical and acoustical circuits. Conversion of ergs to joules by multiplying the number of ergs by 10^{-7} would be necessary before addition were possible.

Active and Reactive Power: Vector Power. It is common in electrical-circuit theory to speak of vector power: the quadrature combination of active and reactive power. By definition the vector power supplied by the generator is the product of the current and the complex conjugate of the voltage at the source.

$$\text{Vector power} = W_{avz} + jQ_{avz} = e^* i \quad (3.52)$$

where e^* is the complex conjugate of the rms voltage e at the source and i is the rms current at the source. Note that if $e = |e| \angle \phi$, then $e^* = |e| \angle -\phi$.

Since $i = e/Z$, one may alternatively write

$$W_{avz} + jQ_{avz} = \frac{|e|^2}{Z} \quad (3.53)$$

where $|e|$ is the rms magnitude of the voltage across the complex impedance Z . Clearly the active power W_{avz} in a linear passive circuit must always be positive. The reactive power, however, may have either sign, being *positive in a predominantly capacitive-type circuit and negative in a predominantly inductive one*. The units of W_{avz} are watts, and the units of Q_{avz} are called "vars"—a contraction of "volt-ampere reactive." Instead of Eq. (3.53) it is also possible to write

$$W_{avz} + jQ_{avz} = |i|^2 Z^* \quad (3.54)$$

where Z^* is the complex conjugate of Z . For example, if $Z = R + jX$, then $Z^* = R - jX$.

In a complex circuit, such as that given in Fig. 3.43, the total vector power supplied by the generator is found by summing the vector powers supplied to each element in the circuit. For a purely electrical circuit, we write

$$W_{avz} + jQ_{avz} = \sum e_k^* i_k = \sum |i_k|^2 Z_k^* = \sum \frac{|e_k|^2}{Z_k} \quad (3.55)$$

where i_k is the complex current in the k th element of impedance Z_k . The voltage across the k th element is e_k . A similar equation holds for electro-mechano-acoustical circuits. For example, from Fig. 3.43, remembering that we have the mobility analogy, we find that

$$W_{avz} + jQ_{avz} = |i|^2 (R_F - jI\omega) - \frac{|f_1|^2}{jM_M\omega} - |f_2|^2 jC_M\omega + |f_3|^2 r_M + |p|^2 \left(\frac{j}{M_A\omega} + r_A \right)$$

or

$$W_{avz} + jQ_{avz} = (|i|^2 R_F + |f_3|^2 r_M + |p|^2 r_A) + 2j\omega \left(-\frac{1}{2} L |i|^2 + \frac{1}{2} \frac{|f_1|^2}{M_M\omega^2} - \frac{1}{2} |f_2|^2 C_M + \frac{1}{2} \frac{|p|^2}{M_A\omega^2} \right) \quad (3.56)$$

We see that the quantities contained within the first parentheses are exactly the same as those found in Eq. (3.49). Consider the terms in the second parentheses. From Eq. (3.2) we see that $|f_1|^2 = \omega^2 M_M^2 |u|^2$ and from Eq. (3.22) that $|p|^2 = \omega^2 M_A^2 |U_1|^2$. Hence, comparison of the second parentheses of Eq. (3.56) with Eqs. (3.50) and (3.51) shows that the value in these second parentheses is equal to $V_{avz} - T_{avz}$.

In general, the reactive power is

$$Q_{avz} = 2\omega(V_{avz} - T_{avz}) \quad (3.57)$$

The total stored energies V_{avz} and T_{avz} are found by the procedures described in connection with Eqs. (3.50) and (3.51). It should be noted that *at resonance* the average energy stored in the inductance-type elements T_{avz} is just equal to the average energy stored in the capacitance-type elements V_{avz} so that the total reactive power supplied by the generator is zero.

Finally, it is seen from Eqs. (3.54) and (3.57) that the impedance presented to the generator is equal to

$$Z = \frac{W_{avz} - jQ_{avz}}{|i|^2} = \frac{W_{avz} + j^2\omega(T_{avz} - V_{avz})}{|i|^2} \quad (3.58)$$

3.11. Transducer Impedances. Let us look a little closer at the impedances at the terminals of electromechanical transducers. It has become popular in recent years for electrical-circuit specialists to express the equations for their circuits in matrix form. The matrix notation is a condensed manner of writing systems of linear equations.⁷ We shall express the properties of transducers in matrix form for those who are familiar with this concept. An explanation of the various mathematical operations to be performed with matrices is beyond the scope of this book.

⁷ P. LeCorbeiller, "Matrix Analysis of Electric Networks," Harvard University Press, Cambridge, Mass., and John Wiley & Sons, Inc., New York, 1950.

The student not familiar with matrix theory is advised to deal directly with the simultaneous equations from which the matrix is derived. A knowledge of matrix theory is not necessary, however, for an understanding of any material in this text.

Let us determine the impedance matrix for the electromechanical transducer of Fig. 3.44a. In that circuit Z_E is the electrical impedance measured with the mechanical terminals "blocked," that is, $u = 0$; z_M is the mechanical mobility of the mechanical elements in the transducer measured with the electrical circuit "open-circuited"; and z_L is the mechanical mobility of the acoustic load on the diaphragm. The

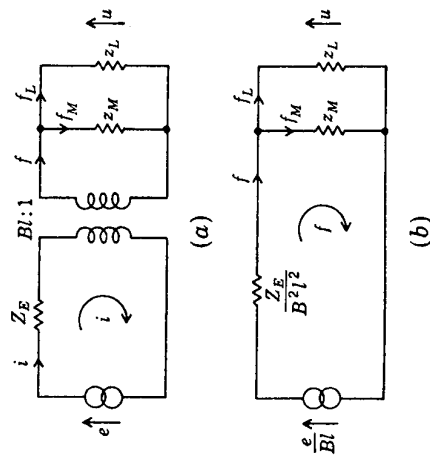


FIG. 3.44. Analogous circuits for an electromechanical-mechanical transducer. The mechanical side is of the mobility type.

quantity Bl is the product of the flux density times the effective length of the wire cutting the lines of force perpendicularly.

Removing the transformer from Fig. 3.44a yields the two-mesh circuit of Fig. 3.44b. The equations for this circuit are

$$e = iZ_E + uBl \tag{3.59}$$

$$0 = -iBl + u(Z_M + Z_L) \tag{3.60}$$

where $Z_M = 1/z_M$, $Z_L = 1/z_L$, and $f = Bl\dot{u}$. The impedance matrix is drawn from these equations and is a square array of four impedances.

$$Z = \begin{bmatrix} Z_E & Bl \\ -Bl & Z_M + Z_L \end{bmatrix} \tag{3.61}$$

The total electrical impedance Z_{ET} as viewed from the voltage generator is found from the matrix or from Eqs. (3.59) and (3.60) to be

$$Z_{ET} = Z_E + \frac{(Bl)^2}{Z_M + Z_L} \tag{3.62}$$

The second term on the right-hand side is usually called the *motional impedance* because, if the mechanical side is blocked so there is no movement, then $Z_{ET} = Z_E$. This equation illustrates a striking fact, *viz.*, that the electromagnetic transducer is an *impedance inverter*. By an inverter we mean that a mass reactance on the mechanical side becomes a capacitance reactance when referred to the electrical side of the transformer, and vice versa. Similarly, an inductance on the electrical side reflects through the transformer as a mechanical compliance. These statements are well illustrated by the circuit of Fig. 3.47.

For an electrostatic-mechanical transducer of the type shown in Fig. 3.45, the circuit equations are

$$e_0 = iZ_E - u \frac{\tau}{j\omega} \tag{3.63}$$

$$0 = -i \frac{\tau}{j\omega} + u(Z_M + Z_L) \tag{3.64}$$

where

$$Z_E \equiv Z'_E + \frac{1}{j\omega C'_E}$$

= the electrical impedance with the mechanical motion blocked

Z_L = mechanical impedance of the acoustical load on the diaphragm

$Z_M \equiv R_M + j\omega M_M + \frac{1}{j\omega C_M}$ = mechanical impedance of the mechanical elements in the transducer measured with $i = 0$

$C_M = \frac{C'_M}{1 + C'_M C'_E \tau^2}$ = mechanical compliance in the transducer with $i = 0$

The impedance matrix is

$$Z = \begin{bmatrix} Z_E & -\tau/j\omega \\ -\tau/j\omega & Z_M + Z_L \end{bmatrix} \tag{3.65}$$

This matrix is symmetrical about the main diagonal, as for any ordinary electrical passive network. By contrast matrix (3.61) is skew-symmetrical. For transient problems, replace $j\omega$ by the operator $s = d/dt$.

The impedance matrix for the electrostatic transducer is almost identical in form to that for the electromagnetic transducer, the difference being that the mutual terms have the same sign, as contrasted to opposite signs for the electromagnetic case.

For the electrostatic transducer the total impedance is

$$Z_{ET} = Z_E - \frac{\tau^2/j^2\omega^2}{Z_M + Z_L} = Z_E + \frac{\tau^2/\omega^2}{Z_M + Z_L} \tag{3.66}$$

The second term on the right-hand side is called the motional impedance as before.

Again we see that the transducer acts as a sort of *impedance* inverter. An added positive mechanical reactance (+ X_M) comes through the transducer as a negative electrical reactance.

Some interesting facts can be illustrated by assuming that we have an electrostatic and an electromagnetic transducer, each stiffness controlled on the mechanical side so that

$$Z_M + Z_L = \frac{1}{j\omega C_{M1}} \tag{3.67}$$

Substitution of Eq. (3.67) into (3.62) yields

$$Z_{ET} = Z_E + j\omega(B^2)^2 C_{M1} \tag{3.68}$$

The mechanical compliance C_M appears from the electrical side to be an inductance with a magnitude $B^2)^2 C_{M1}$. Substitute now Eq. (3.67) into (3.66).

$$Z_{ET} = Z_E + j \frac{\tau^2 C_{M1}}{\omega} \tag{3.69}$$

The mechanical compliance C_M of this transducer appears from the electrical side to be a negative capacitance, that is to say, C_{M1} appears to be

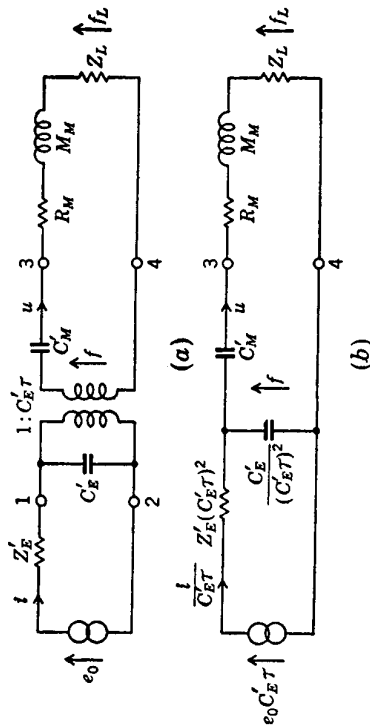


FIG. 3.45. Analogous circuits for an electrostatic-mechanical transducer. The mechanical side is of the impedance type.

an inductance with a magnitude that varies inversely with ω^2 . The effect of this is simply to reduce the value of C_M . Another way of looking at this is to note from Fig. 3.45 that with $R_M = M_M = 0$ and $Z_L = 1/j\omega C_{ML}$, the total compliance is less than C_M because of the added compliance C_{ML} .

3.12. Combinations of Electrostatic and Electromagnetic Transducers. The engineer sometimes is called upon to join an electromagnetic and an electrostatic transducer together both electrically and mechanically, say,

by a feedback loop. Inspection of Figs. 3.44a and 3.45a reveals that it is not possible to make such a connection directly, because we have the mobility-type analogy on the secondary side in one circuit and the impedance-type analogy on that side in the other.

One method has been advanced for overcoming this difficulty.⁸ Inspection of the impedance matrices [Eqs. (3.61) and (3.65)] reveals that the same circuit could be used for both types of devices provided some means were introduced for changing one of the signs of the mutual terms. To do this, the " β operator" will be introduced.

The Operator β . The method for transforming one of the impedance matrices into the other is to multiply the mutual terms of one matrix by an arbitrary operator β . This operator is a 90° "direction rotator," and

$$\begin{aligned} \beta^2 &= -1 \\ \beta^4 &= 1 \\ j\beta &= -\beta j \end{aligned} \tag{3.70}$$

For example, the circuit for an electrostatic transducer can be drawn like that shown in Fig. 3.46. The impedance matrix for that circuit is

$$Z = \begin{bmatrix} Z_E & \tau\beta/j\omega \\ -(\tau\beta/j\omega) & Z_M + Z_L \end{bmatrix} \tag{3.71}$$

The total impedance of that circuit, with the application of Eq. (3.71) above, is that given in Eq. (3.66). As a word of caution, the quantity β^2

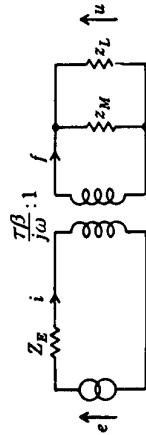


FIG. 3.46. Analogous circuit of the mobility type, using the β operator, for handling electrostatic-mechanical transducers. For use with transient problems, replace $j\omega$ by the operator s .

should not be replaced by (-1) until the equations have been reduced to their final form. This avoids the problem of having to decide whether a negative number should be replaced by j or β when a square root is taken. In Fig. 3.46, going from left to right, $u = iz \tau/j\omega/\beta$, and, going from right to left, the open-circuit voltage $e_0 = f\sigma z/j\omega/-\beta$, so that the transfer impedances in the two directions are the negative of each other.

When both β and j appear in the transformation ratio, the values of the stored energy components T_{av} and V_{av} are the same as those found when

⁸ F. V. Hunt, "Symmetry in the Equations for Electromechanical Coupling," Paper B1, presented at the thirty-ninth meeting of the Acoustical Society of America. Professor Hunt has used this concept of a β operator in a variety of useful ways.

neither appear in the transformation ratio, because

$$j^2\beta^2 = \frac{j^2}{\beta^2} = 1 \tag{3.72}$$

Analytically the results for power and energy are the same as were found in connection with Eqs. (3.50), (3.51), (3.56), and (3.57).

In a similar manner, the circuit for an electromagnetic transducer may be drawn like that of Fig. 3.37b if the transducer ratio is $jB\beta C_M\omega \cdot 1$. In this case, the impedance matrix would be

$$Z = \begin{bmatrix} Z_E & -B\beta \\ -B\beta & Z_M + Z_L \end{bmatrix} \tag{3.73}$$

The total electrical impedance is found from this matrix and is the same as that given by Eq. (3.62).

Example 3.9. A moving-coil earphone actuated by frequencies above its first resonance frequency may be represented by the circuit of Fig. 3.42a. Its mechanical and electrical characteristics are

- $R_E = 10$ ohms
- $B = 10^4$ gauss (1 weber/m²)
- $l = 3$ m
- $M_{MD} = 2$ g
- $z_{MR} = j\omega 2.7 \times 10^{-4}$ m/newton-sec

where z_{MR} is the mobility that the diaphragm sees when the earphone is on the ear, M_{MD} is the mass of the diaphragm, R_E and l are the resistance and the length of wire

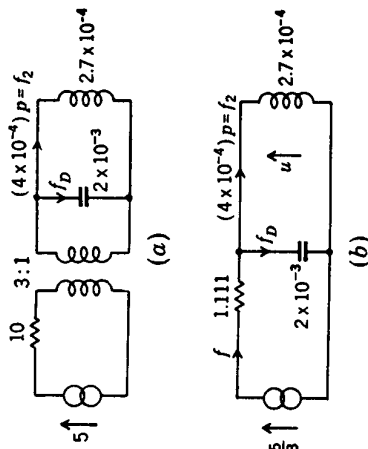


FIG. 3.47. Analogous circuits for Example 3.9.

wound on the voice coil, and B is the flux density cut by the moving coil. Determine the sound pressure level produced at the ear at 1000 cps when the earphone is operated from a very low impedance amplifier with an output voltage of 5 volts. Assume that the area of the diaphragm is 4 cm².

Solution. The circuit diagram for the earphone with the element sizes given in mks units is shown in Fig. 3.47a. Eliminating the transformer gives the circuit of

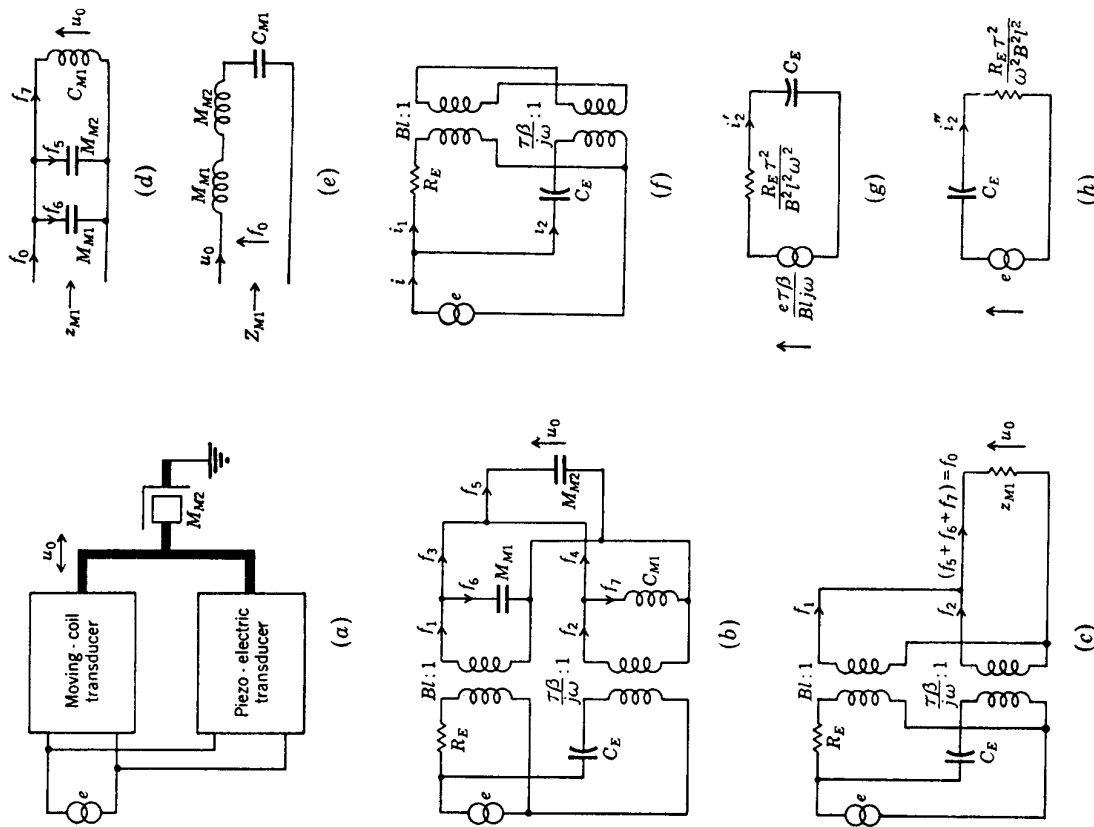


FIG. 3.48. Combined electrostatic-electromagnetic transducers. (a) Block mechanical diagram of the device. (b) Analogous circuit with mobilities on mechanical side. The β operator is used for the piezoelectric transducer. (c) Same as (b), except that z_{M1} replaces the three parallel mobilities as shown by (d). (e) Dual of (d). (f) Because the circuit of (d) has infinite mobility, (b) simplifies to this form. (g) and (h) Solution of (f) by superposition.

Fig. 3.47b. Solving, we get

$$\begin{aligned}
 u &= f_{zMR} = (4 \times 10^{-4})j6280(2.7 \times 10^{-4}) \\
 &= j6.78 \times 10^{-4}p \\
 f_D &= j\omega M_{MM} = -8.54 \times 10^{-3}p \\
 f &= f_D + f_z = -8.14 \times 10^{-3}p \\
 \frac{1}{2} &= u + 1.111f = p(j6.78 \times 10^{-4} - 9 \times 10^{-3}) \\
 |p| &= \frac{1.667 \times 10^2}{0.9} \doteq 185 \text{ newton/m}^2
 \end{aligned}$$

$$\text{SPL} = 20 \log \frac{185}{2 \times 10^{-5}} = 139.3 \text{ db re } 0.0002 \text{ microbar}$$

Example 3.10. Two transducers, one a piezoelectric crystal and the other a moving coil in a magnetic field, are connected to a mass M_{M2} of 1.533 kg as shown in Fig. 3.48a. Determine the stored electrical energy in the condenser C_E at 100 cps for the following constants:

- $e = 1$ volt
- $R_E = 10$ ohms
- $B = 1$ weber/m²
- $l = 30$ m
- $C_E = 4 \times 10^{-9}$ farad
- $M_{M1} = 1.0$ kg
- $C_{M1} = 10^{-6}$ m/newton
- $\tau = 1.28 \times 10^7$
- $\omega = 628$ radians/sec

Solution. The transducers are shown schematically in (b) of Fig. 3.48. A further simplification of this diagram is shown in (c). Let us determine the value of z_{M1} first. We note that the dual of (d) is given by (e).

$$\begin{aligned}
 \frac{1}{z_{M1}} &= Z_{M1} = j\omega(M_{M1} + M_{M2}) - j \frac{1}{C_{M1}\omega} \\
 &= j(629 + 964) - j1593 = 0
 \end{aligned}$$

In other words, the mobility is infinite at 100 cps. Hence, circuit (c) simplifies to that shown in (f). By superposition, i_2 can be broken into two parts i_2' and i_2'' given by the two circuits (g) and (h), so that $i_2 = i_2' - i_2''$.

$$\begin{aligned}
 \frac{\tau}{B l \omega} &= \frac{1.28 \times 10^7}{1 \times 30 \times 628} = 680 \\
 \frac{1}{\omega C_E} &= 4 \times 10^6 \\
 i_2' &= \frac{e \tau B / B l j \omega}{(R_{ET}' / B^2 l^2 \omega^2) + (1 / j \omega C_E)} = \frac{e B l \omega}{j l e \tau} = \frac{1}{j 6800} \\
 i_2'' &= \frac{e \omega^2 B^2 l^2}{R_{ET}''} = \frac{(10)(680)^2}{1} = 4.64 \times 10^6 \\
 i_2 &= i_2' - i_2'' = j1.47 \times 10^{-4} \\
 |i_2| &= 1.47 \times 10^{-4} \text{ amp}
 \end{aligned}$$

The voltage drop across the capacitor is

$$|e_c| = 1.47 \times 10^{-4} \times 4 \times 10^6 = 59 \text{ volts}$$

The electric stored energy on the capacitor C_E is

$$\frac{1}{2} C_E |e_c|^2 = 2 \times 10^{-9} \times 3.48 \times 10^3 = 7 \times 10^{-6} \text{ watt-sec}$$

CHAPTER 4

RADIATION OF SOUND

In order fully to specify a source of sound, we need to know, in addition to other properties, its directivity characteristics at all frequencies of interest. Some sources are nondirective, that is to say, they radiate sound equally in all directions and as such are called spherical radiators. Others may be highly directional, either because their size is naturally large compared to a wavelength or because of special design.

The most elementary radiator of sound is a spherical source whose radius is small compared to one-sixth of a wavelength. Such a radiator is called a *simple source* or a *point source*. Its properties are specified by the magnitude of the velocity of its surface and by its phase relative to some reference. More complicated sources such as plane or curved radiators may be treated analytically as a combination of simple sources, each with its own surface velocity and phase.

A particularly important consideration in the design of loudspeakers and horns is their directivity characteristics. This chapter serves as an important basis for later chapters dealing with loudspeakers, baffles, horns, and noise sources.

The basic concepts governing radiation of sound must be grasped thoroughly at the outset. It is then possible to reason from those concepts in deducing the performance of any particular equipment or in planning new systems. Examples of measured radiation patterns for common loudspeakers are given here as evidence of the applicability of the basic concepts.

PART X Directivity Patterns

The *directivity pattern* of a transducer used for the emission or for reception of sound is a description, usually presented graphically, of the response of the transducer as a function of the direction of the transmitted or incident sound waves in a specified plane and at a specified frequency.