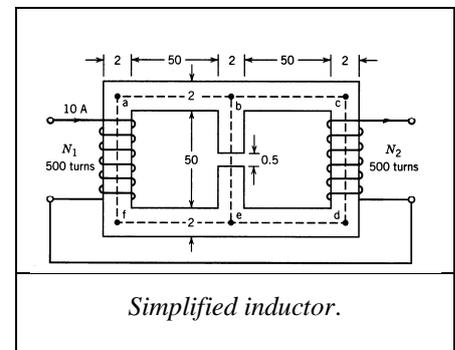



1. Explain the following concepts, use drawings and equations when adequate.
 - a) Construction and operation principles of a synchronous generator. (Stator, rotor, windings, frequencies, armature current, etc...) (2 p.)
 - b) List the loss components in an asynchronous motor. Explain why and where they occur. (2 p.)
 - c) Explain the three running modes of operation of an induction machine by drawing the Torque-Speed/Slip curve and give the range of the slip for each mode of operation (2 p.)
 - d) What are the necessary conditions for connecting (synchronizing) a running synchronous generator to the infinite bus? What happens if any of them is not satisfied and why? (2 p.)
 - e) Explain how the voltage builds-up in a self-excited (shunt) DC-generator and list the three conditions necessary for this voltage to build-up (hint: magnetization curve, remanence) (2 p.)
 - f) Explain how the power factor of a synchronous machine can be controlled, while the machine is delivering a constant active power. Draw the phasor diagram of the machine at unity power factor and lagging power factor (hint: use the terminal voltage as reference, 0 deg) (2p.).

2. In the simplified inductor of the figure, the relative permeability of the core is 1200. All dimensions are in centimeters, and the magnetic material has a square cross section area (2x2 cm). Neglect fringing and magnetic leakage. Use the dashed line as the average magnetic flux path.



- a) Draw the magnetic equivalent circuit of the inductor and calculate its parameters (2 p.)
- b) Calculate the air gap flux and flux density (2 p.)
- c) Calculate the force acting on one of the air gap ferromagnetic surfaces. (2 p.)

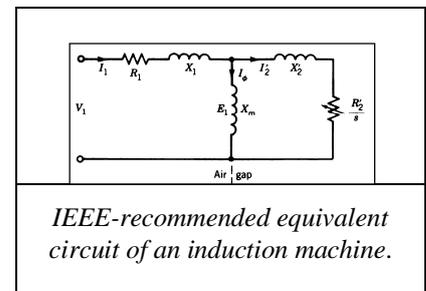3. A three phases, 250 kW, 460 V, 60 Hz, eight poles, star-connected induction machine is connected to a 460 V infinite bus and is running as a generator at a slip $s = -2,5\%$. The equivalent circuit of the machine (Fig. 3) has the following parameters



$$R_1 = 0,015\Omega; \quad R_2' = 0,035\Omega;$$

$$X_1 = 0,145\Omega; \quad X_2' = 0,145\Omega; \quad X_m = 6,5\Omega$$

- a) Determine the speed of the rotor (2 p.)
 - b) Determine the power delivered to the infinite bus and the power factor (2 p.)
 - c) Determine the efficiency of the generator. The rotational and core losses are 3 kW (2 p.)
4. A 1 MVA, 3 phases, 2300 V, 60 Hz, 10 poles, star-connected cylindrical-rotor synchronous motor is connected to an infinite bus. The synchronous reactance is 4,23 Ω . The synchronous motor delivers 746 kW and operates at 0,85 power factor **leading**. All losses may be neglected.
 - a) Determine the armature current I_a (2p)
 - b) Determine the excitation voltage E_f and the load angle δ . (2 p.)
 - c) Determine the maximum power the motor can deliver for the excitation of part (b). (2 p.)

Evaluation:

Grade	Lower limit	Upper limit
0	0	13
1	14	16
2	17	19
3	20	22
4	23	26
5	27	30

Some useful formulas and drawings:

Magnetic reluctance: $R = \frac{l}{\mu A}$


Magnetomotive force: $F = Ni$

Force pressure: $F_m = \frac{B_g^2}{2\mu_0}$

Speed of AC-machine: $n = \frac{120 f}{p}$ (p is the number of poles!)

Slip of induction machine: $s = \frac{n_s - n}{n_s}$

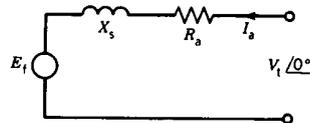Equivalent circuit of a synchronous motor:



Convention: lagging reactive power positive -- > phase angle of current negative

AC active power: $P = 3VI \cos \phi$