



**Aalto University**  
School of Electrical  
Engineering

# Lecture 4: Pulse-Width Modulation and Current Control

ELEC-E8402 Control of Electric Drives and Power Converters

Marko Hinkkanen

Spring 2018

# Learning Outcomes

After this lecture and exercises you will be able to:

- ▶ Explain the difference between the standard suboscillation PWM method and the symmetrical suboscillation PWM method
- ▶ Explain the principle of three-phase synchronous-frame current control
- ▶ Understand operation of the current controller in Homework Assignment 1

The current controller is presented here for induction motors, but it can be easily extended for other AC machines and for grid converters (equipped with L filter).

# Outline


3-Phase Inverter

Pulse-Width Modulation


Current Control

Anti-Windup, Sampling, PWM Update

# 3-Phase Inverter

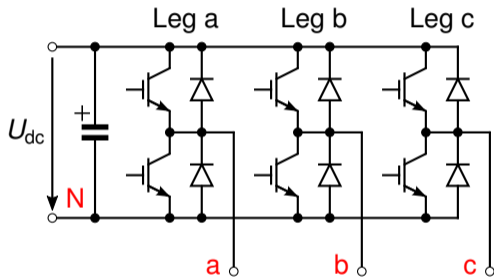
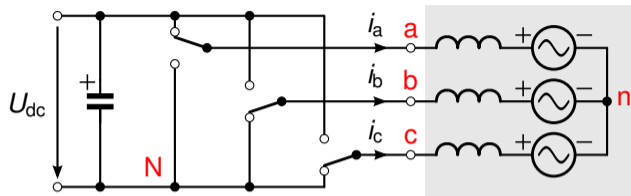
# Space Vector of the Converter Output Voltages



- ▶ Zero-sequence voltage does not affect the phase currents
- ▶ Reference potential of the phase voltages can be freely chosen

$$\underline{u}_s^s = \frac{2}{3} \left( u_{an} + u_{bn} e^{j2\pi/3} + u_{cn} e^{j4\pi/3} \right) \quad \text{Neutral } n \text{ as a reference}$$
$$= \frac{2}{3} \left( u_{aN} + u_{bN} e^{j2\pi/3} + u_{cN} e^{j4\pi/3} \right) \quad \text{Negative DC bus } N \text{ as a reference}$$


► Converter output voltage vector

$$\begin{aligned}\underline{u}_s^s &= \frac{2}{3} \left( u_{aN} + u_{bN}e^{j2\pi/3} + u_{cN}e^{j4\pi/3} \right) \\ &= \frac{2}{3} \left( q_a + q_b e^{j2\pi/3} + q_c e^{j4\pi/3} \right) U_{dc}\end{aligned}$$

where  $q_{abc}$  are the switching states (either 0 or 1)

► Vector (1, 0, 0) as an example
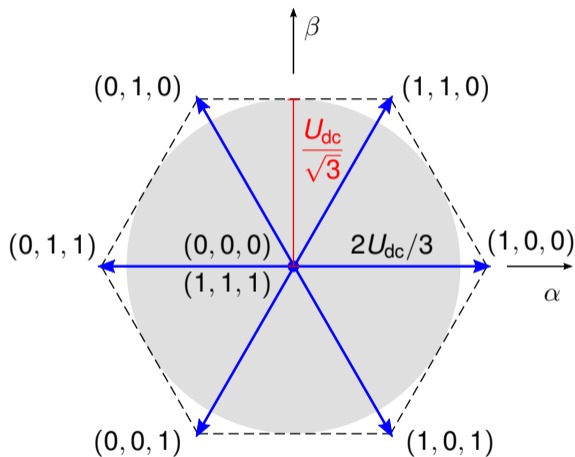
$$\underline{u}_s^s = \frac{2U_{dc}}{3}$$



## Switching-Cycle Averaged Voltage

- ▶ Using PWM, any voltage vector inside the voltage hexagon can be produced in average over the switching period

$$\underline{\bar{u}}_s^s = \frac{2}{3} \left( d_a + d_b e^{j2\pi/3} + d_c e^{j4\pi/3} \right) U_{dc}$$

where  $d_{abc}$  are the duty ratios (between 0...1)

- ▶ Maximum magnitude of the voltage vector is  $u_{\max} = U_{dc}/\sqrt{3}$  in linear modulation (the circle inside the hexagon)
- ▶ PWM can be implemented, e.g., using the carrier comparison
- ▶ Mainly switching-cycle averaged quantities will be needed in this course (overlining will be omitted for simplicity)

# Outline

3-Phase Inverter

**Pulse-Width Modulation**

Current Control

Anti-Windup, Sampling, PWM Update




# Suboscillation Method

- ▶ Duty ratios for carrier comparison

$$d_a = \frac{1}{2} + \frac{u_{a,\text{ref}}}{U_{\text{dc}}} \quad d_b = \frac{1}{2} + \frac{u_{b,\text{ref}}}{U_{\text{dc}}} \quad d_c = \frac{1}{2} + \frac{u_{c,\text{ref}}}{U_{\text{dc}}}$$

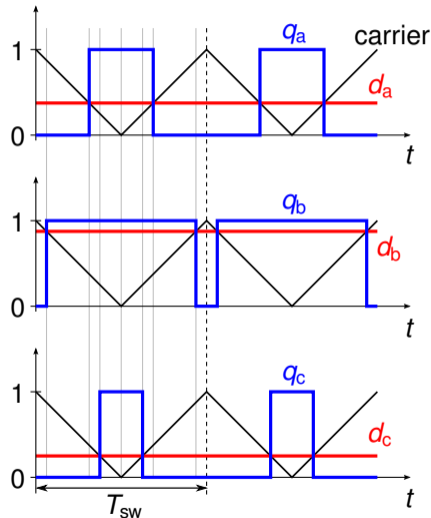- ▶ Voltage vectors during  $T_{\text{sw}}$  in the example:  
 $(0, 0, 0) \rightarrow (0, 1, 0) \rightarrow (1, 1, 0) \rightarrow (1, 1, 1) \rightarrow$   
 $(1, 1, 1) \rightarrow (1, 1, 0) \rightarrow (0, 1, 0) \rightarrow (0, 0, 0)$
- ▶ Problem: **only 87% of the maximum available voltage** can be used!
- ▶ Proper zero-sequence component should be added to utilize all available voltage



# Symmetrical Suboscillation Method

- ▶ Zero sequence

$$u_0 = \frac{\min(u_{a,\text{ref}}, u_{b,\text{ref}}, u_{c,\text{ref}}) + \max(u_{a,\text{ref}}, u_{b,\text{ref}}, u_{c,\text{ref}})}{2}$$

- ▶ Modified voltage references

$$u'_{a,\text{ref}} = u_{a,\text{ref}} - u_0 \quad u'_{b,\text{ref}} = u_{b,\text{ref}} - u_0 \quad u'_{c,\text{ref}} = u_{c,\text{ref}} - u_0$$


- ▶ Duty ratios for carrier comparison

$$d_a = \frac{1}{2} + \frac{u'_{a,\text{ref}}}{U_{\text{dc}}} \quad d_b = \frac{1}{2} + \frac{u'_{b,\text{ref}}}{U_{\text{dc}}} \quad d_c = \frac{1}{2} + \frac{u'_{c,\text{ref}}}{U_{\text{dc}}}$$


- ▶ Whole voltage hexagon can be now used
- ▶ Following example:  $u_{a,\text{ref}} = u_{c,\text{ref}} = -U_{\text{dc}}/4$  and  $u_{b,\text{ref}} = U_{\text{dc}}/2$

---

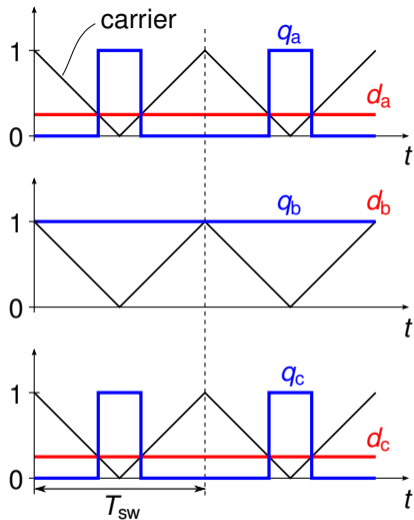The symmetrical suboscillation method is identical to the continuous space-vector PWM.



Suboscillation method

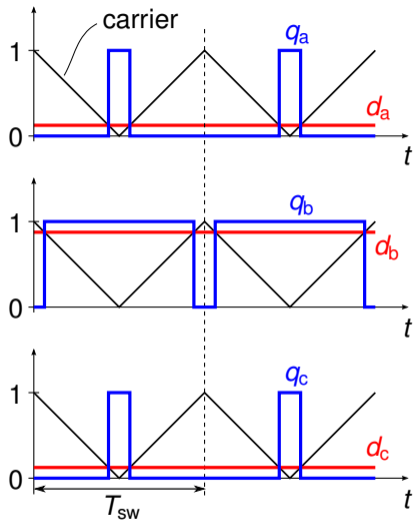

Symmetrical suboscillation method

# Outline


3-Phase Inverter

Pulse-Width Modulation

**Current Control**


Anti-Windup, Sampling, PWM Update
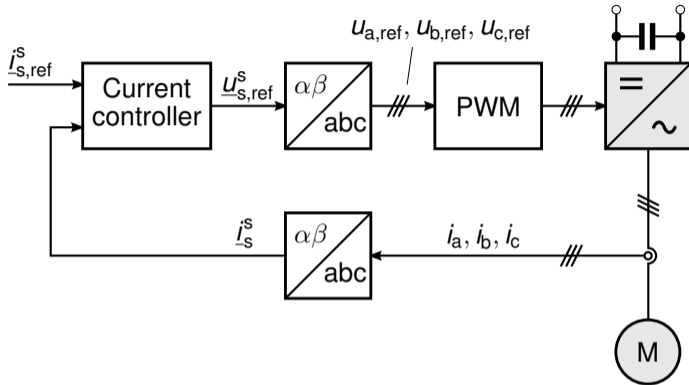
## Current Controller in Stator Coordinates



- ▶ PI controller cannot give zero steady-state error for sinusoidal references
- ▶ Actual current does not follow its reference in the steady state (phase shift and magnitude error)

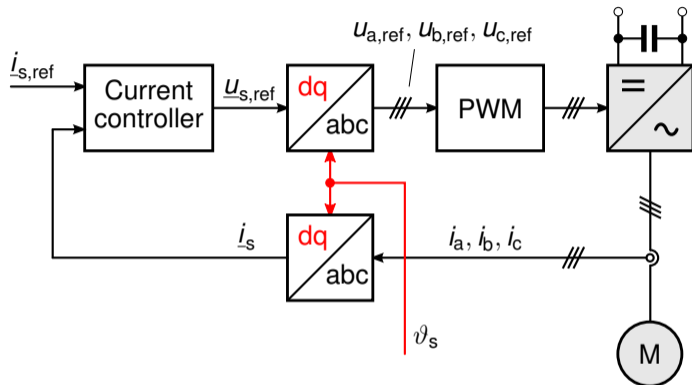
# Current Controller in Synchronous Coordinates



- ▶ DC signals in steady state, no steady-state error
- ▶ Synchronous-frame two-degree-of-freedom PI control will be considered

# Review: Electrical Dynamics of the DC Motor and SPM


DC motor

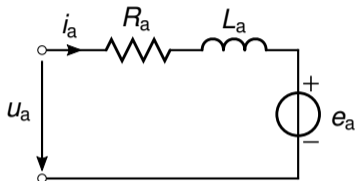

$$L_a \frac{di_a}{dt} = u_a - R_a i_a - e_a$$

$$\text{Back-emf: } e_a = k_f \omega_m$$

SPM in stator coordinates

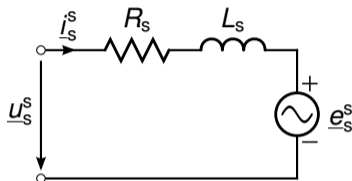

$$L_s \frac{di_s^s}{dt} = \underline{u}_s^s - R_s i_s^s - \underline{e}_s^s$$

$$\text{Back-emf: } \underline{e}_s^s = j\omega_m \psi_f e^{j\vartheta_m}$$

- ▶ Back-emf is a quasi-constant disturbance for the current controller

# Electrical Dynamics of the Induction Motor


- ▶ State-space representation in stator coordinates
- ▶ Stator current and rotor flux as state variables

$$L_{\sigma} \frac{di_{\underline{s}}^s}{dt} = \underline{u}_{\underline{s}}^s - R_{\sigma} i_{\underline{s}}^s - \underbrace{\left( j\omega_m - \frac{R_R}{L_M} \right) \underline{\psi}_{\underline{R}}^s}_{\text{back-emf } \underline{e}_{\underline{s}}^s}$$

$$\frac{d\underline{\psi}_{\underline{R}}^s}{dt} = R_R i_{\underline{s}}^s + \left( j\omega_m - \frac{R_R}{L_M} \right) \underline{\psi}_{\underline{R}}^s$$

where  $R_{\sigma} = R_s + R_R$

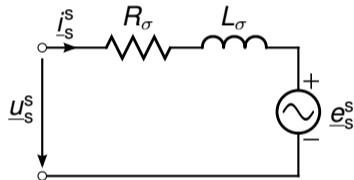- ▶ Rotor-flux magnitude and speed change slowly as compared to the stator current






# General 3-Phase Load

- ▶ Differential equation in synchronous coordinates

$$L \frac{di_s}{dt} + j\omega_s L i_s = \underline{u}_s - R i_s - \underline{e}_s$$

General	SPM	Induction motor
$L$	$L_s$	$L_\sigma$
$R$	$R_s$	$R_\sigma$
$\underline{e}_s$	$j\omega_m \psi_f$	$\left(j\omega_m - \frac{R_R}{L_M}\right) \psi_{-R}$
$\omega_s$	$\omega_m$	$\omega_s$

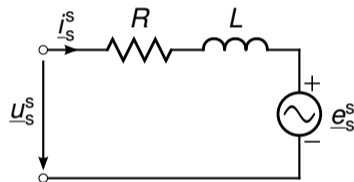


# Transfer Function in Synchronous Coordinates

- ▶ Transfer function of the system to be controlled

$$\frac{\underline{i}_s(s)}{\underline{u}_s(s)} = \underline{Y}(s) = \frac{1}{(s + j\omega_s)L + R}$$

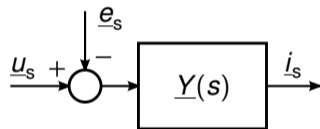- ▶ Back emf  $\underline{e}_s$  can be seen as a load disturbance
- ▶ Similar to the transfer function of the DC motor
- ▶ Ideal converter and PWM will be assumed  
( $\underline{u}_s = \underline{u}_{s,\text{ref}}$ )



# Cross-Coupling Compensation and Active Resistance

$$L \frac{di_s}{dt} = \underline{u}_s - (R + j\omega_s L) \underline{i}_s - \underline{e}_s$$

- ▶ Term  $j\omega_s L \underline{i}_s$  causes the cross-coupling between the axes


$$L \frac{di_d}{dt} = u_d - Ri_d + \omega_s Li_q - e_d$$

$$L \frac{di_q}{dt} = u_q - Ri_q - \omega_s Li_d - e_q$$

- ▶ Cross-coupling is cancelled by adding  $j\omega_s \hat{L} \underline{i}_s$  to the controller output
- ▶ **Active resistance**  $r$  improves disturbance-rejection capability

$$\underline{u}_s = \underline{u}'_s + (j\omega_s \hat{L} - r) \underline{i}_s$$

# Control Algorithm

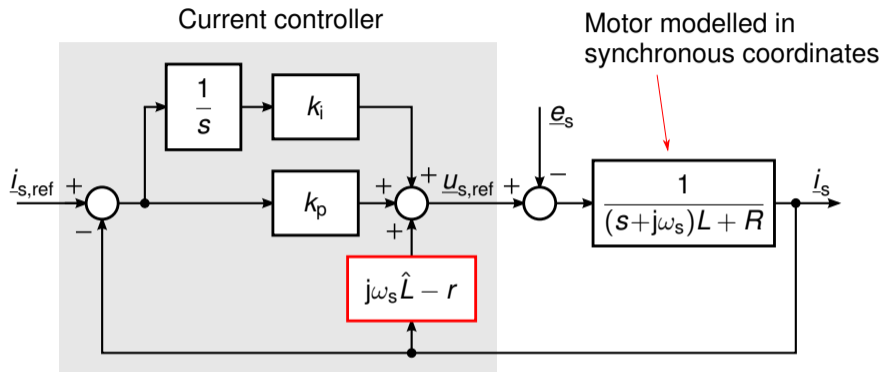

$$\frac{di}{dt} = i_{s,ref} - i_s$$

$$u_{s,ref} = k_p(i_{s,ref} - i_s) + k_i \int (i_{s,ref} - i_s) dt + (j\omega_s \hat{L} - r)i_s$$

# Tuning

- ▶ PI controller sees the system (assuming  $\hat{L} = L$ )

$$L \frac{di_s}{dt} = \underline{u}'_s - (R + r)i_s - \underline{e}_s \quad \text{or} \quad \frac{i_s(s)}{\underline{u}'_s(s)} = Y'(s) = \frac{1}{sL + R + r}$$

- ▶ PI controller and closed-loop transfer functions

$$K(s) = k_p + \frac{k_i}{s} \quad \frac{i_s(s)}{i_{s,\text{ref}}(s)} = \frac{K(s)Y'(s)}{1 + K(s)Y'(s)} = \frac{\alpha_c}{s + \alpha_c}$$

where  $\alpha_c$  is the desired closed-loop bandwidth

- ▶ Gain selection

$$r = \alpha_c \hat{L} - R \quad k_p = \alpha_c \hat{L} \quad k_i = \alpha_c^2 \hat{L}$$

# Outline

3-Phase Inverter

Pulse-Width Modulation

Current Control

Anti-Windup, Sampling, PWM Update

## Anti-Windup


- ▶ Maximum converter output voltage is limited:  $|\underline{u}_s| < u_{\max}$
- ▶ Reference  $|\underline{u}_{s,\text{ref}}|$  may exceed  $u_{\max}$  for large current steps (especially at high rotor speeds due to the large back-emf  $|\underline{e}_s|$ )
- ▶ Realisable voltage vector  $\underline{u}_s$  is obtained from the PWM algorithm
- ▶ Algorithm is augmented with the anti-windup

$$\frac{d\underline{l}}{dt} = \underline{i}_{s,\text{ref}} - \underline{i}_s + \frac{1}{k_p}(\underline{u}_s - \underline{u}_{s,\text{ref}})$$

$$\underline{u}_{s,\text{ref}} = k_p(\underline{i}_{s,\text{ref}} - \underline{i}_s) + k_i \underline{l} + (j\omega_s \hat{L} - r)\underline{i}_s$$

$$\underline{u}_s = \text{PWM}(\underline{u}_{s,\text{ref}}, \vartheta_s)$$


# Back-Calculation Anti-Windup Method

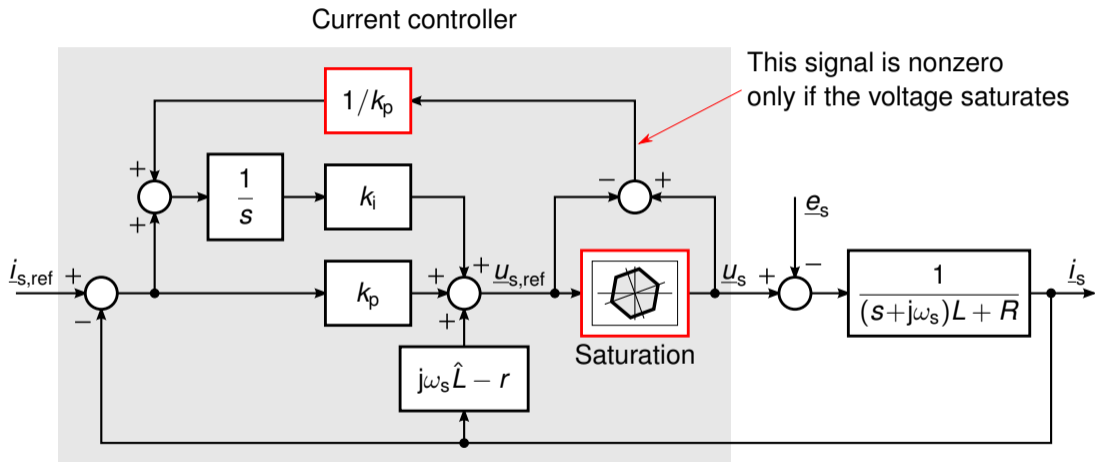


Go through the implementation in Homework Assignment 1. Extra material: M. Hinkkanen, H. A. A. Awan, Z. Qu, T. Tuovinen, and F. Briz, "Current control for synchronous motor drives: Direct discrete-time pole-placement design," *IEEE Trans. Ind. Applicat.*, vol. 52, no. 2, 2016.


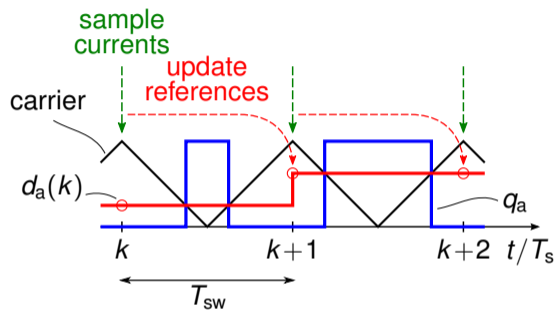
# Discrete Implementation: Synchronous Sampling and PWM Update



Single-update PWM

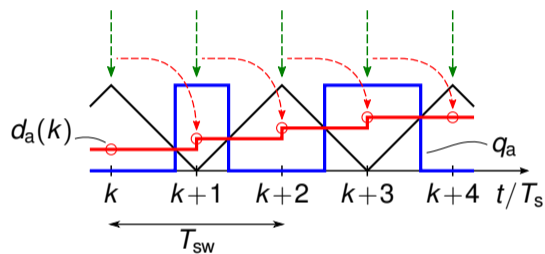

Double-update PWM

- ▶ No switching ripple in the current samples due to synchronous sampling
- ▶ Duty ratios  $d_b$  and  $d_c$  are updated simultaneously with  $d_a$